



**Birla Institute of Technology & Science, Pilani**  
Hyderabad Campus

Innovate

achieve

lead



# CS/ECE/EEE/INSTR F215:Digital Design

**Lecture 28: *Registers***  
***Tue, 16 Nov 2021***

**BITS Pilani**

Hyderabad Campus



**Dr. R. N. Ponnalagu, EEE**

*The Capacity to learn is a gift;*

*The Ability to learn is a skill;*


*The willingness to learn is a choice!*

*- Brian Herbert*
 
# Registers



- Register is an extension of a Flip-flop that can store multiple bits  
Register consists of group of flip-flops and some combinational gates. Each FF is capable of storing one bit of information.  
N-bit register has group of n-FFs capable of storing n-bits of binary information. The logic gates determine how the information is transferred into the register.
- Ex: Used as a Temporary storage element in Microprocessors



Register constructed using four D-FFs

Clock pulse triggers all the FFs

Binary values available at  $I_0I_1I_2I_3$  transferred to register and available as  $A_0A_1A_2A_3$


Four outputs can be sampled at any time to obtain the binary information stored in the register.

Clear input clears all the FFs

How can we store the contents of the register for more than one cycle?

Either inputs must be held constant or clock must be inhibited from the circuit by connecting external gates ( this will involve uneven propagation delays and result in clock skew affect synchronization)

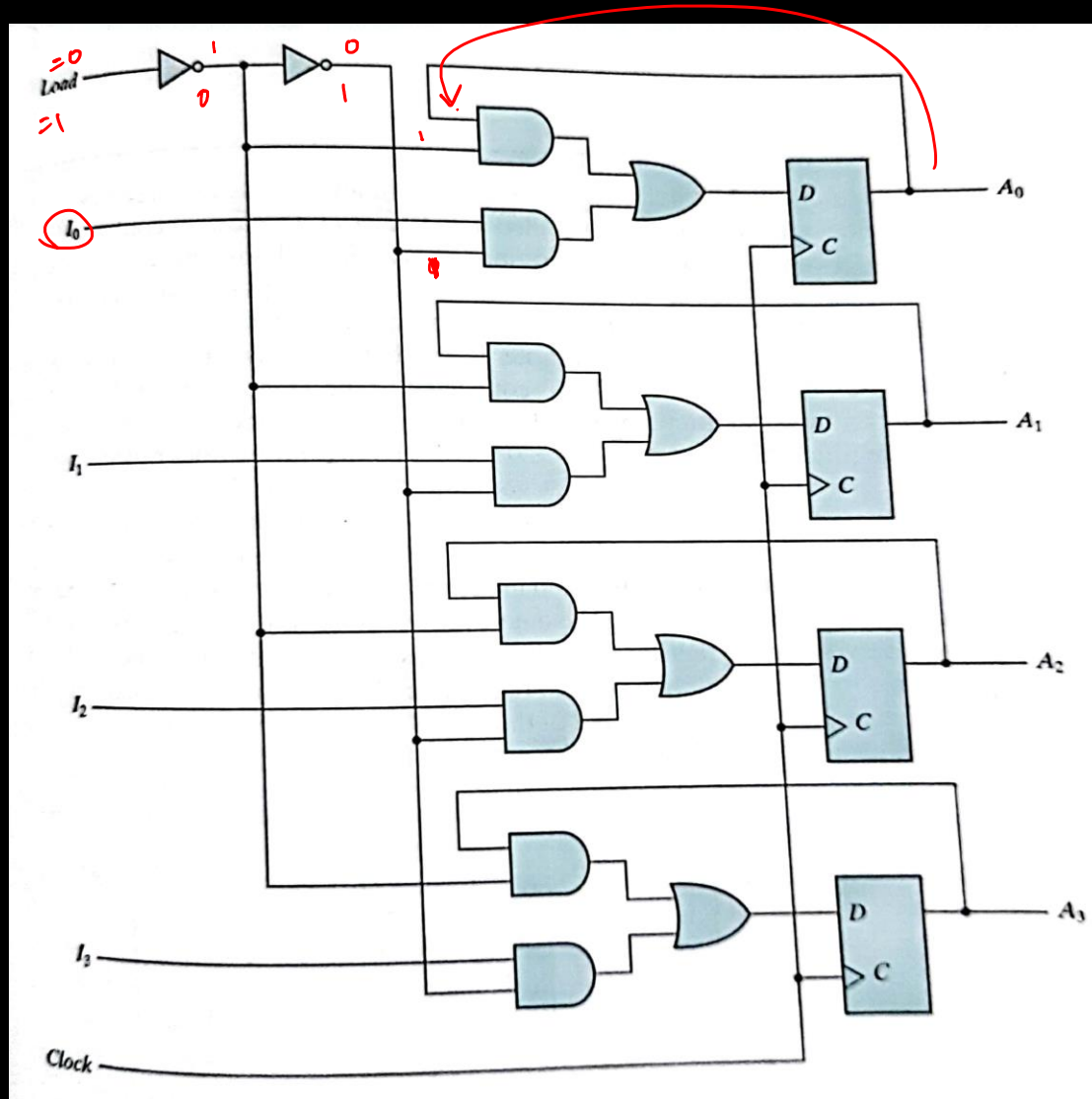Controlling the operation of register by controlling the inputs is better than controlling the clock



**Load = 1** means data at the four ext. i/p transferred to register with the next positive edge of the clock.


**Load = 0** means outputs of the FFs are connected to their respective inputs.

This implies no change condition leaving the output unchanged.

**Shift register:** A register capable of shifting its binary information in one or both directions is called shift registers. It consists of chain of FFs in cascade with output of one connected to i/p of next. All FFs receive common CP which activate shift from one stage to next.

**Serial Mode-** information altered or manipulated one bit at a time

 A **shift register** "shifts" its output once every clock cycle. **SI** is an input that supplies a new bit to shift "into" the register.



After first clock pulse

$$\begin{aligned} Q0(t+1) &= \text{SI} \\ Q1(t+1) &= Q0(t) \\ Q2(t+1) &= Q1(t) \\ Q3(t+1) &= Q2(t) \end{aligned}$$

Here is one example transition.

Present State Q0-Q3	Input SI	Next State Q0-Q3
0110	1	1011

The current Q3 (0 in this example) will be lost on the next cycle.



Applications of shift register – serial data transfer (e.g. USB, UART)

- serial

Parallel





# Serial Transfer

 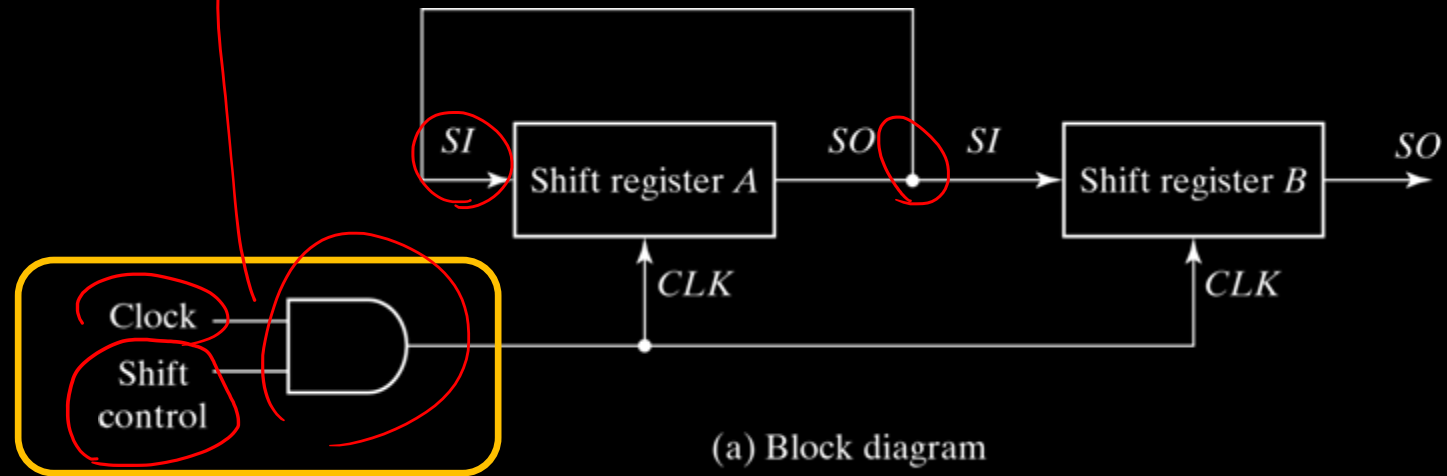



# Serial Transfer

Operation assuming 4-bit shift register

 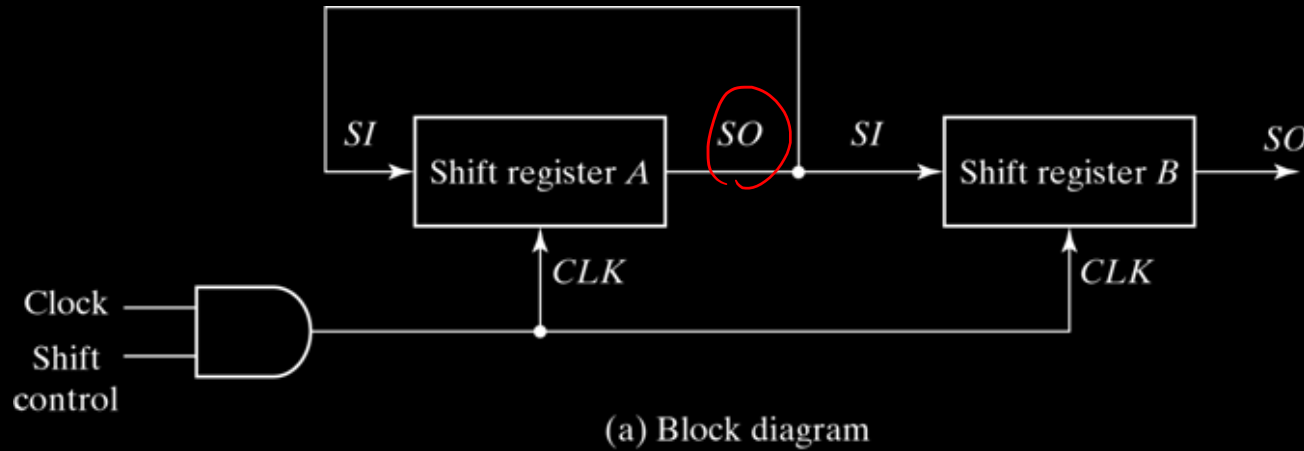

Timing pulse	Shift Register A	Shift Register B
Initial value	1 0 1 1	0 0 1 0
After T <sub>1</sub>	1 1 0 1	1 0 0 1
After T <sub>2</sub>	1 1 1 0	1 1 0 0
After T <sub>3</sub>	0 1 1 1	0 1 1 0
After T <sub>4</sub>	1 0 1 1	1 0 1 1

# Universal Shift register

## Capabilities of Universal shift register

Clear signal to clear the register to 0

Clock input to synchronize

 Shift-right  
Shift-left } Bidirectional shift Register

Parallel load


Parallel out

Control state to leave information in register unchanged


# Universal Shift register

Mode control		Register operation
$S_1$	$S_0$	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load


# Universal Shift register

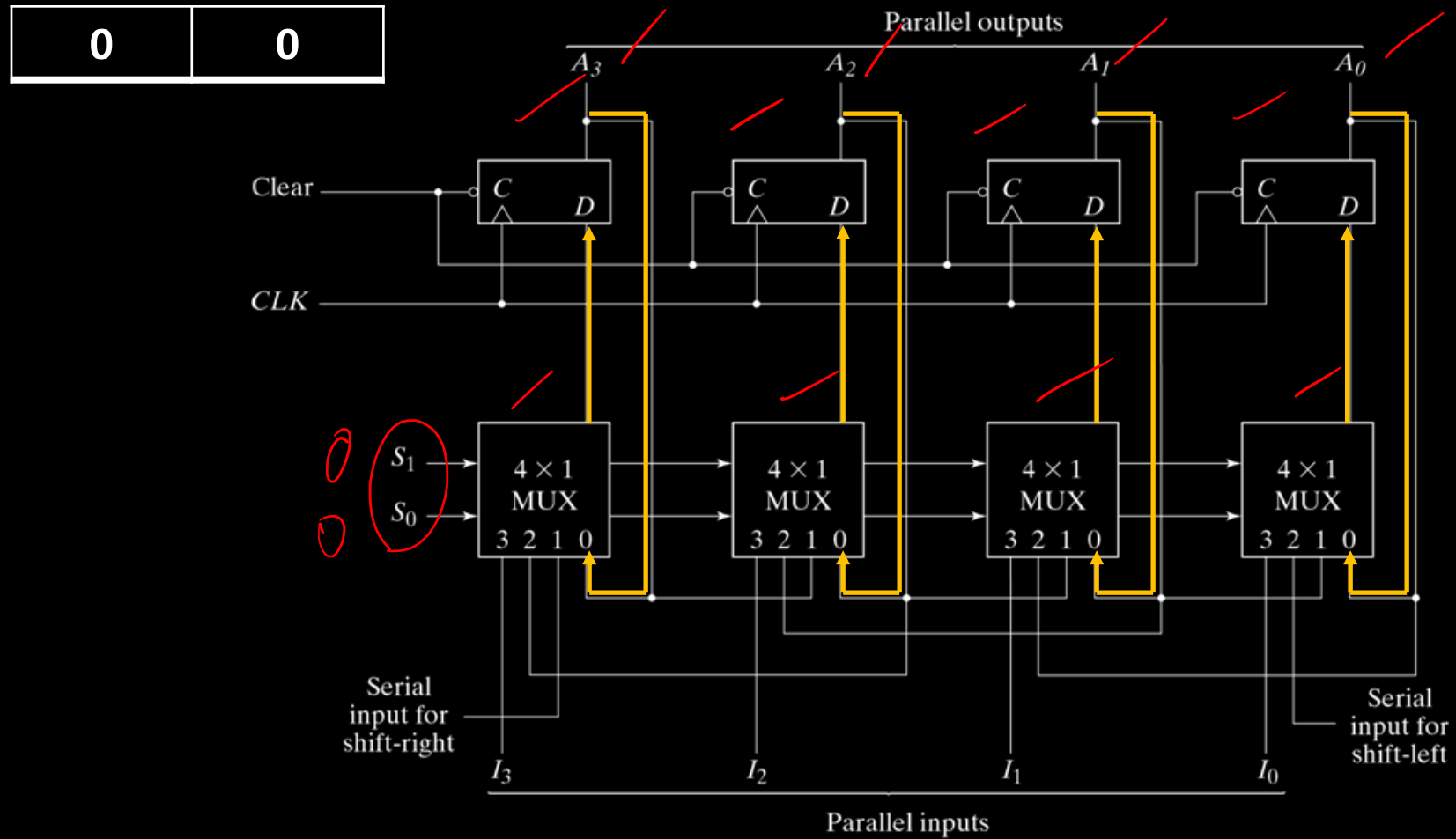


# Universal Shift register

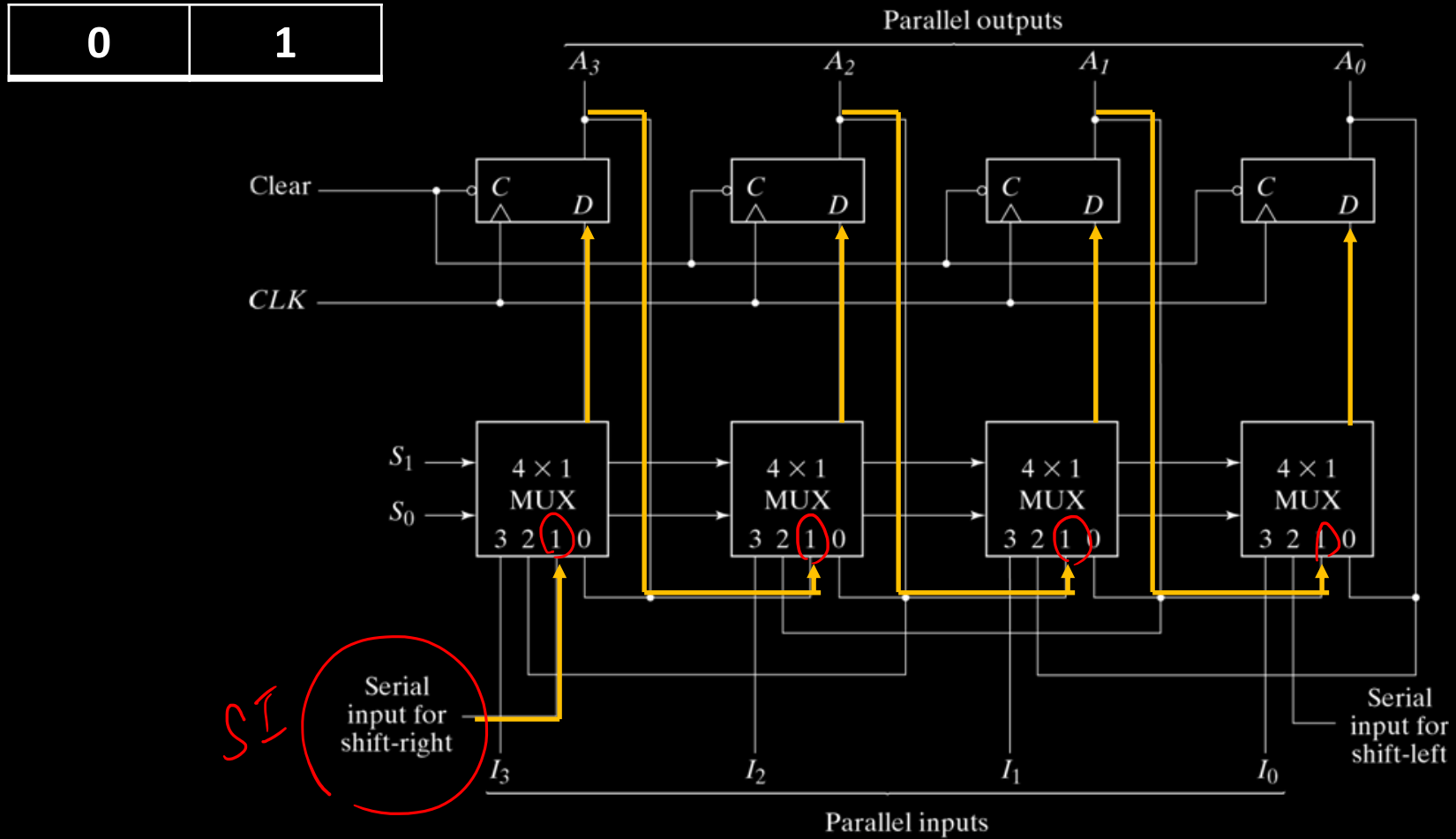

# Universal Shift register

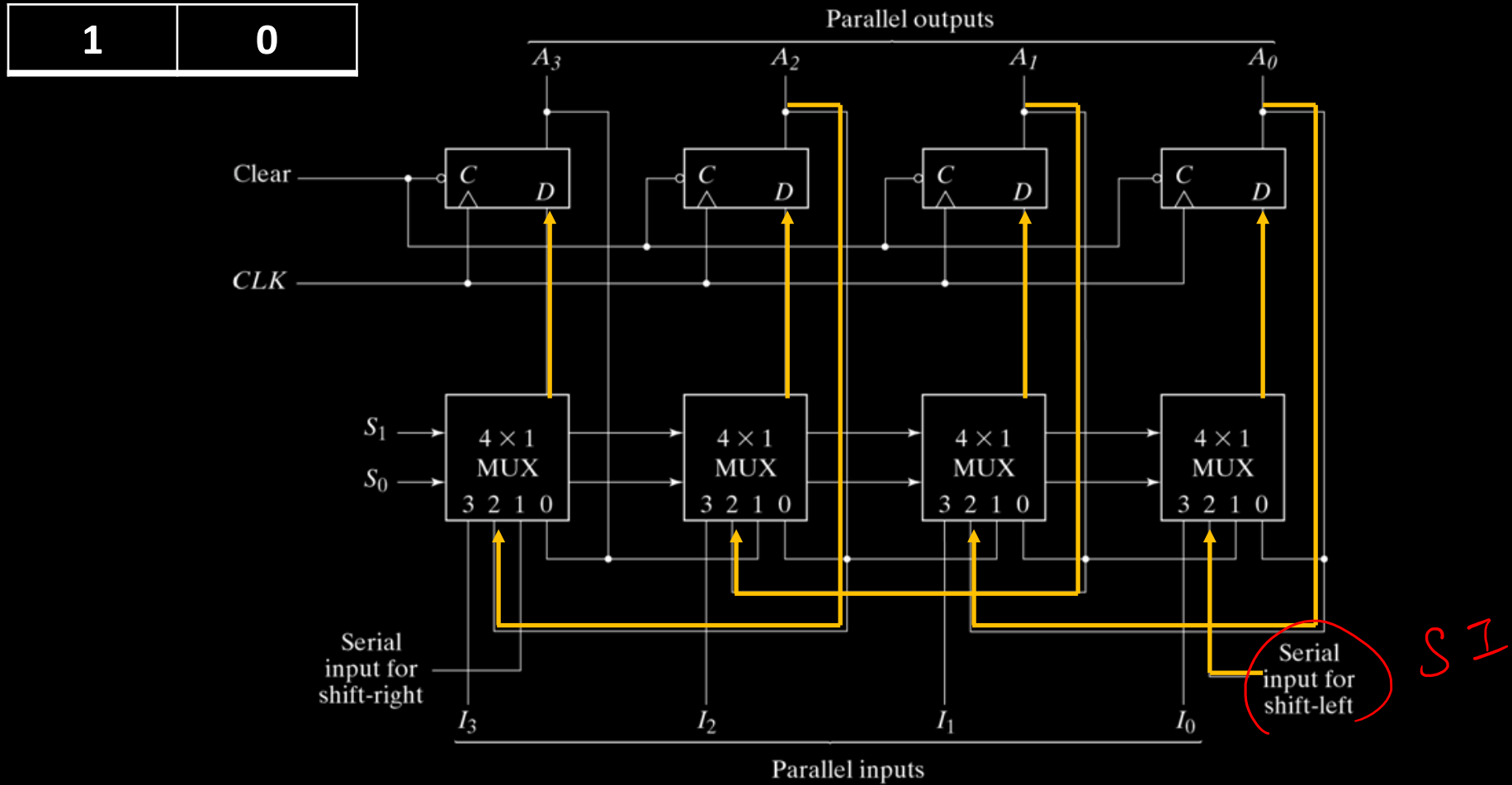

# Universal Shift register

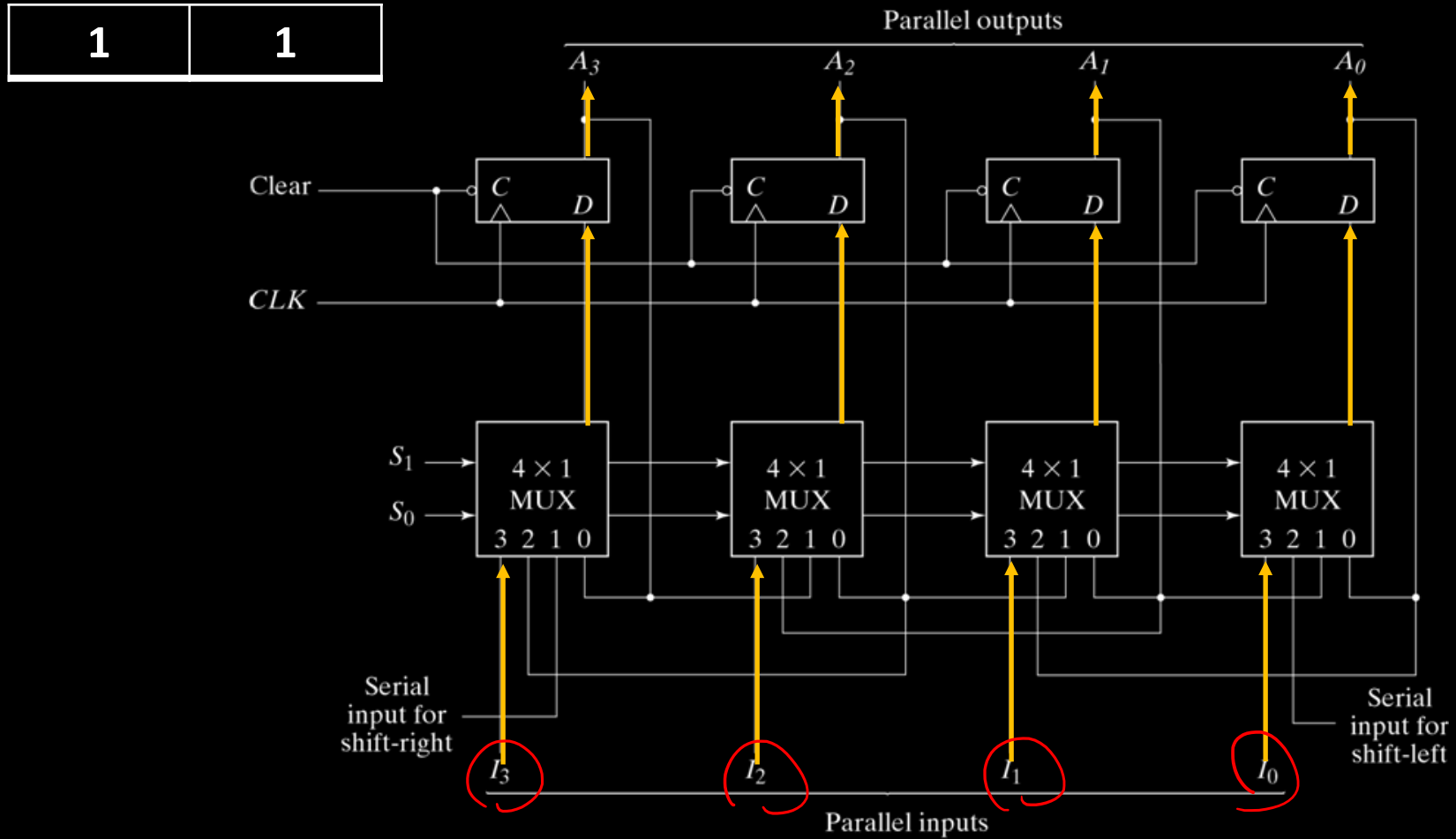


# Serial Adder

bit by bit

X	1	0	0	1
Y	0	1	0	1
t	1	1	1	0



# Serial Adder

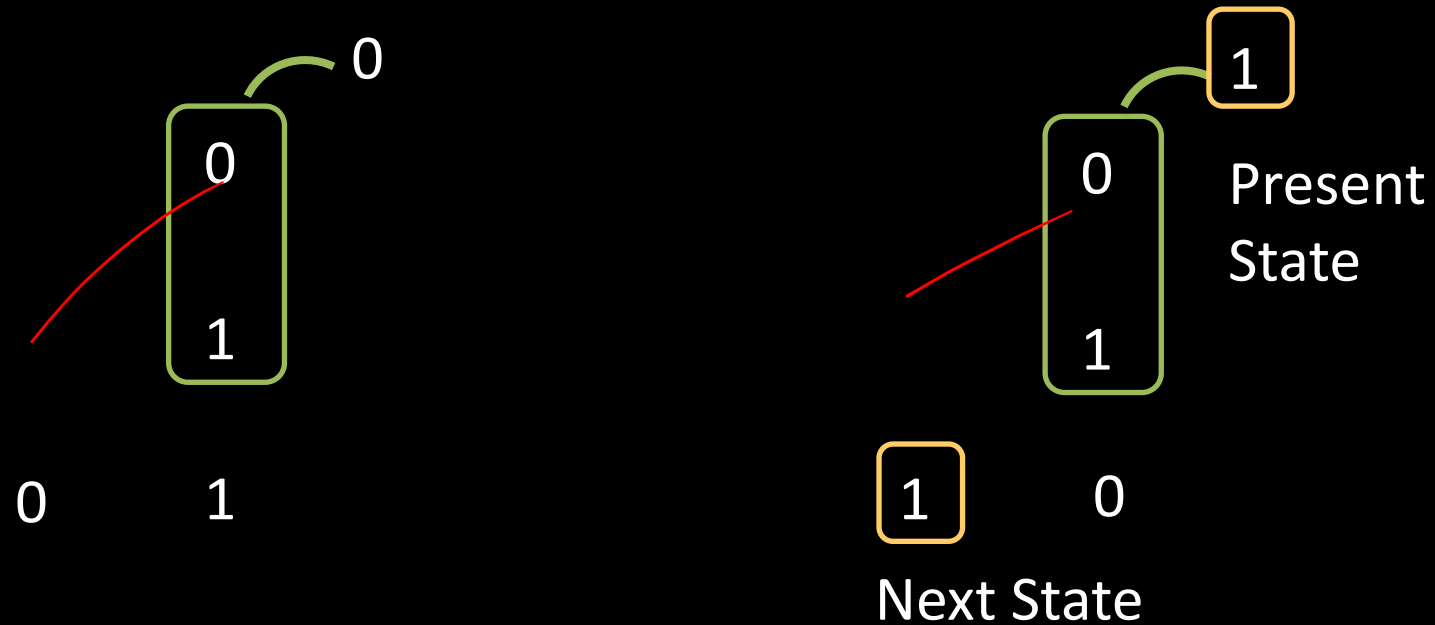

Define two states S0 and S1

S0 indicates carry = 0

S1 indicates carry = 1



# Serial Adder

Define two states S0 and S1

S0 indicates carry = 0

S1 indicates carry = 1

X and Y indicates inputs, Sum is output

  

# Serial Adder

$S_0 \rightarrow 0$   
 $S_1 \rightarrow 1$

Present State				Next State		Out
	$Q_A$	X	Y		$Q_{A(t+1)}$	Sum
S0	0	0	0	S0	0	0
S0	0	0	1	S0	0	1
S0	0	1	0	S0	0	1
S0	0	1	1	S1	1	0
S1	1	0	0	S0	0	1
S1	1	0	1	S1	1	0
S1	1	1	0	S1	1	0
S1	1	1	1	S1	1	1


carry

carry expression of full adder

$$Q_A(t+1) = Q_A X + XY + Q_A Y$$

$$\text{Sum} = Q_A \oplus X \oplus Y$$

# Serial Adder

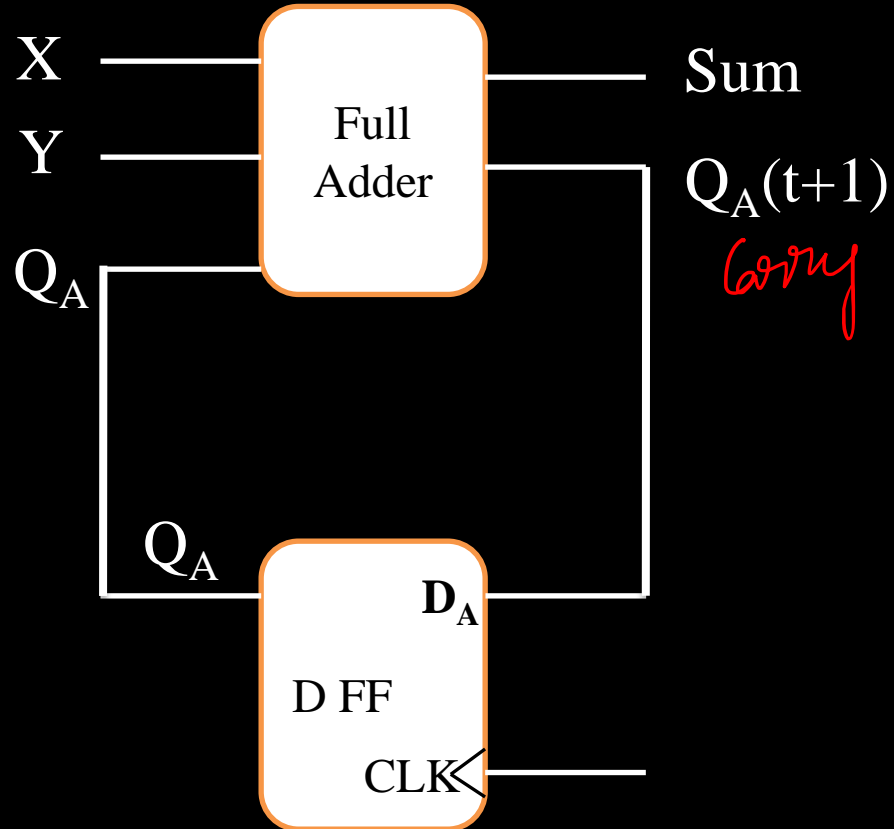

$$Q_A(t+1) = Q_A X + XY + Q_A Y$$


$$\text{Sum} = Q_A \oplus X \oplus Y$$

How to control X and Y ?

# Serial Adder


*Shift register*

*Shift register*

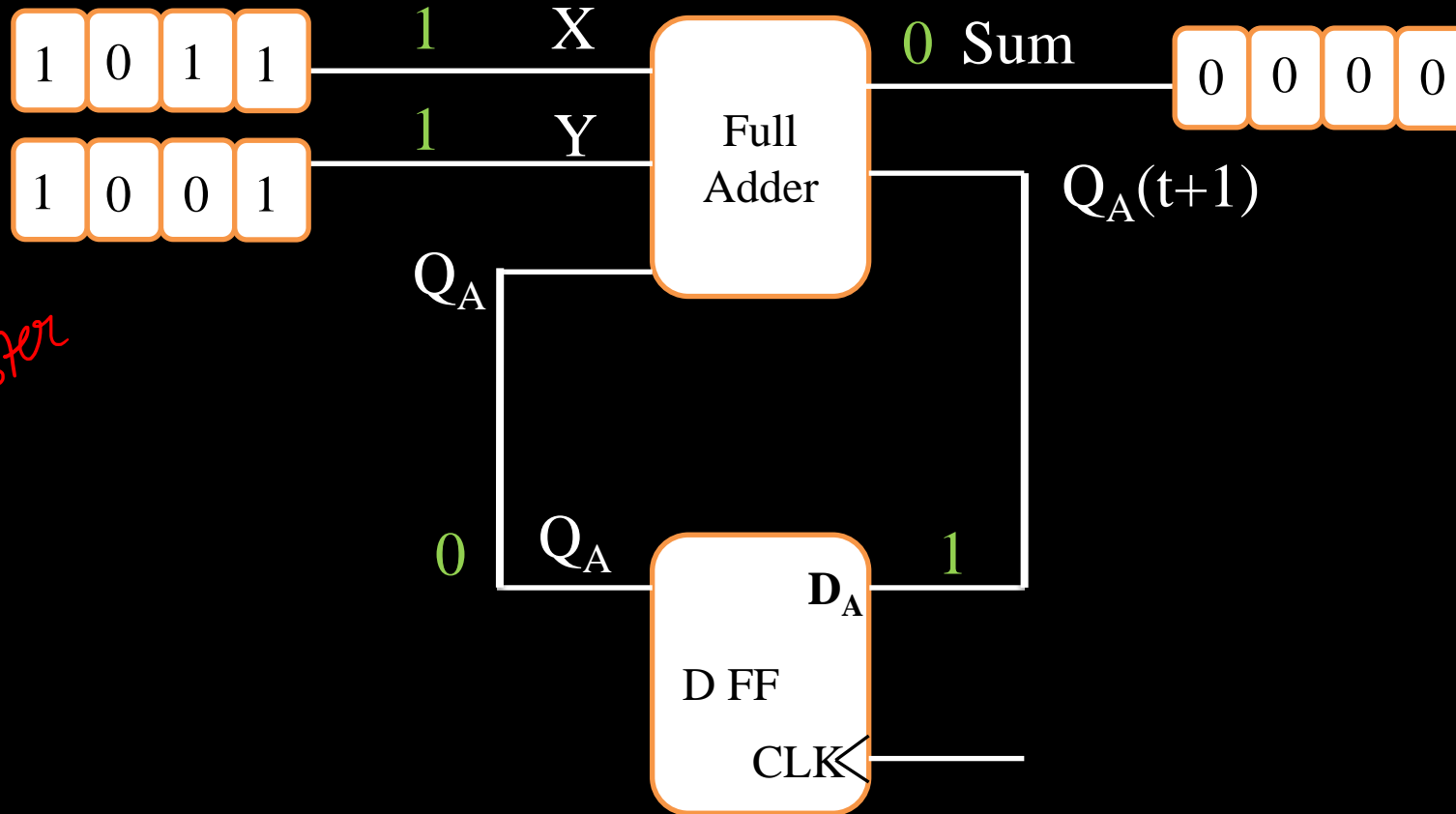


Before any clock pulses


# Serial Adder

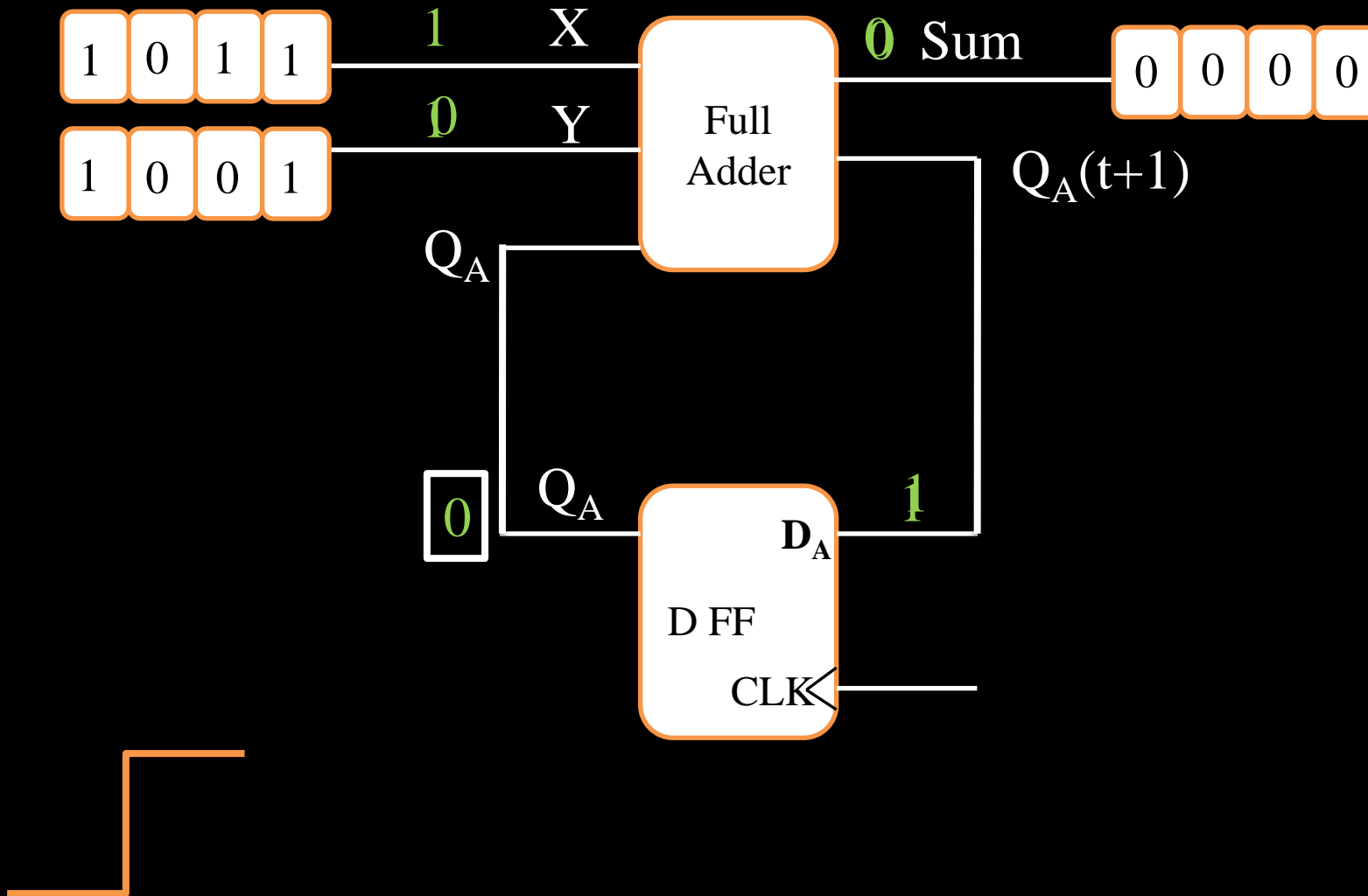

# Serial Adder

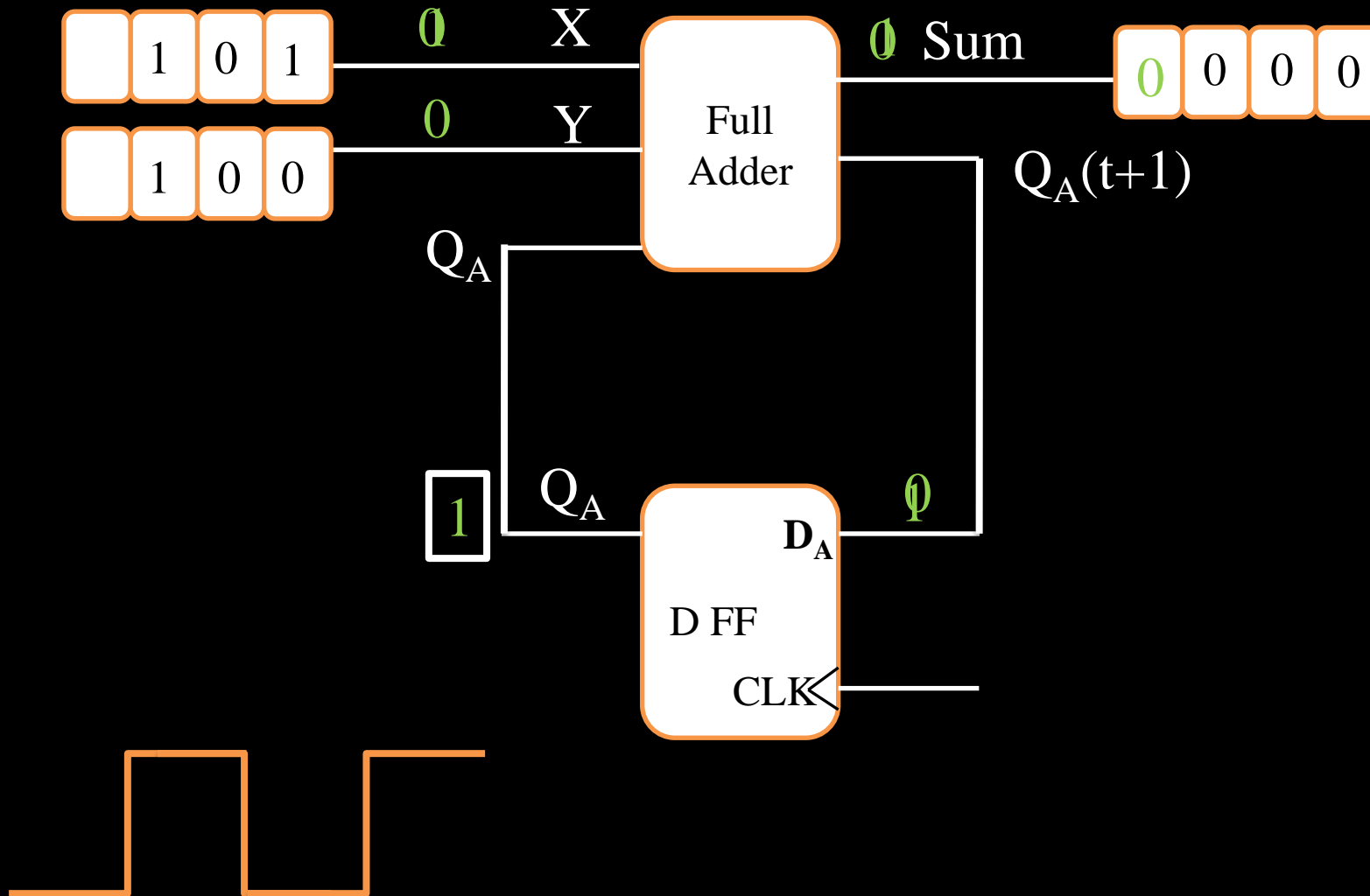


# Serial Adder

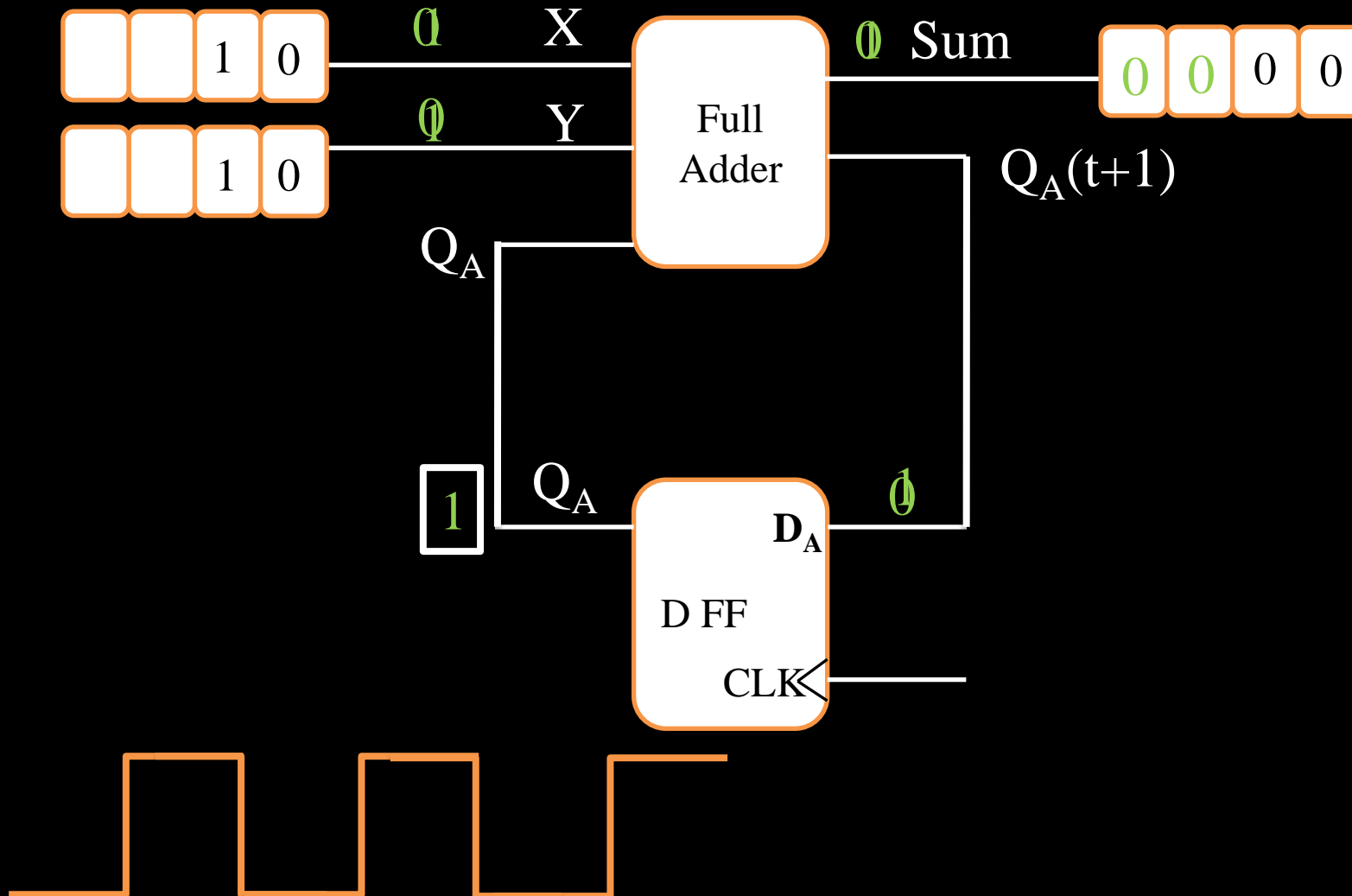



# Serial Adder

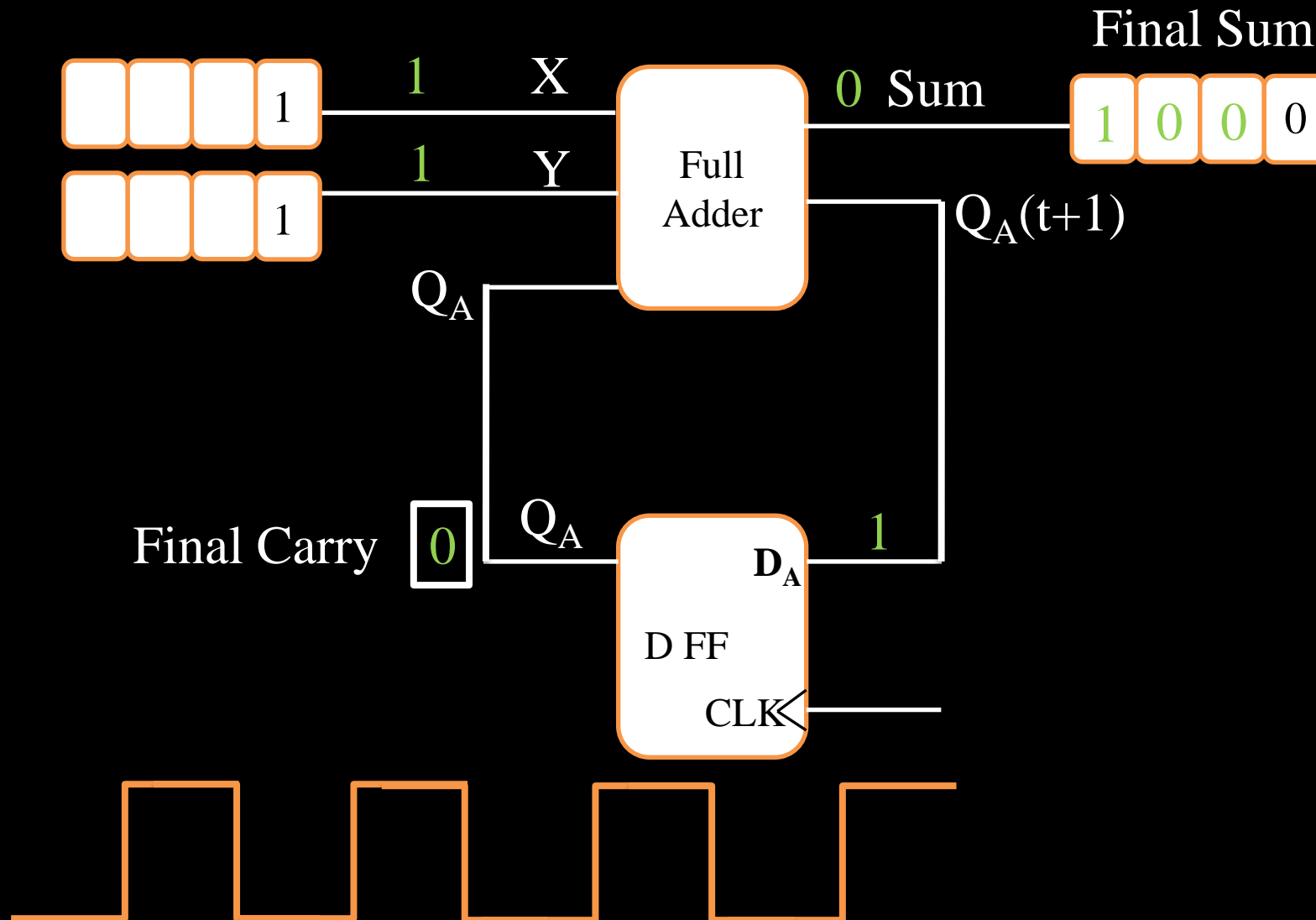

# Serial Adder


A 1-bit full adder is sufficient for n-bit addition

N-clock cycles for N-bit addition

Complex control circuitry

More memory elements required

# Serial Adder

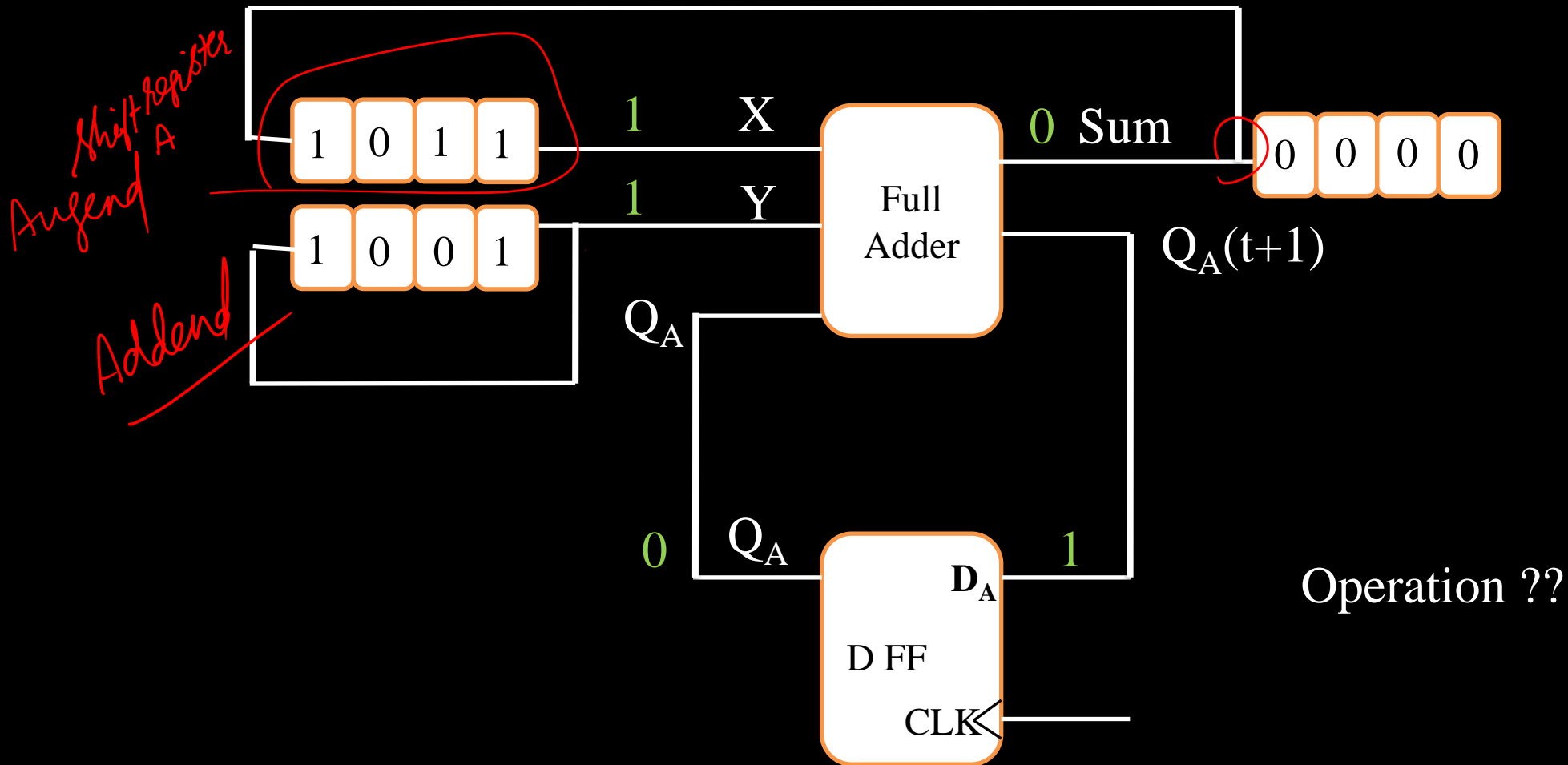

Shift registers will have additional control signals like load, shift control