



Birla Institute of Technology & Science, Pilani
Hyderabad Campus

Innovate

achieve

lead



CS/ECE/EEE/INSTR F215:Digital Design

Lecture 32: ASM
Sat, 27 Nov 2021

BITS Pilani

Hyderabad Campus

Dr. R. N. Ponnalagu, EEE

*Sometimes we are tested,
Not to expose our weakness,
But to discover our strengths.*


- Flowchart developed to design Digital Hardware Algorithms is **Algorithmic State Machines (ASM) chart**

ASM CHART


composed of three basic elements

- ☐ **The State box**
- ☐ **The decision box**
- ☐ **The conditional box**

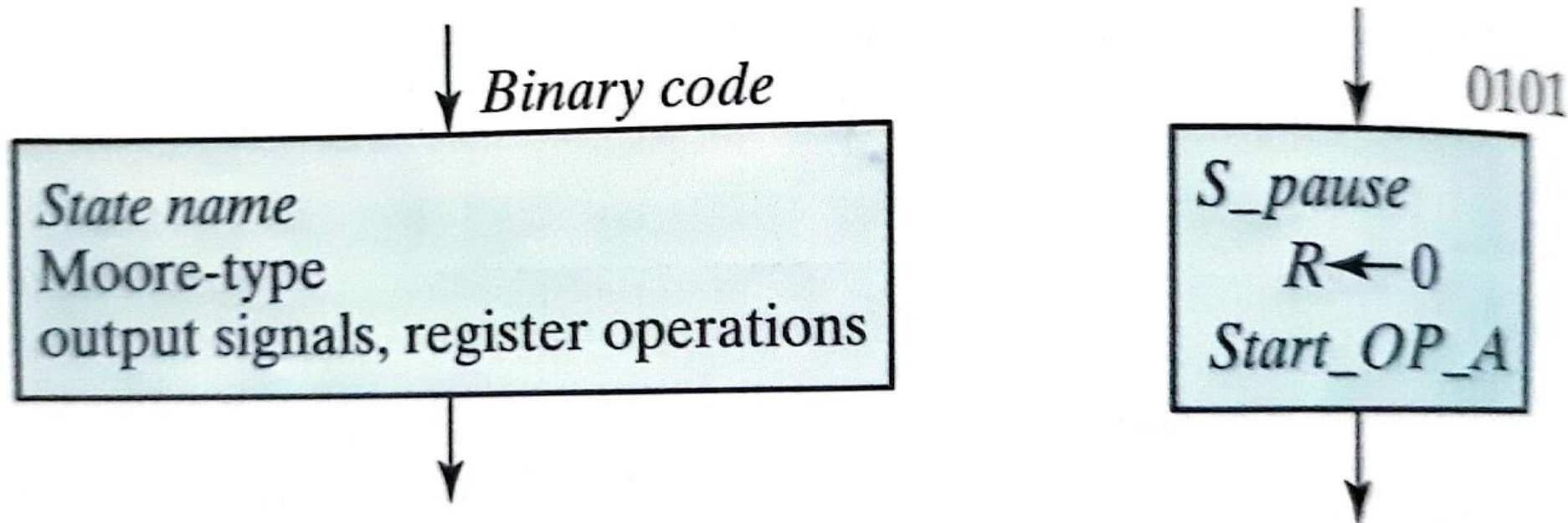- A state is indicated by the **state box** (Rectangle in shape) within which are written
i) register operations that occur when state transitions to next state are written
and/or ii) the names of the output signal that the control generates while being in
the present state.
- State is given a symbolic name (Upper left corner of the box), binary code assigned
to state (upper right)




 - **Decision box (diamond shaped)** indicates the effect of an input on the control subsystem
- **Condition to be tested is written inside the box**
- **One exit path is taken if the condition is true (label 1) and another if false (label 0)**





- **State box and decision box are similar to those used in conventional flowchart**

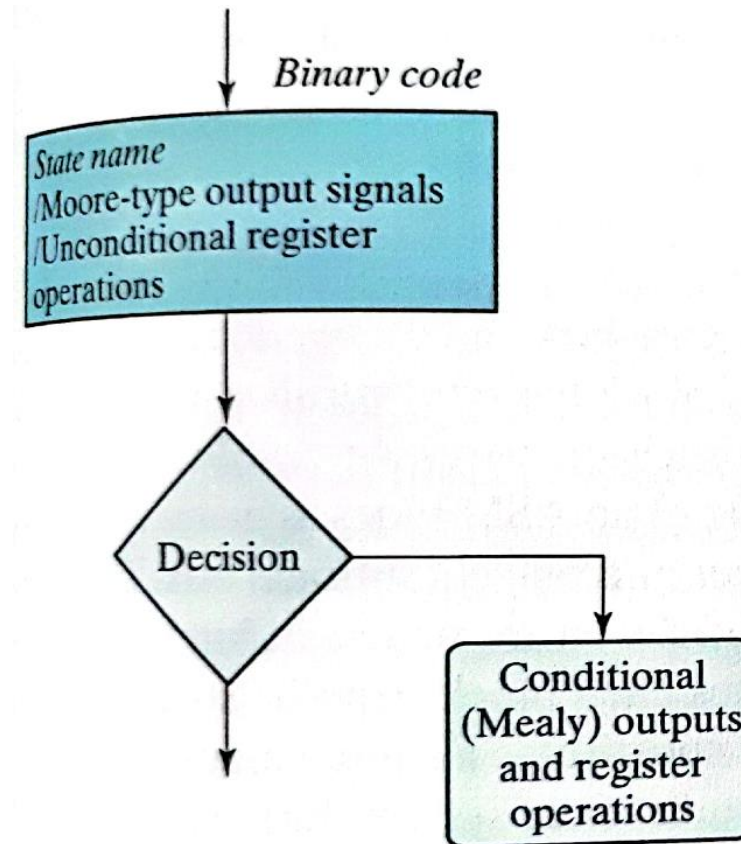- **The conditional box (Shape: rounded corners) is unique to ASM chart**
- **Input path to conditional box comes from one of exit paths of a decision box**
- **The outputs listed inside a conditional box are generated during a given state and the register operations are associated with a transition from the state**




ASM Chart

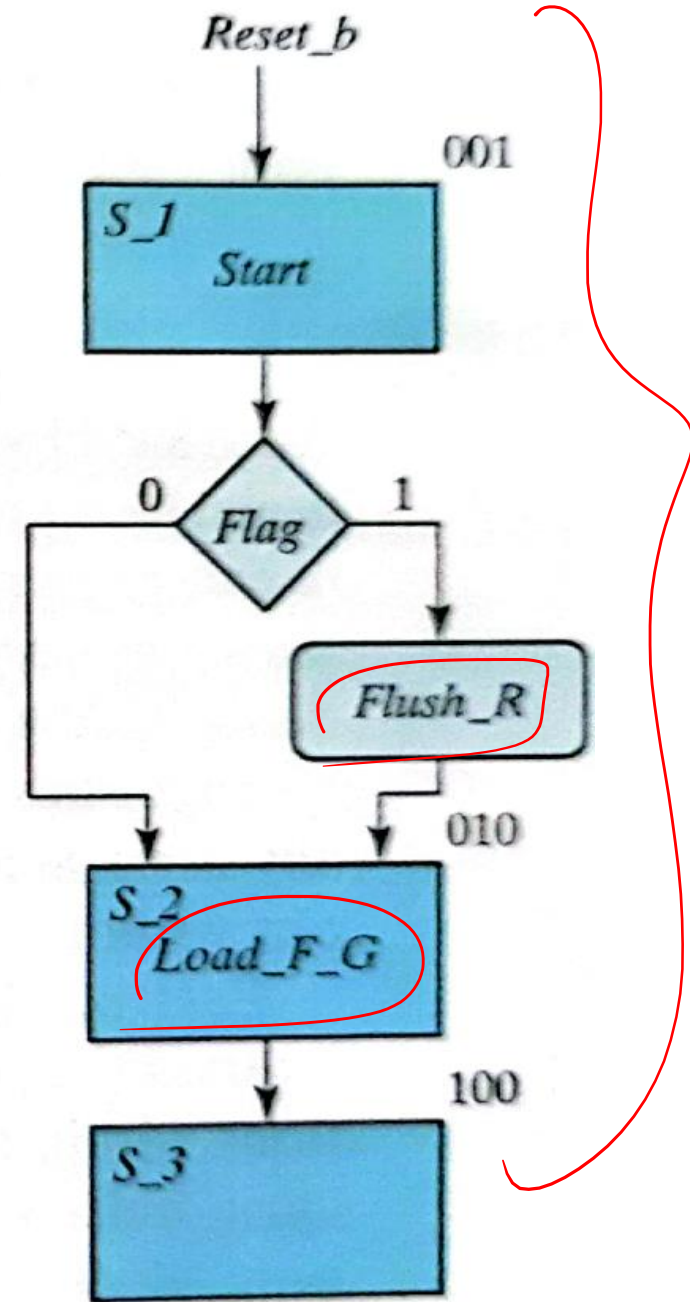 




Control signals

ASM Block in ASM Chart

- A structure consisting of one state box and all the decision and conditional boxes connected to its exit path.
- An ASM block has one entrance and any number of exit paths represented by the structure of the decision boxes
- ASM Chart may have one or more interconnected blocks.
- Each block in the ASM chart describes the state of the system during one clock pulse. (interval between two successive active edges of clock)
- The operations within the state and conditional boxes are executed with a common clock pulse while the system transits from one state to next.
- Same clock pulse transfers system controller to next states.
- ASM chart is very similar to state diagram.

 

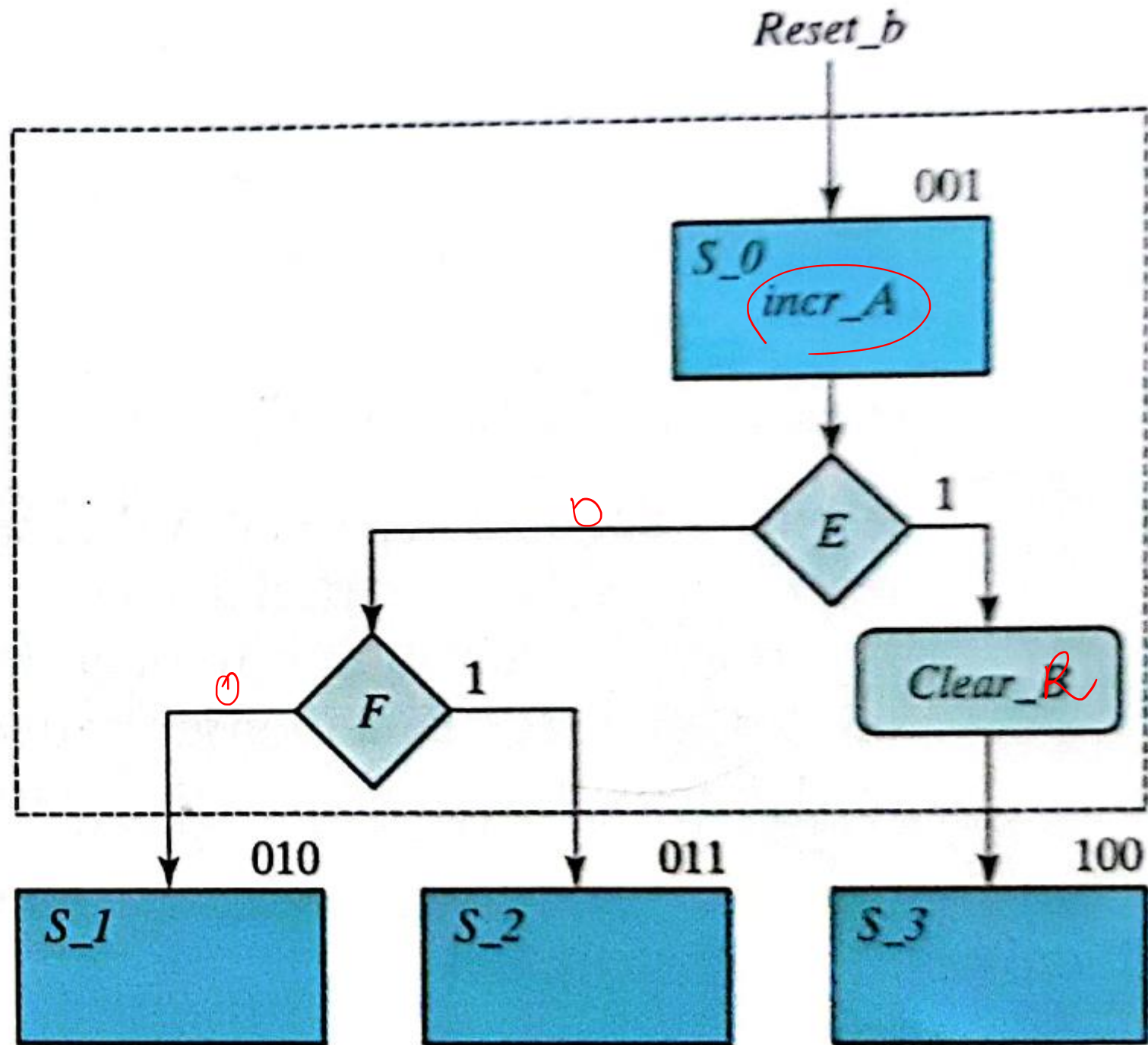

  


➤ Each **state block** is equivalent to a state in a sequential circuit.

➤ **Decision box** is equivalent to the binary information written along the directed lines that connects two states in a state diagram

➤ ASM chart can be easily converted to state diagram and then proceed with the design

➤ The unconditional and conditional operations that must be performed in the data path unit are not indicated in the state diagram of the controller

- In a digital system clock pulses are applied not only to registers of the data path but also to all the FFs in the state machine implementing control unit.
- Inputs are also synchronized to clock and change state in response to an edge transition (synchronous sequential circuit)
- Major difference between a conventional flowchart and an ASM chart is interpreting the timing relations among the various operations
- In conventional flowchart the listed operations follow one after the other in a sequence. No concept of timing and synchronization.
- In contrast, ASM chart consider the entire block as one unit.
- All operations within a block must occur in synchronism during clock edge transition.


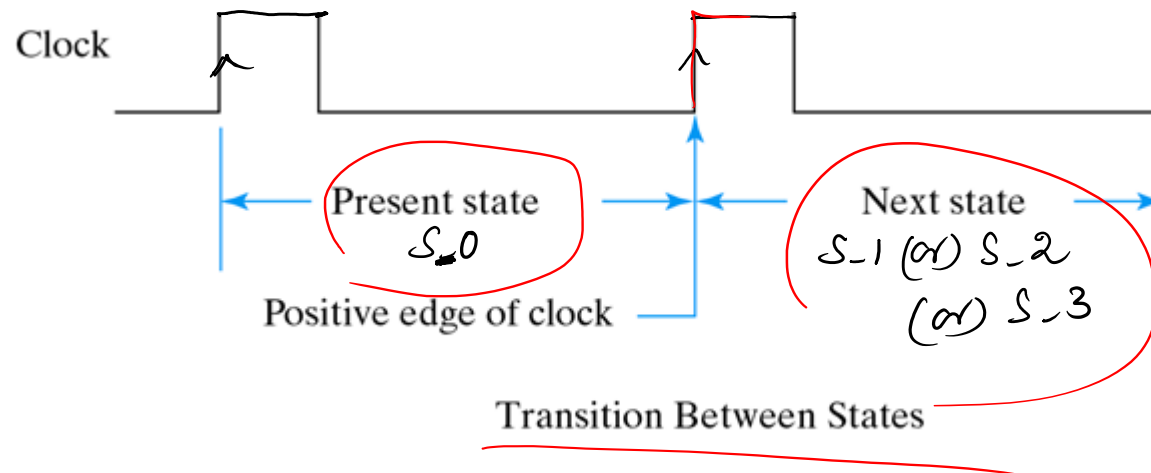


During transition

A is incremented, If $E = 1$, R is cleared

Depending on values of E and F control transferred to states S_1 or S_2 or S_3

  
Draw an ASM chart for a synchronous state machine that is to monitor input x and assert output y after three consecutive 1s are received and remain asserted until a 0 is received.




Example

- Design a Digital system having two FFs **E and F**, one 4-bit binary counter **A** (individual FFs : ~~A₄A₃A₂A₁~~).
A₃ A₂ A₁ A₀
- Initial state is the reset state: **S_idle** (state reached by application of reset_b)
- A Start signal initiates the operation by clearing counter A and flip-flop F.
- Counter incremented by one starting from next clock pulse, continues to increment until operations are such that it stops.
- Counter bits A₂ and A₃ determine sequence of operations
 - ✓ If $A_2 = 0$, E is cleared to 0 and count continues
 - ✓ If $A_2 = 1$, E set to 1; then if $A_3 = 0$, count continues,
 - ✓ but if $A_3 = 1$, F is set to 1 on next clock pulse and system stops counting.
- If Start = 0 system remains in initial state, but if Start = 1 cycle repeats.

Block diagram of the design

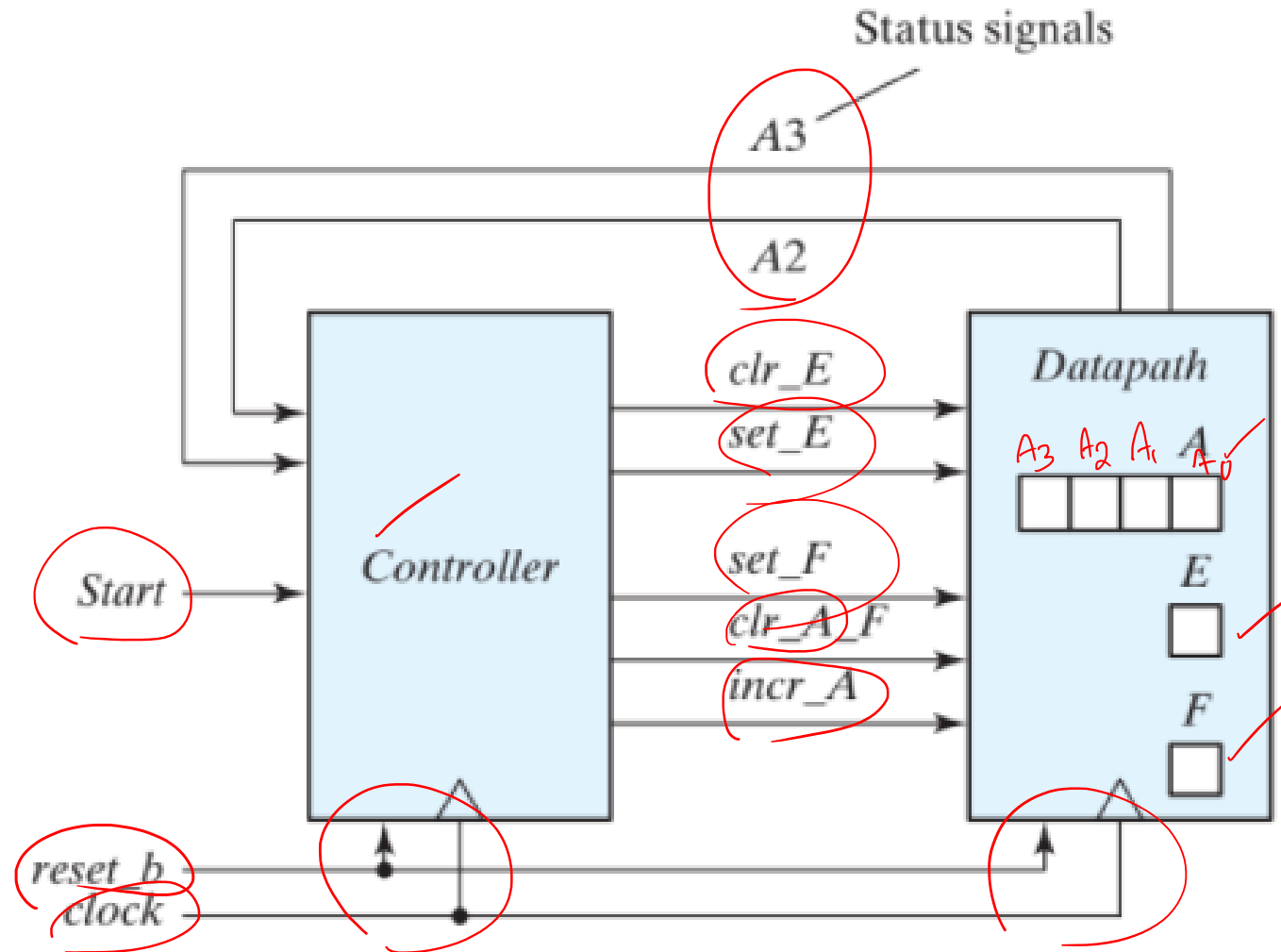

- When no operations the system is in initial state S_idle awaiting for $Start$ signal
- When input $Start = 1$, state changes to S_1 and the counter A and flip-flop F are cleared. The register operations occur unconditionally (Moore type).
- Register A is incremented at every clock edge while machine is state S_1 .
- In state S_1 when the counter is incremented with every clock pulse and at the same time, one of three operations occur during clock transition either
 - ✓ E is cleared and control stays in state S_1 ($A_2 = 0$); or
 - ✓ E is set and control stays in state S_1 ($A_2A_3 = 10$); or
 - ✓ E is set and control goes to state S_2 ($A_2A_3 = 11$).
- Hence block with state S_1 has two decision and two conditional boxes
- In state S_2 , a Moore type control signal is asserted to set flipflop F and state changes to S_idle .

 

Sequence of operations

A2
0 0 1 1
0 0 0 0
0 1 0 1

Counter

Flipflops

Conditions

State

A3 A2 A1 A0

E

F

A2=0, A3=0

S_1

0 0 0 0 ✓

1 0 ✓

0 0 0 1 ✓

0 0

0 0 1 0 ✓

0 0

0 0 1 1 ✓

0 0

0 1 0 0

0 0

A2=1, A3=0

0 1 0 1

1 0

0 1 1 0

1 0

0 1 1 1

1 0

1 0 0 0

1 0

A2=1, A3=0

1 0 0 1

0 0

1 0 1 0

0 0

1 0 1 1

0 0

1 1 0 0

0 0

A2=1, A3=1

1 1 0 1

1 0

S_2

1 1 0 1

1 0

S_idle

TABLE 6.3

Sequence of Operations for Design Example

Counter				Flip-Flops		Conditions	State
A_3	A_2	A_1	A_0	E	F		
0	0	0	0	1	0	$A_2 = 0, A_3 = 0$	S_1
0	0	0	1	0	0		
0	0	1	0	0	0		
0	0	1	1	0	0		
0	1	0	0	0	0	$A_2 = 1, A_3 = 0$	
0	1	0	1	1	0		
0	1	1	0	1	0		
0	1	1	1	1	0		
1	0	0	0	1	0	$A_2 = 0, A_3 = 1$	
1	0	0	1	0	0		
1	0	1	0	0	0		
1	0	1	1	0	0		
1	1	0	0	0	0	$A_2 = 1, A_3 = 1$	
1	1	0	1	1	0		S_2
1	1	0	1	1	1		S_{idle}