



Birla Institute of Technology & Science, Pilani
Hyderabad Campus

Innovate

achieve

lead



BITS Pilani
Hyderabad Campus


CS/ECE/EEE/INSTR F215:Digital Design

Lecture 27: *Design of clocked sequential circuits_2*
Sat, 13 Nov 2021

Dr. R. N. Ponnalagu, EEE

*If you have choice
choose the best,
If you have No choice
do the best*

➤ To detect a pattern 1001

 

Present State	Input	Next State	Output
A	0	A	0
A	1	B	0
B	0	C	0
B	1	B	0
C	0	D	0
C	1	B	0
D	0	A	0
D	1	B	1

Present State		Input X	Next State		Output Z
Q ₁	Q ₀		Q ₁	Q ₀	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	0	1	1

Present State		Input X	Next State		Flip-flop Inputs				Output Z
Q_1	Q_0		Q_1	Q_0	J_1	K_1	J_0	K_0	
0	0	0	0	0	0	x	0	x	0
0	0	1	0	1	0	x	1	x	0
0	1	0	1	0	1	x	x	1	0
0	1	1	0	1	0	x	x	0	0
1	0	0	1	1	x	0	1	x	0
1	0	1	0	1	x	1	1	x	0
1	1	0	0	0	x	1	x	1	0
1	1	1	0	1	x	1	x	0	1


$$J_1 = X'Q_0$$

$$K_1 = X + Q_0$$

$$J_0 = X + Q_1$$

$$K_0 = X'$$

$$Z = Q_1Q_0X$$

 

Building the same circuit with D flip-flops

- What if you want to build the circuit using D flip-flops instead?
- We already have the state table and state assignments, so we can just start from Step 3, finding the flip-flop input values.
- D flip-flops have only one input, so our table only needs two columns for D_1 and D_0 .

Present State		Input X	Next State		Flip-flop Inputs		Output Z
Q_1	Q_0		Q_1	Q_0	D_1	D_0	
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	0	1	0	0
0	1	1	0	1	0	1	0
1	0	0	1	1	1	1	0
1	0	1	0	1	0	1	0
1	1	0	0	0	0	0	0
1	1	1	0	1	0	1	1

Finding equations (Step 4)

- If you use K-maps again, you should find the following equations.


$$D_1 = Q_1 Q_0' X' + Q_1' Q_0 X'$$

$$D_0 = X + Q_1 Q_0'$$

$$Z = Q_1 Q_0 X$$


Present State $Q_1 \quad Q_0$		Input X	Next State $Q_1 \quad Q_0$		Flip-flop Inputs $D_1 \quad D_0$		Output Z
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	0	1	0	0
0	1	1	0	1	0	1	0
1	0	0	1	1	1	1	0
1	0	1	0	1	0	1	0
1	1	0	0	0	0	0	0
1	1	1	0	1	0	1	1

Building the circuit (Step 5)

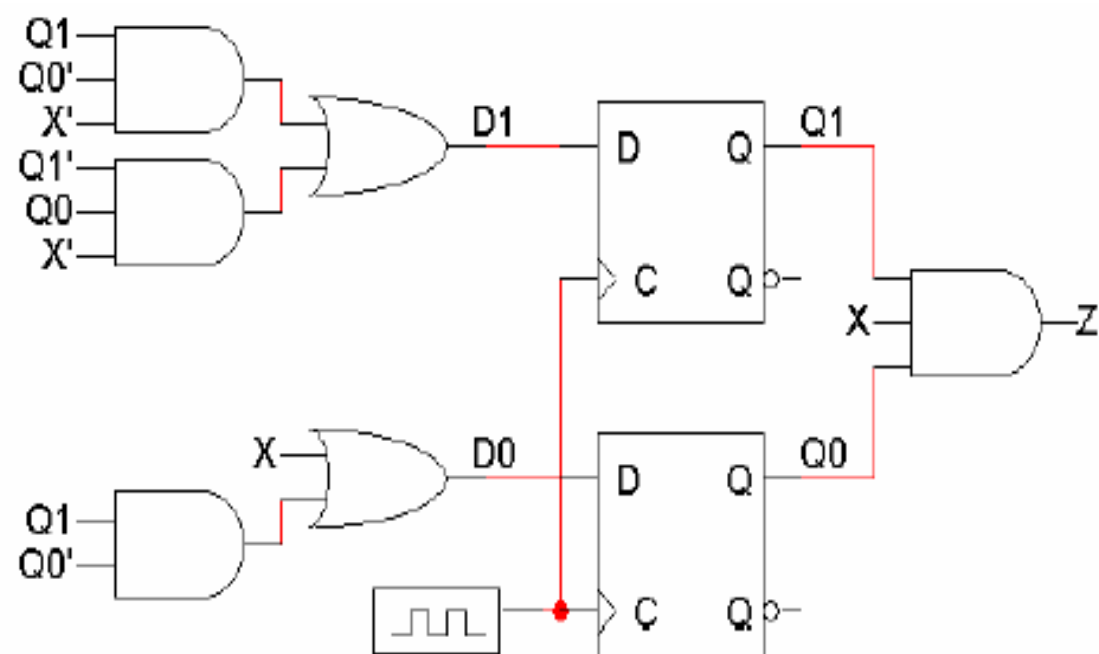


Flip-flop comparison

 - JK flip-flops are good because there are many don't care values in the flip-flop inputs, which can lead to a simpler circuit.



 
- D flip-flops have the advantage that you don't have to set up flip-flop inputs at all, since $Q(t+1) = D$. However, the D input equations are usually more complex than JK input equations.



- In practice, D flip-flops are used more often.
 - There is only one input for each flip-flop, not two.
 - There are no excitation tables to worry about.
 - D flip-flops themselves are simpler to implement than JK flip-flops.

DESIGN WITH UNUSED STATES

 • Design the circuit using ~~D~~ Flip Flops



P.S	I/P	N.S	O/P	ff	I/P	T _A	T _B	T _C
A	B	C	Y					
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0

PS			X	NS			T D_a	T D_b	T D_c	Y
A	B	C		A	B	C				
0	0	0	0	0	1	1				0
0	0	0	1	1	0	0				1
0	0	1	0	0	0	1				0
0	0	1	1	1	0	0				1
0	1	0	0	0	1	0				0
0	1	0	1	0	0	0				1
0	1	1	0	0	0	1				0
0	1	1	1	0	1	0				1
1	0	0	0	0	1	0				0
1	0	0	1	0	1	1				0

PS			X	NS			D _A	D _B	D _C	Y
A	B	C		A	B	C				
0	0	0	0	0	1	1	0	1	1	0
0	0	0	1	1	0	0	1	0	0	1
0	0	1	0	0	0	1	0	0	1	0
0	0	1	1	1	0	0	1	0	0	1
0	1	0	0	0	1	0	0	1	0	0
0	1	0	1	0	0	0	0	0	0	1
0	1	1	0	0	0	1	0	0	1	0
0	1	1	1	0	1	0	0	1	0	1
1	0	0	0	0	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1	1	0

$$T_A = A + \bar{B}X$$


$$T_B = A + \bar{B}CX$$

AB \ CX				
	00	01	11	10
00	0	1	1	0
01	0	0	0	0
11	X	X	X	X
10	0	0	X	X

AB \ CX				
	00	01	11	10
00	1			
01	1		1	
11	X	X	X	X
10	1	1	X	X

AB \ CX				
	00	01	11	10
00	1			1
01				1
11	X	X	X	X
10		1	X	X

AB \ CX				
	00	01	11	10
00		1	1	
01		1	1	
11	X	X	X	X
10			X	X

 


Answer:

$$\mathbf{D_a = A'B'x}$$

$$\mathbf{D_b = C'x' + A + BCx}$$

$$\mathbf{D_c = A'B'x' + Cx' + Ax}$$

$$\mathbf{Y = A'x}$$

 

Answer:

$$D_a = A'B'x$$

$$D_b = C'x' + A + BCx$$

$$D_c = A'B'x' + Cx' + Ax$$

$$Y = A'x$$

The circuit is self correcting

PS			X	NS			T _a	T _b	T _c	Y
A	B	C		A	B	C				
0	0	0	0	0	1	1				0
0	0	0	1	1	0	0				1
0	0	1	0	0	0	1				0
0	0	1	1	1	0	0				1
0	1	0	0	0	1	0				0
0	1	0	1	0	0	0				1
0	1	1	0	0	0	1				0
0	1	1	1	0	1	0				1
1	0	0	0	0	1	0				0
1	0	0	1	0	1	1				0

Answer:

$$T_a = A + B'x$$

$$T_b = B'C'x' + A + BCx' + BC'X$$

$$T_c = A'B'C'x' + Cx + Ax$$

$$Y = A'x$$

000
001
010
011
100 } used states

N.S
A B C
0 1 0
0 1 0 } unused states

101
110
111 }

Self correcting

A B C x
1 0 1 0
1 0 1 1
1 1 0 0
1 1 0 1
1 1 1 0
1 1 1 1

T_A T_B T_C
1 1 0
1 1 1

011
010
011
010

Flip flop Conversions

SR
D
JK
T

Char. table

SR to JK

J	K	Q_t Q_{t+1}		S R	
		Q_t	Q_{t+1}	S	R
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	1	0
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	0	0
0	1	1	0	1	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	0	1	0	0
1	1	1	0	1	0
1	1	1	1	0	0

Excitation table

J	\bar{Q}_t	\bar{K}_t	\bar{Q}_t	\bar{K}_t
0	0	0	0	0
0	0	0	1	0
0	1	0	0	0
0	1	0	1	0
1	0	0	0	0
1	0	0	1	0
1	1	0	0	0
1	1	0	1	0

$S = J \bar{Q}_t$
 $R = K Q_t$

X	0	1	X
0	0	1	0

$R = K Q_t$

Registers



- Register is an extension of a Flip-flop that can store multiple bits. Register consists of group of flip-flops and some combinational gates. Each FF is capable of storing one bit of information. N-bit register has group of n-FFs capable of storing n-bits of binary information. The logic gates determine how the information is transferred into the register.
- Ex: Used as a Temporary storage in Microprocessors

A basic register

An example: Register constructed using D FFs.

D0-D3 Data inputs; **Q0-Q3** data output.

