



**Birla Institute of Technology & Science, Pilani**  
Hyderabad Campus



# CS/ECE/EEE/INSTR F215:Digital Design

## Lecture 29: *Counters*

*Thu, 18 Nov 2021*

**BITS Pilani**

Hyderabad Campus



**Dr. R. N. Ponnalagu, EEE**

*Desire for success > Fear for Failure  
is the formula for success*

# Counters

- A sequential circuit that goes through **prescribed sequence of states** upon application of input pulses.
- Input pulses may be clock pulses.
- Sequence of states may follow binary sequence or any other sequence of states.
- A counter that follows binary sequence – **Binary Counter**
- An n-bit binary counter has n-FFs and can count in binary from 0 through  $2^n - 1$ .
- Types of counters: Ripple or Asynchronous counters and Synchronous counters

Ring Counter, Johnson Counter – **Other counters**


**Ripple Counter** – Asynchronous Counters

The FF output transition serves as a source for triggering other FFs. No common clock.

**Synchronous Counters**

All FFs receive the common clock pulse, and the change of state is determined from the present state.

# Ripple Counter – Asynchronous Counters

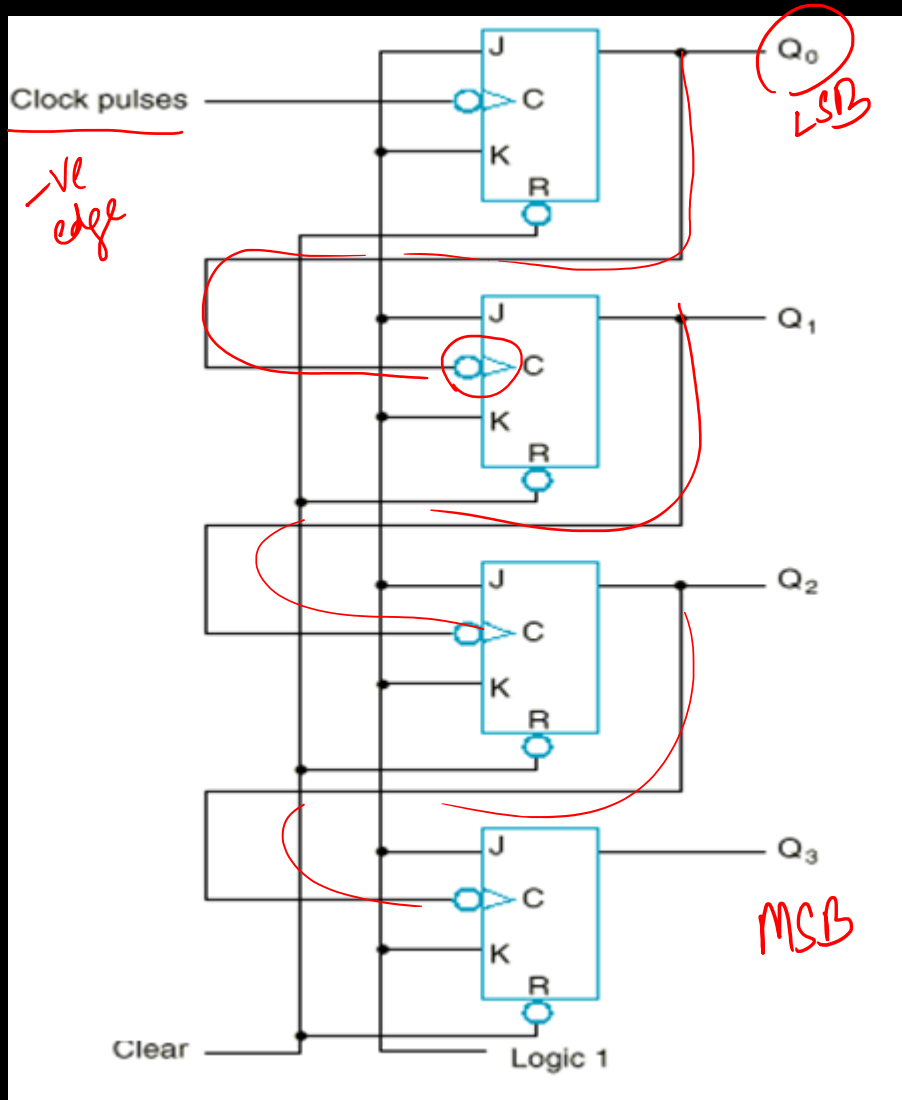

In Asynchronous counter, ext. clock pulse is applied only to the flip flop (LSB).


Instead of the ext. clock pulse, the output of first flip-flop acts as a clock pulse to the next flip flop, whose output is used as a clock to the next in line flip-flop and so on.


- The output of each FF is connected to the Clock input of the next FF in sequence.
- The FF holding the least significant bit receives the incoming clock pulses.
- The J and K inputs of all FFs are connected to a permanent logic 1.

- Operation:
- The least significant bit ( $Q_0$ ) is complemented with each negative-edge clock pulse input.
- Every time that  $Q_0$  goes from 1 to 0,  $Q_1$  is complemented.
- Every time that  $Q_1$  goes from 1 to 0,  $Q_2$  is complemented.
- Every time that  $Q_2$  goes from 1 to 0,  $Q_3$  is complemented, and so on.


Upward Counting Sequence			
$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

# Timing diagram

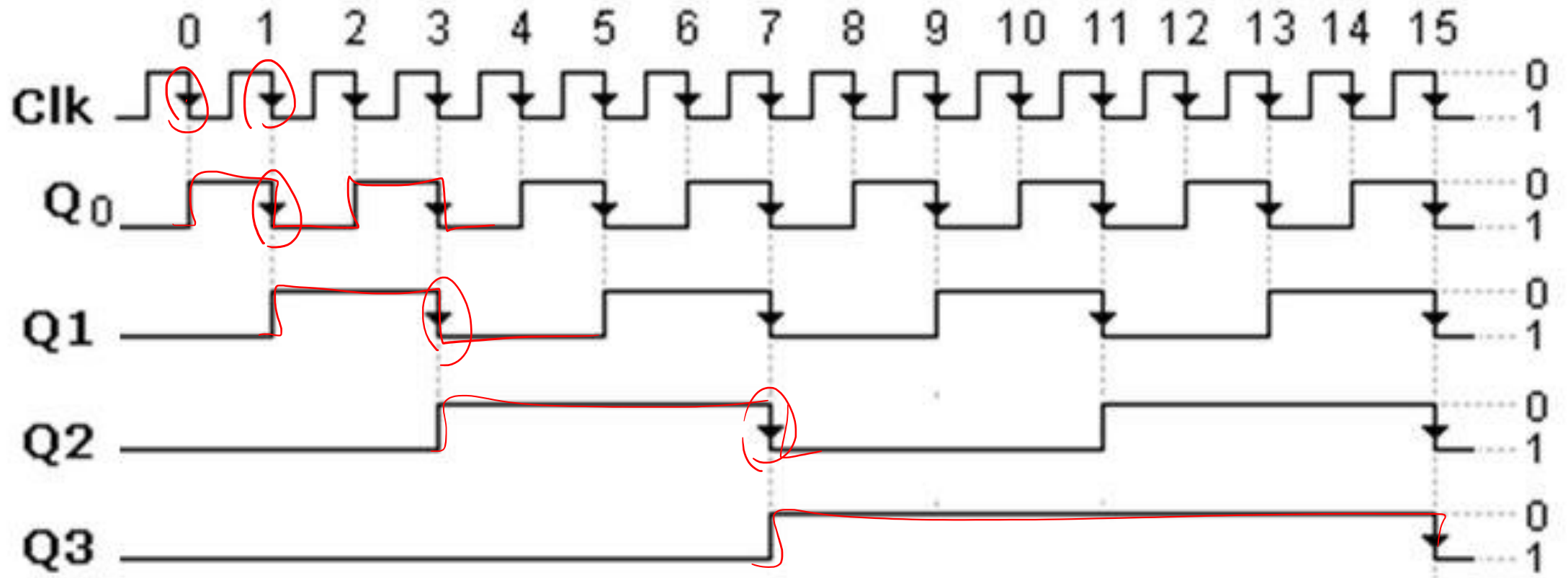

 

(a) With T flip-flops

 

(b) With D flip-flops

# 4-Bit Binary Ripple Counter

# Design a Binary Down Counter

## Approach:

*preset  $\Rightarrow 1111$*

Use direct Set (S) signals (PRESET) instead of direct Reset (R), in order to start at 1111.


Method 1: Change edge-triggering to positive

Method 2: Connect the complement output of each FF to the C (CLOCK) input of the next FF in the sequence



*decade counter*


*10*

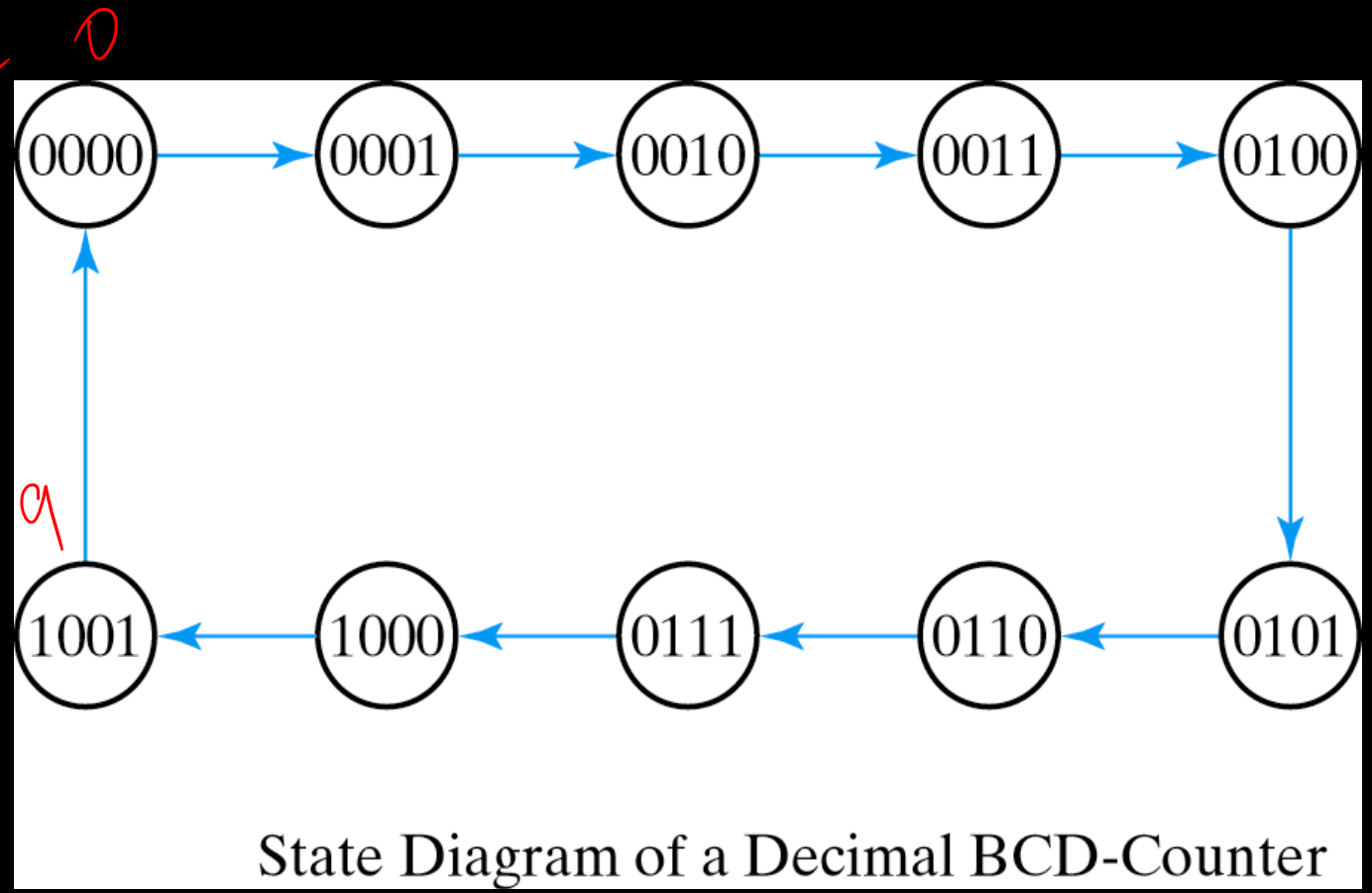


- Q1 complemented on every clock edge
- Q2 complemented when Q1 goes from 1 to 0. as long as Q8=0, when Q8=1, Q2 remains at 0
- Q4 complemented when Q2 goes from 1 to 0
- Q8 cleared (remains at zero) as long as Q4 or Q2 is 0 and Q8 complemented when Q4Q2 = 11 and Q1 goes from 1 to 0.

0000  
1111

Q8	Q4	Q2	Q1
0	0	0	0 ✓
0	0	0	1 ✓
0	0	1	0 ✓
0	0	1	1 ✓
0	1	0	0 ✓
0	1	0	1 ✓
0	1	1	0 ✓
0	1	1	1 ✓
1	0	0	0 ✓
1	0	0	1 ✓
0	0	0	0 ✓

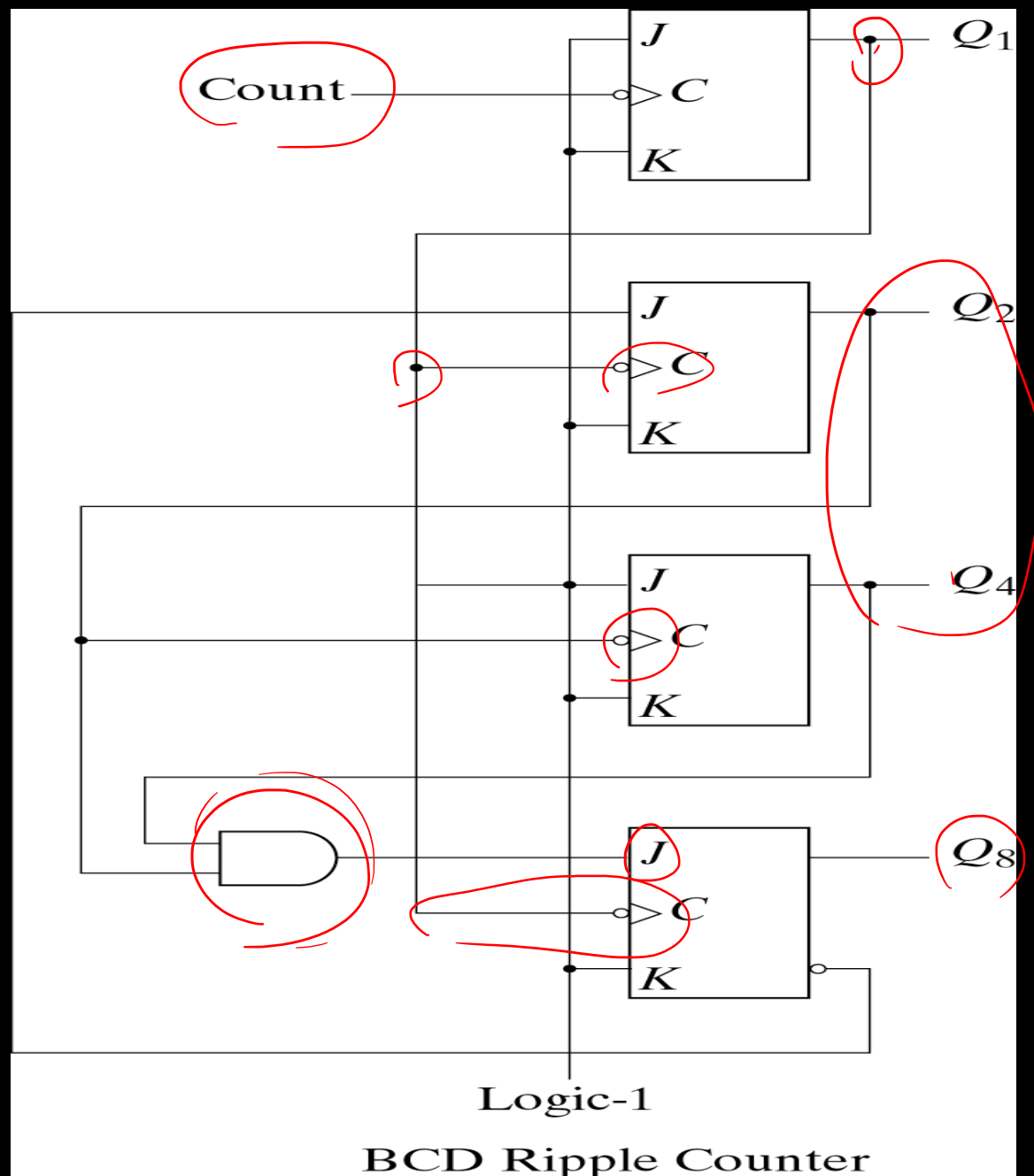

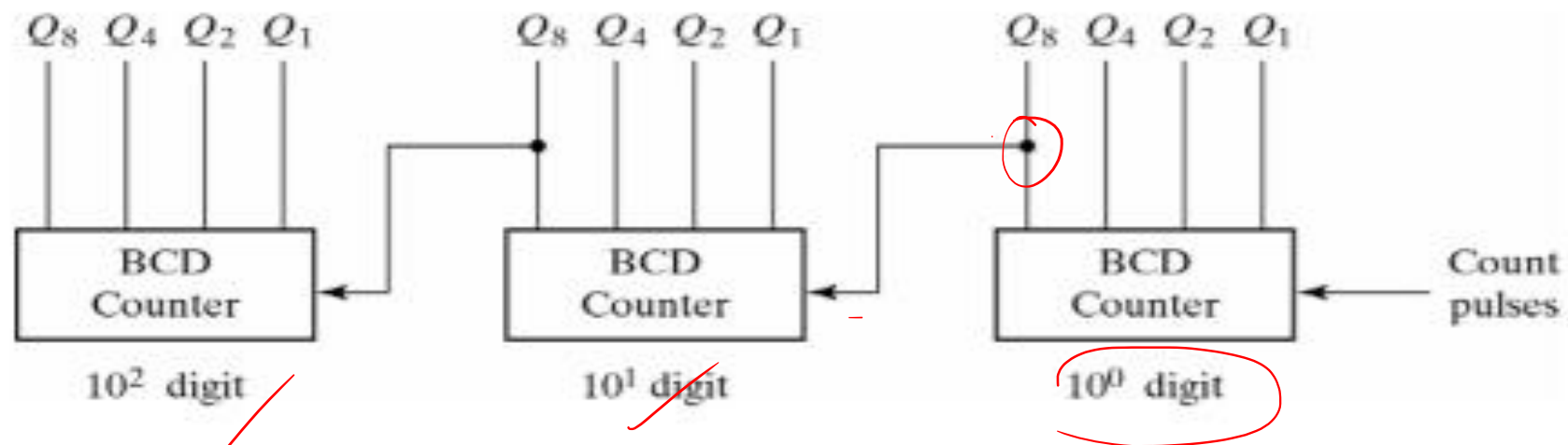A multiple decade counter can be constructed by connecting BCD counters in cascade. A three-*decade* counter is shown below:



The inputs to the second and third decades come from  $Q_8$  of the previous decade. When  $Q_8$  in one decade goes from 1 to 0, it triggers the count for the next higher-order decade while its own goes from 9 to 0.

## Modulo- $N$ counter

A counter that goes through a repeated sequence of ' $n$ ' states.

Ex. Mod-3 counter will go through 3 states 00 to 01 to 10 to 00

divide by  $N$  counter


Mod-10  
counter

## Mod Ripple counter

0 to 9

Can you design mod 10 counter counts till 9

1010  
0000

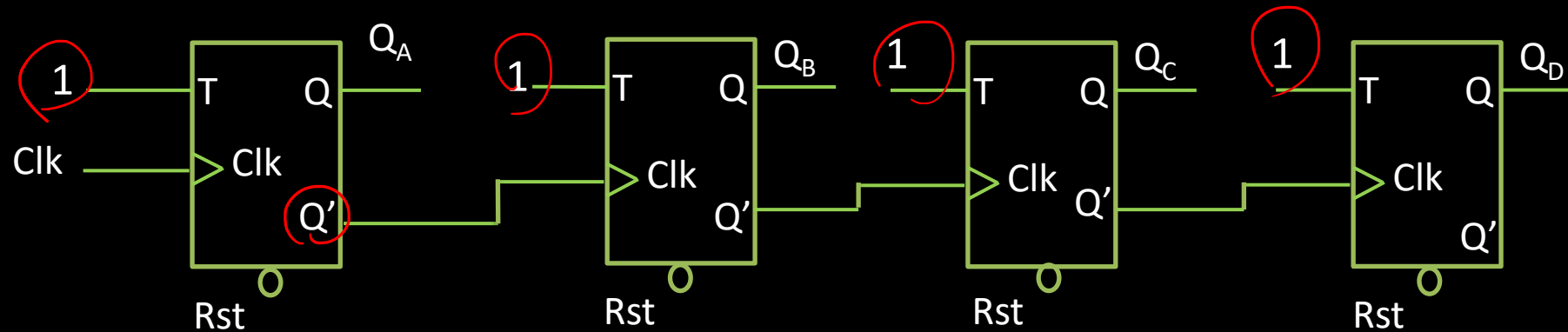

Counts from 0000 → 1111


As soon as 1010 reached all flip flops should be reset 0000

# Ripple Counters

mod-12  
0 to 11  
1100  
↓  
0000

Mod Ripple counter


Mod 10 counter counts till 9

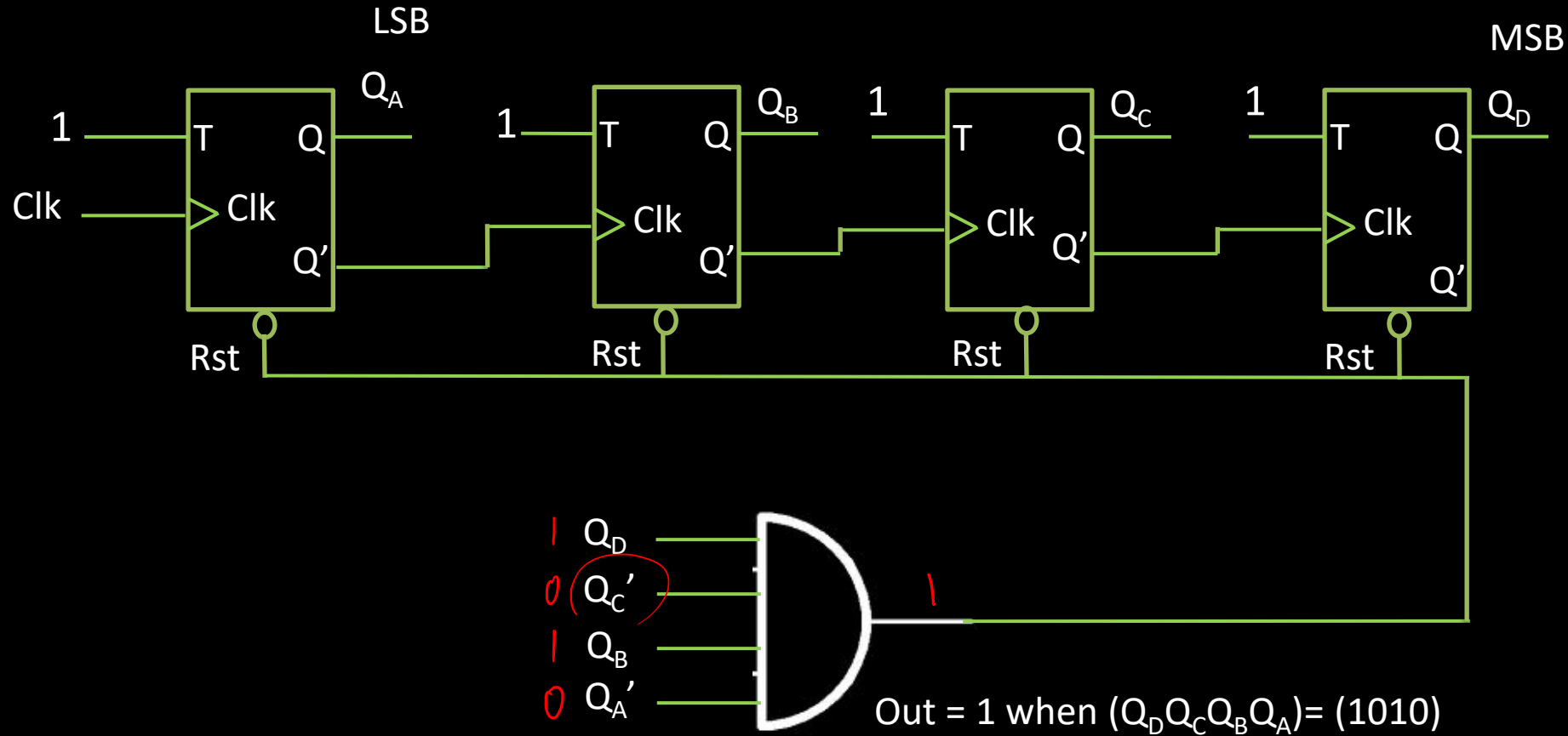

# Ripple Counters

Mod Ripple counter

Can you design Mod 12 counter

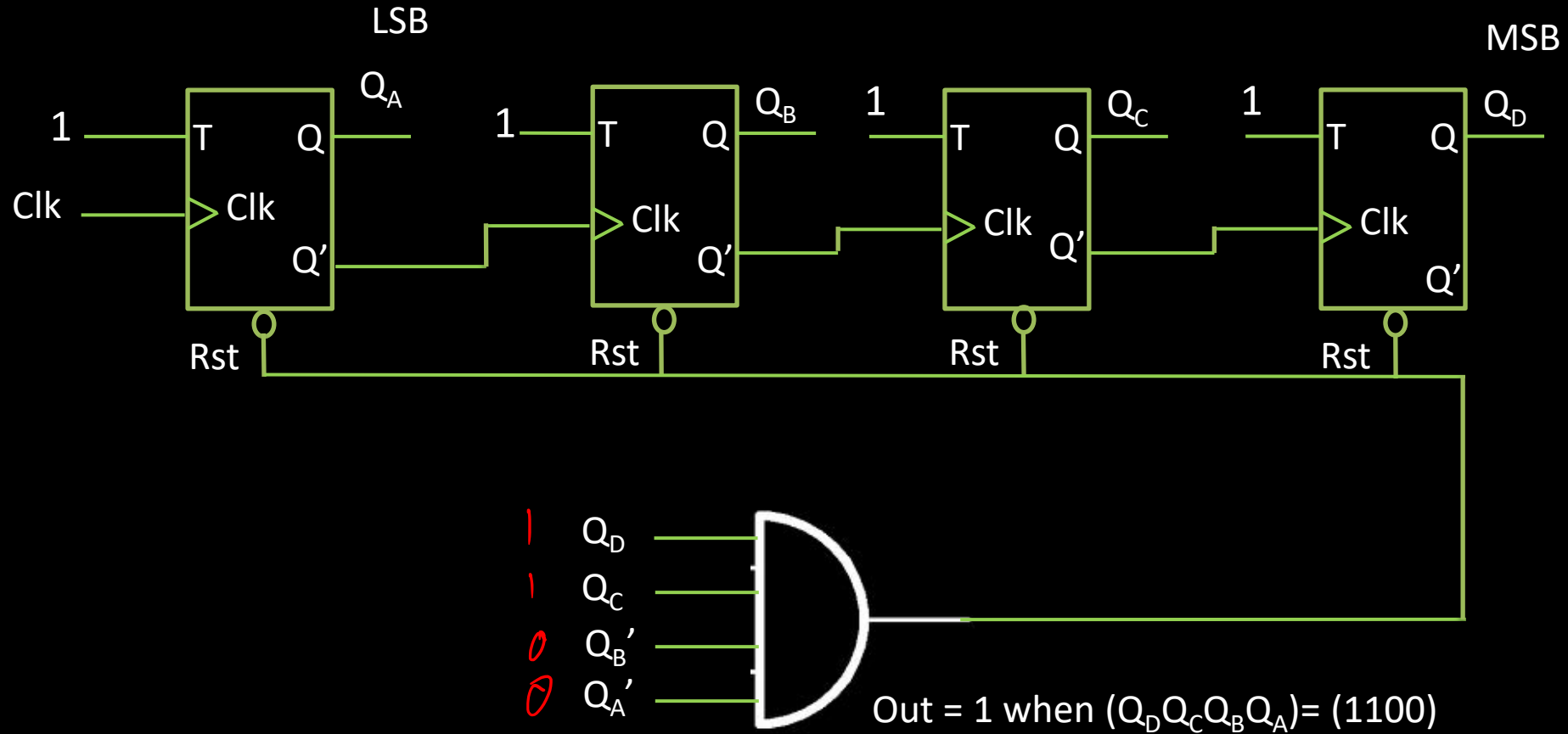



# Synchronous Counters

- The design procedure for a synchronous counter is the same as any other synchronous sequential circuit.
- The primary inputs of the circuit are the CLK and any control signals (EN, Load, etc).
- The primary outputs are the FF outputs (present state).
- Most efficient implementations usually use T-FFs or JK-FFs. (complementing FFs)

We will examine JK, T and D flip-flop designs.


# J-K Flip Flop Design of a 4-bit Binary Up Counter

innovate

achieve

lead

State diagram

 

# J-K Flip Flop Design of a 4-bit Binary Up Counter

innovate

achieve


lead

Present state				Next state				Flip-flop inputs							
Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	J <sub>Q3</sub>	K <sub>Q3</sub>	J <sub>Q2</sub>	K <sub>Q2</sub>	J <sub>Q1</sub>	K <sub>Q1</sub>	J <sub>Q0</sub>	K <sub>Q0</sub>
0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	0	0	1	1	0	1	0	X	0	0	X	1	X	X	1
1	0	1	0	1	0	1	1	X	0	0	X	X	0	1	X
1	0	1	1	1	1	0	0	X	0	1	X	X	1	X	1
1	1	0	0	1	1	0	1	X	0	X	0	0	X	1	X
1	1	0	1	1	1	1	0	X	0	X	0	1	X	X	1
1	1	1	0	1	1	1	1	X	0	X	0	X	0	1	X
1	1	1	1	0	0	0	0	X	1	X	1	X	1	X	1

# Synchronous Binary Counters:

## J-K Flip Flop Design of a Binary Up Counter

Present state				Next state					
$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3$	$Q_2$	$Q_1$	$Q_0$	$J_{Q3}$	$K_{Q3}$
0	0	0	0	0	0	0	1	0	X
0	0	0	1	0	0	1	0	0	X
0	0	1	0	0	0	1	1	0	X
0	0	1	1	0	1	0	0	0	X
0	1	0	0	0	1	0	1	0	X
0	1	0	1	0	1	1	0	0	X
0	1	1	0	0	1	1	1	0	X
0	1	1	1	1	0	0	0	1	X
1	0	0	0	1	0	0	1	X	0
1	0	0	1	1	0	1	0	X	0
1	0	1	0	1	0	1	1	X	0
1	0	1	1	1	1	0	0	X	0
1	1	0	0	1	1	0	1	X	0
1	1	0	1	1	1	1	0	X	0
1	1	1	0	1	1	1	1	X	0
1	1	1	1	0	0	0	0	X	1

 

# Synchronous Binary Counters:

## J-K Flip Flop Design of a Binary Up Counter

Present state				Next state				Flip-flop	
$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3$	$Q_2$	$Q_1$	$Q_0$	$J_{Q2}$	$K_{Q2}$
0	0	0	0	0	0	0	1	0	X
0	0	0	1	0	0	1	0	0	X
0	0	1	0	0	0	1	1	0	X
0	0	1	1	0	1	0	0	1	X
0	1	0	0	0	1	0	1	X	0
0	1	0	1	0	1	1	0	X	0
0	1	1	0	0	1	1	1	X	0
0	1	1	1	1	0	0	0	X	1
1	0	0	0	1	0	0	1	0	X
1	0	0	1	1	0	1	0	0	X
1	0	1	0	1	0	1	1	0	X
1	0	1	1	1	1	0	0	1	X
1	1	0	0	1	1	0	1	X	0
1	1	0	1	1	1	1	0	X	0
1	1	1	0	1	1	1	1	X	0
1	1	1	1	0	0	0	0	X	1

		1	
X	X	X	X
X	X	X	X
		1	

$$J_{Q2} = Q_0 Q_1$$

X	X	X	X
		1	
		1	
X	X	X	X

$$K_{Q2} = Q_0 Q_1$$

# Synchronous Binary Counters:

## J-K Flip Flop Design of a Binary Up Counter

Present state				Next state				p inputs	
$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3$	$Q_2$	$Q_1$	$Q_0$	$J_{Q1}$	$K_{Q1}$
0	0	0	0	0	0	0	1	0	X
0	0	0	1	0	0	1	0	1	X
0	0	1	0	0	0	1	1	X	0
0	0	1	1	0	1	0	0	X	1
0	1	0	0	0	1	0	1	0	X
0	1	0	1	0	1	1	0	1	X
0	1	1	0	0	1	1	1	X	0
0	1	1	1	1	0	0	0	X	1
1	0	0	0	1	0	0	1	0	X
1	0	0	1	1	0	1	0	1	X
1	0	1	0	1	0	1	1	X	0
1	0	1	1	1	1	0	0	X	1
1	1	0	0	1	1	0	1	0	X
1	1	0	1	1	1	1	0	1	X
1	1	1	0	1	1	1	1	X	0
1	1	1	1	0	0	0	0	X	1

		1	X	X
		1	X	X
		1	X	X
		1	X	X

$$J_{Q1} = Q_0$$

X	X	1	
X	X	1	
X	X	1	
X	X	1	

$$K_{Q1} = Q_0$$

