

BIRLA INSTITUTE OF SCIENCE AND TECHNOLOGY PILANI, HYDERABAD CAMPUS

DIGITAL DESIGN LABORATORY (Session 2021-22)

Workbook

Experiment -2

Full Name of the Student:



Complete ID of the student:

Title of Experiment:

 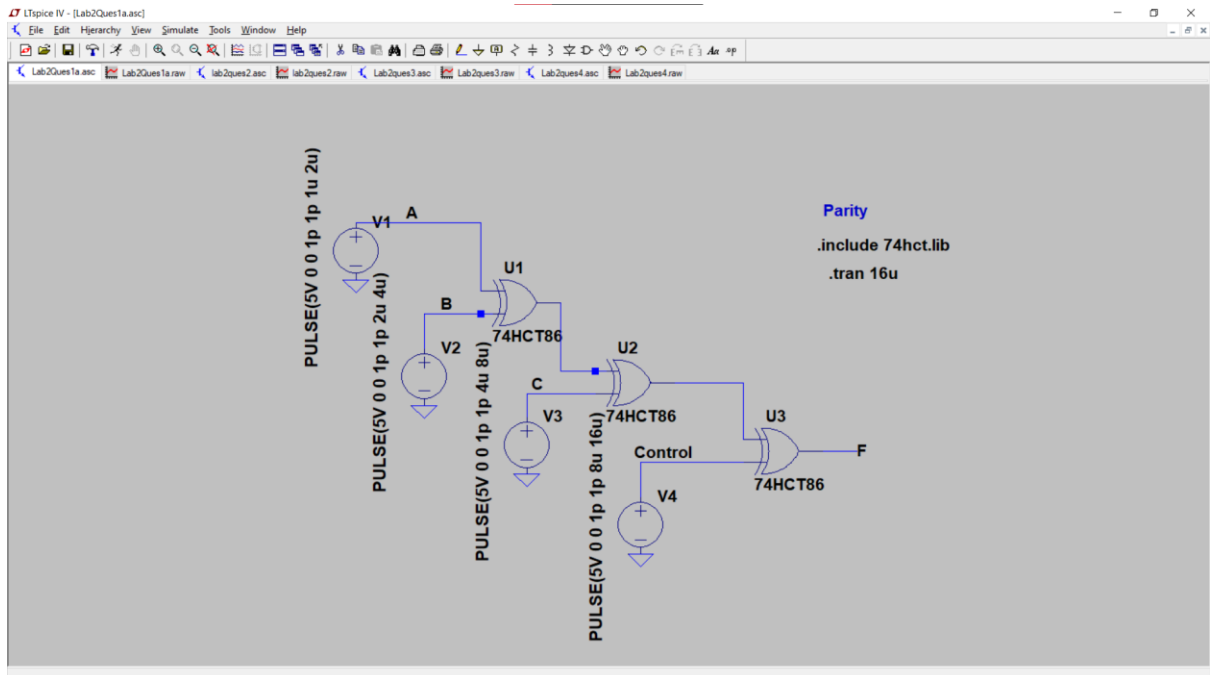Problem 1:

Implement the three variable (X,Y,Z) based 'Odd Parity' and 'Even Parity' Generator circuits using EX-OR Gates on LT-SPICE simulation platform.

(Provide proper LTSPICE model snapshot with neat levelling and show the graphical output at all the logic gates used in the circuit)



Left-Click to manually enter Left Vertical Axis Limits

Problem 2:


Design and implement '4-bit Binary to Grey code converter' with the help of Truth-Table on LT-SPICE simulation platform.

(Provide proper LTSPICE model snapshot with neat levelling and show the graphical output)

Problem 3:

Design and implement a two input Half- Adder circuit on LTSPICE platform.

(Provide proper LTSPICE model snapshot with neat levelling and show the graphical result containing the Inputs and Sum with Carry)

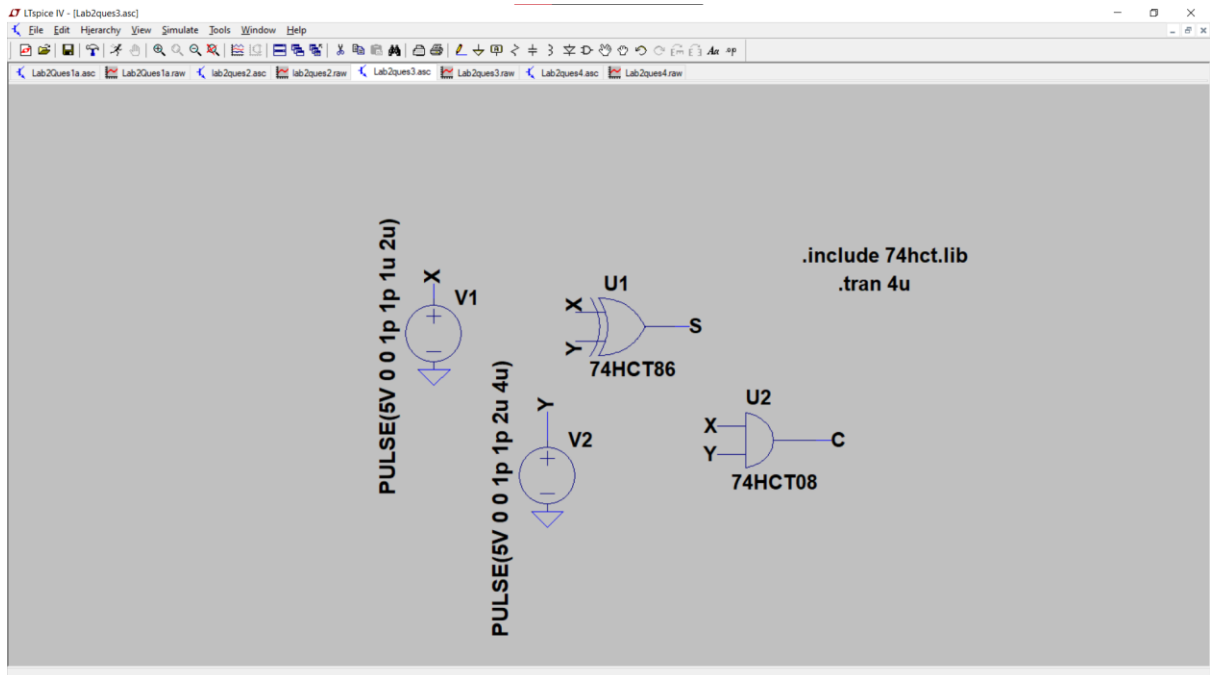

Problem 4:

Design and implement a two input Full- Adder circuit on LTSPICE platform.

(Provide proper LTSPICE model snapshot with neat levelling and show the graphical result containing the Inputs and Sum with Carry)

