

BIRLA INSTITUTE OF SCIENCE AND TECHNOLOGY PILANI, HYDERABAD CAMPUS

DIGITAL DESIGN LABORATORY

Experiment -1

Full Name of the Student: Shyam N V

Complete ID of the student: 2020A7PS2081H



Title: Implementation of majority circuit.

Problem 1:

Implement the Majority circuit; $F = AB + BC + AC$

with combination of 'THREE' 2 input AND & 'TWO' 2 input OR Gates using LTSPICE

(Provide proper LTSPICE model with neat levelling and Show the graphical output at all the logic gates used in the circuit)

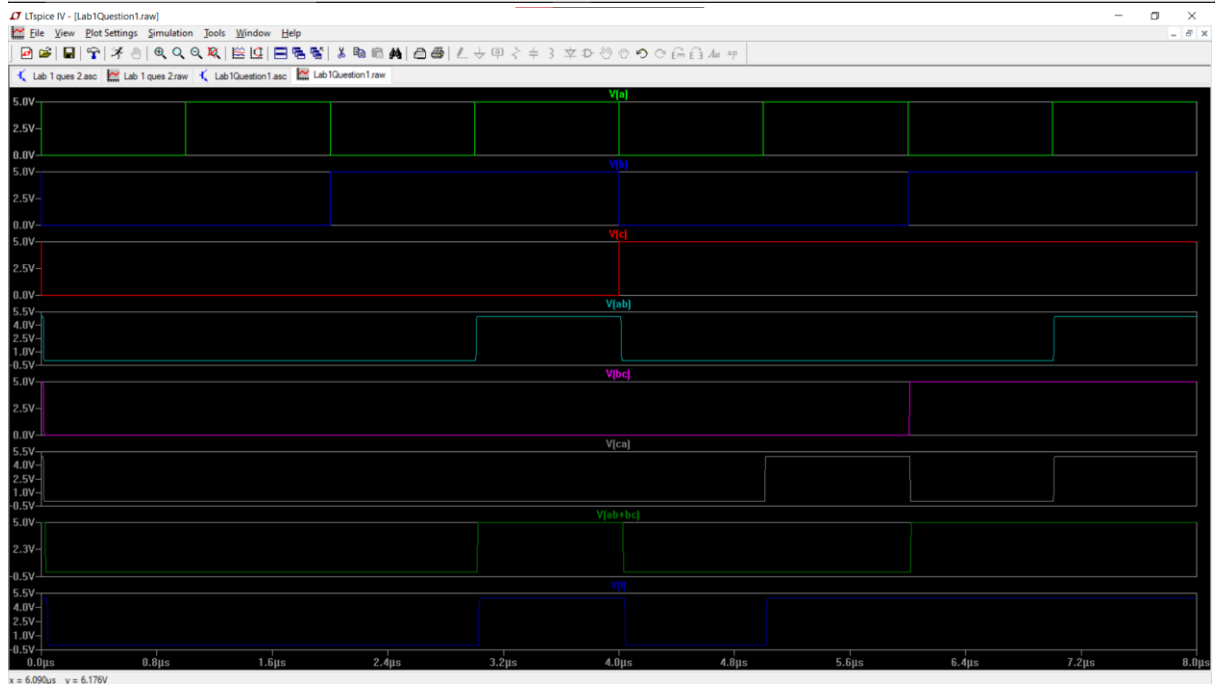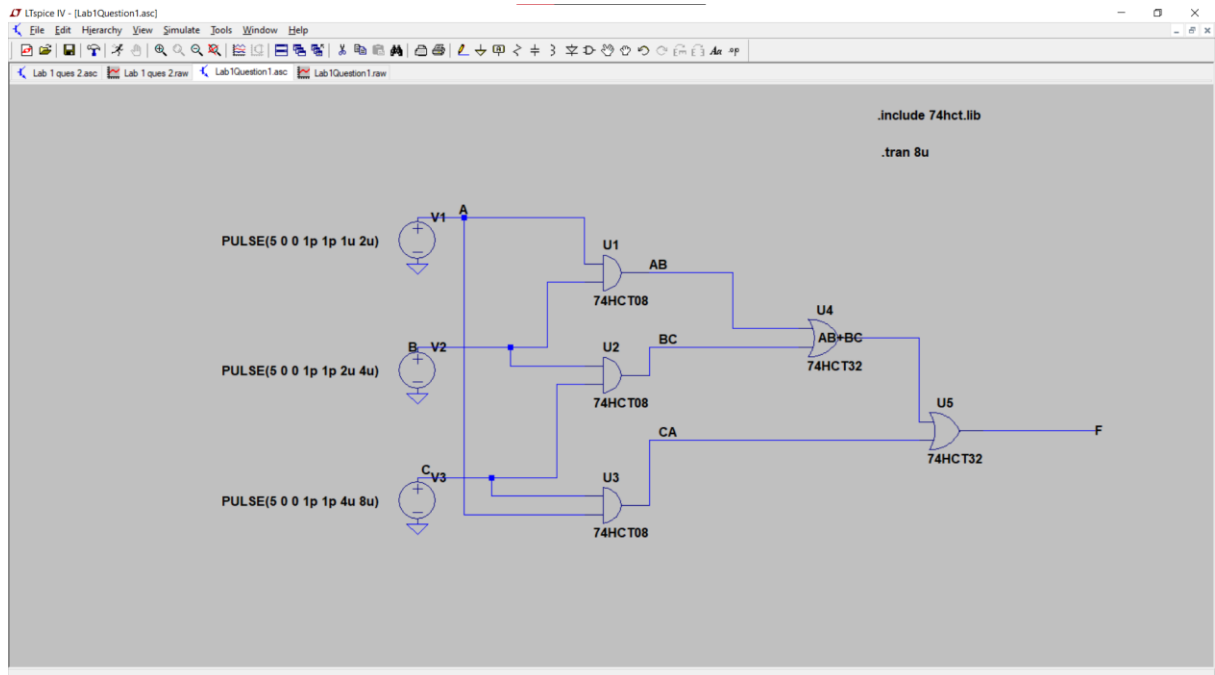

Problem 2:

Implement the Majority circuit; $F = AB + BC + AC$

with combination of 'TWO' 2 input NAND & 'ONE' 3 input NAND Gates using LTSPICE

(Provide proper LTSPICE model with neat levelling and Show the graphical output at all the logic gates used in the circuit)

