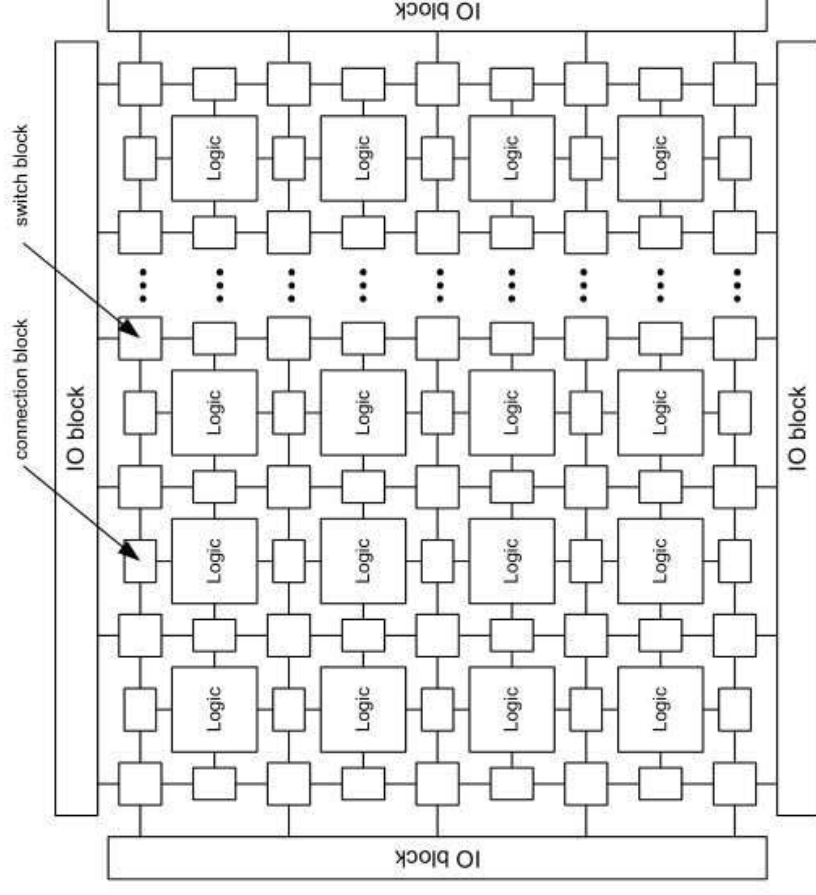




Thank You

Field Programmable Gate Array (FPGA)

- Typical FPGA consists of many small logic blocks interconnected by programmable routing resources.



Tabular Form Specification of interconnection


Solution

Contd.:

| Product term | AND Inputs | | | | Outputs |
|-----------------|------------|---|---|---|-------------------------------------------------------------------------------------------------------------------|
| | A | B | C | D | |
| 1 | 1 | 1 | 0 | — | $W = \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} \overline{C} \overline{D}$ |
| 2 | 0 | 0 | 1 | 0 | |
| 3 | — | — | — | — | |
| 4 | 1 | — | — | — | $X = A + B \overline{C} \overline{D}$ |
| 5 | — | 1 | 1 | 1 | |
| 6 | — | — | — | — | |
| 7 | 0 | 1 | — | — | $Y = \overline{A} \overline{B} + \overline{C} \overline{D} + \overline{B} \overline{D}$ |
| 8 | — | — | 1 | 1 | |
| 9 | — | 0 | — | 0 | |
| 10 | — | — | — | 1 | $Z = \overline{W} + \overline{A} \overline{C} \overline{D} + \overline{A} \overline{B} \overline{C} \overline{D}$ |
| 11 | 1 | — | 0 | 0 | |
| 12 | 0 | 0 | 0 | 1 | |

Solution

Contd...:

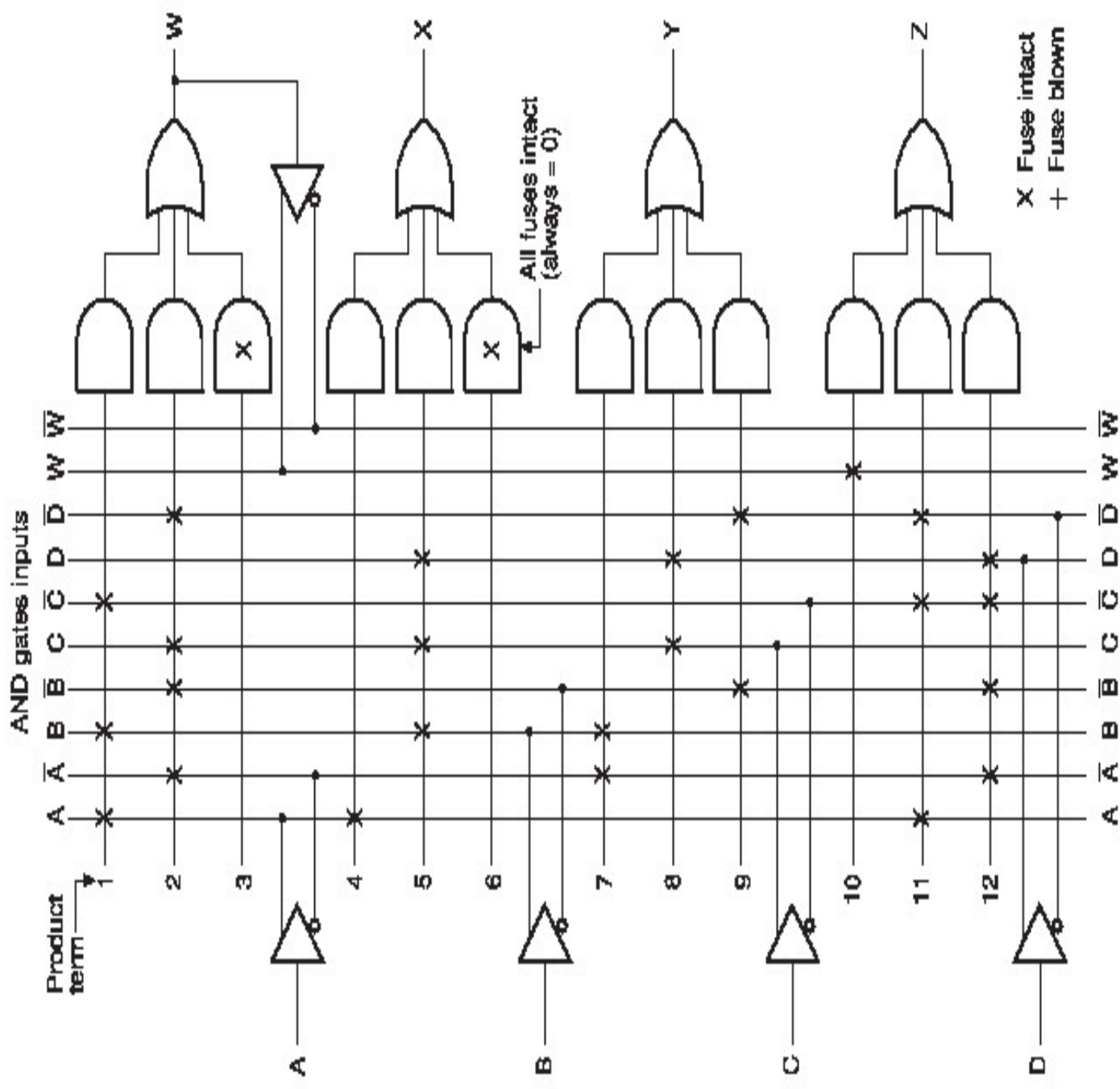



Solution:

Use function simplification techniques to derive:

$$W = ABC' + A'B'CD'$$

$$X = A + BCD$$

$$Y = A'B + CD + B'D'$$

$$\begin{aligned} Z &= ABC' + A'B'CD' + AC'D' + A'B'C'D \\ &= W + AC'D' + A'B'C'D \end{aligned}$$



Example:

Implement the combinational circuit described by the following equations, using a PAL with 4 inputs, 4 outputs, and 3-wide AND-OR structure.


$$W(A,B,C,D) = \sum m(2,12,13)$$

$$X(A,B,C,D) = \sum m(7,8,9,10,11,12,13,14,15)$$

$$Y(A,B,C,D) = \sum m(0,2,3,4,5,6,7,8,10,11,15)$$

$$Z(A,B,C,D) = \sum m(1,2,8,12,13)$$

PAL-based circuit implementation

 

$$\begin{aligned}
 W &= AB''C' + CD \\
 X &= A'BC'' + A'CD + ACD' + BCD \\
 Y &= A'C'D + ACD + A'BD
 \end{aligned}$$




PAL

- ❑ Similar to a PLA, but only has a programmable AND plane.
 - The OR plane is fixed.
- ❑ Not as flexible as a PLA since only certain AND gates feed each OR gate, but has fewer things that need programming.

PLA example

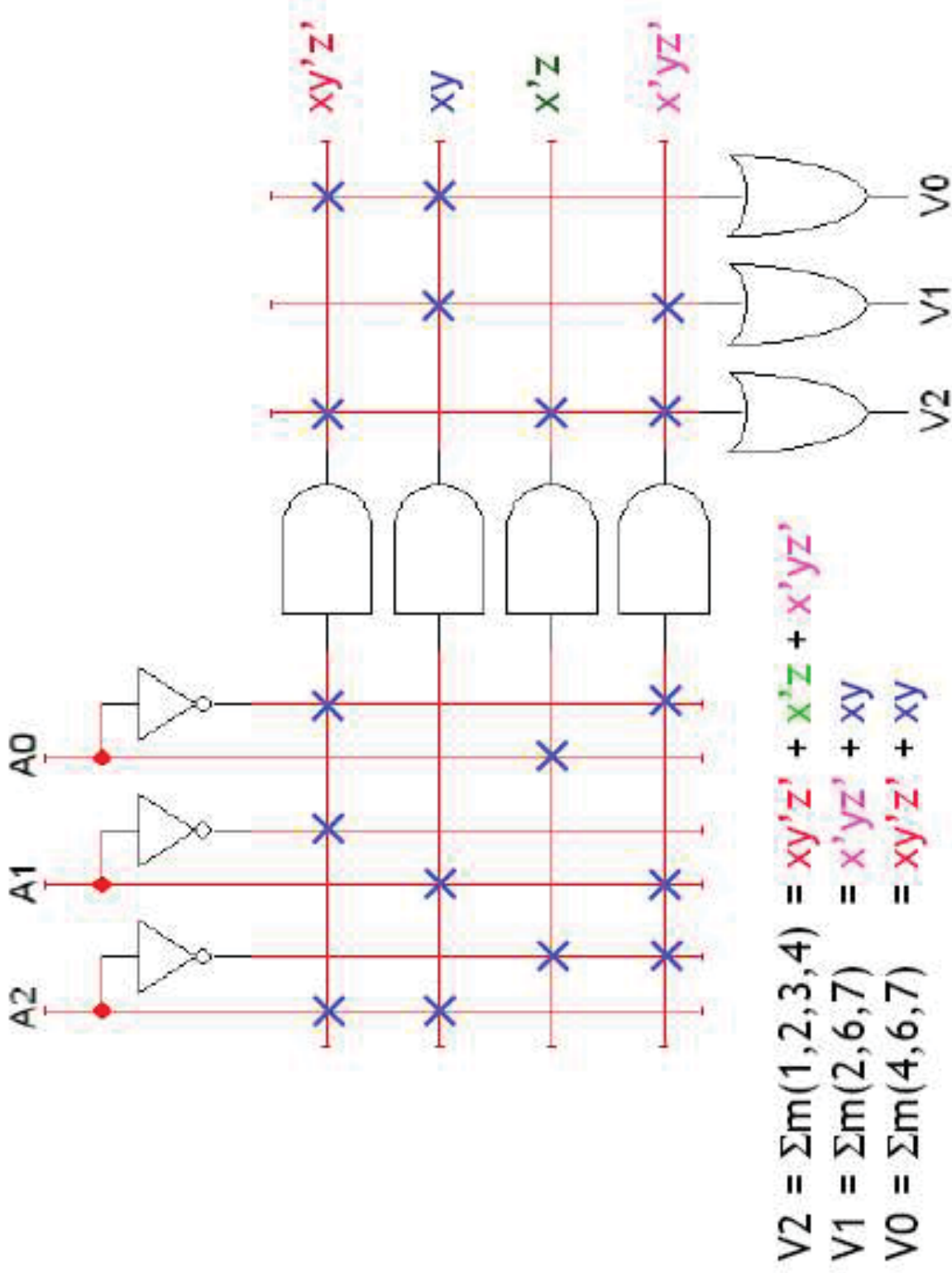- So we can implement these three functions using a $3 \times 4 \times 3$ PLA.



PLA minimization

- But for a PLA, what we really want is to minimize the number of product terms in *all* of the functions.
- We could express V2, V1 and V0 with just *four* total products instead.

$$V2 = \Sigma m(1, 2, 3, 4)$$

$$V1 = \Sigma m(2, 6, 7)$$

$$V0 = \Sigma m(4, 6, 7)$$

| | Y | | Z | |
|---|---|---|---|---|
| | 0 | 1 | 0 | 1 |
| X | 0 | 1 | 0 | 0 |
| | 1 | 0 | 0 | 0 |

$$V2 = xy'z' + x'z + x'yz'$$

| | Y | | Z | |
|---|---|---|---|---|
| | 0 | 0 | 1 | 1 |
| X | 0 | 0 | 0 | 1 |
| | 1 | 0 | 0 | 1 |

$$V1 = x'yz' + xy$$

| | Y | | Z | |
|---|---|---|---|---|
| | 0 | 0 | 1 | 1 |
| X | 0 | 0 | 0 | 1 |
| | 1 | 0 | 1 | 1 |

$$V0 = xy'z' + xy$$

Regular K-map minimization

- The normal K-map approach is to minimize the number of product terms for each *individual* function.
- For our three sample functions, this would result in a total of six different product terms.

$$V2 = \Sigma m(1, 2, 3, 4)$$

$$V1 = \Sigma m(2, 6, 7)$$

$$V0 = \Sigma m(4, 6, 7)$$

| | Y | | |
|---|---|---|---|
| | 0 | 1 | 1 |
| X | 0 | 1 | 0 |
| | 1 | 0 | 0 |

$$V2 = xy'z' + x'z + x'y$$

| | Y | | |
|---|---|---|---|
| | 0 | 0 | 1 |
| X | 0 | 0 | 1 |
| | 1 | 1 | 1 |


$$V1 = yz' + xy$$

| | Y | | |
|---|---|---|---|
| | 0 | 0 | 0 |
| X | 1 | 0 | 1 |
| | 1 | 1 | 1 |

$$V0 = xz' + xy$$

A blank $3 \times 4 \times 3$ PLA

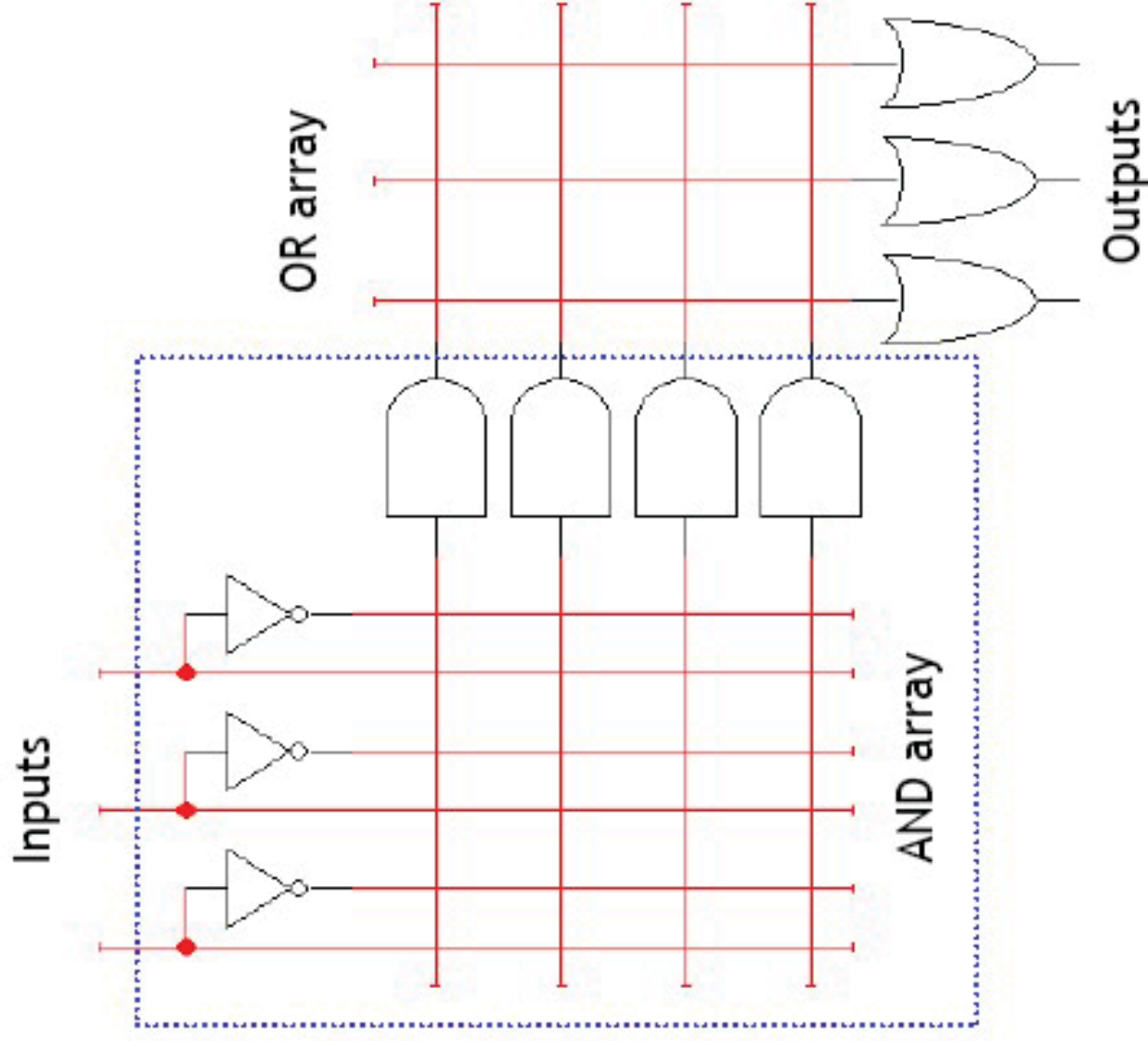- This is a $3 \times 4 \times 3$ PLA (3 inputs, up to 4 product terms, and 3 outputs), ready to be programmed.
- The left part of this diagram replaces the decoder used in a ROM.
- Connections are made within the **AND array** to produce four arbitrary products.
- Those products are then summed in the **OR array**.





PLA

It's a programmable device capable of implementing functions expressed in SOP.

- Consists of input buffers and inverters followed by:
- Programmable AND plane, followed by
- Programmable OR plane.
- Can implement ' m ' logic functions of ' n ' variables.



Types of PLD

Programmable Read Only Memory (PROM)

Programmable Logic Array (PLA)

Programmable Array Logic (PAL)

Field Programmable Gate Arrays (FPGAs)

Digital Design

Lecture 18: Programmable Logic Devices Contd..



Birla Institute of Technology & Science, Pilani
Hyderabad Campus






Thank You

- ROM implementation is not efficient for inputs with many don't care conditions
- It uses Decoders and generates all possible 'minterms', thus no circuit minimization is done


The same example again

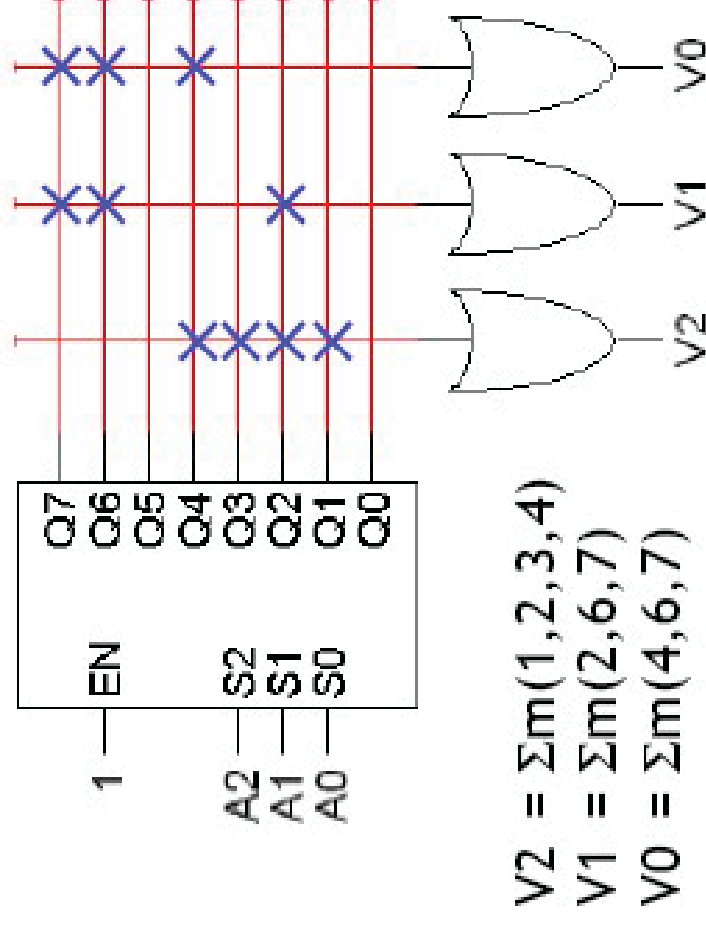- Here is an alternative presentation of the same 8×3 ROM, but with some simplified OR gates just to make the diagram neater.



ROM example

 - Here are three functions V_2 , V_1 and V_0 , implemented with our ROM.
- Blue crosses (X) indicate connections between decoder outputs and OR gates. Empty intersections are not connected.
- This is an **8 × 3 ROM** since there are 8 decoder outputs and 3 OR gates.




Boolean Function Implementation using ROM


$$V0 = \sum (4, 6, 7)$$

$$V1 = \sum (2, 6, 7)$$

$$V2 = \sum (1, 2, 3, 4)$$

- Building circuits with decoders is so easy that **programmable logic devices** are often based around decoders.
- The diagram below shows a blank **read-only memory**, or **ROM**, device.
 - It's just a decoder whose outputs may be sent to several OR gates.
 - The connections between the decoder outputs and the OR gate inputs are "programmable," so different functions can be implemented.
- To program a ROM for some specific functions, you just have to make the right connections.


 


 

- Address: m bits; data: n bits
- ROM contains 2^N word of M bit each
- The input bits decide the particular word that becomes available on output lines

ROM basics

  - A Memory Device in which permanent binary Information is stored
- Used to implement combinational circuits or store binary information
- ROM includes both decoders and OR gates within a single IC



Basic Configuration of Three PLDs



Types of PLD

Programmable Read Only Memory (PROM)

Programmable Logic Array (PLA)


Programmable Array Logic (PAL)

Simple Programmable Logic Device (SPLD)

Complex Programmable Logic Device (CPLD)

Field Programmable Gate Arrays (FPGAs)

PLD basic Architecture

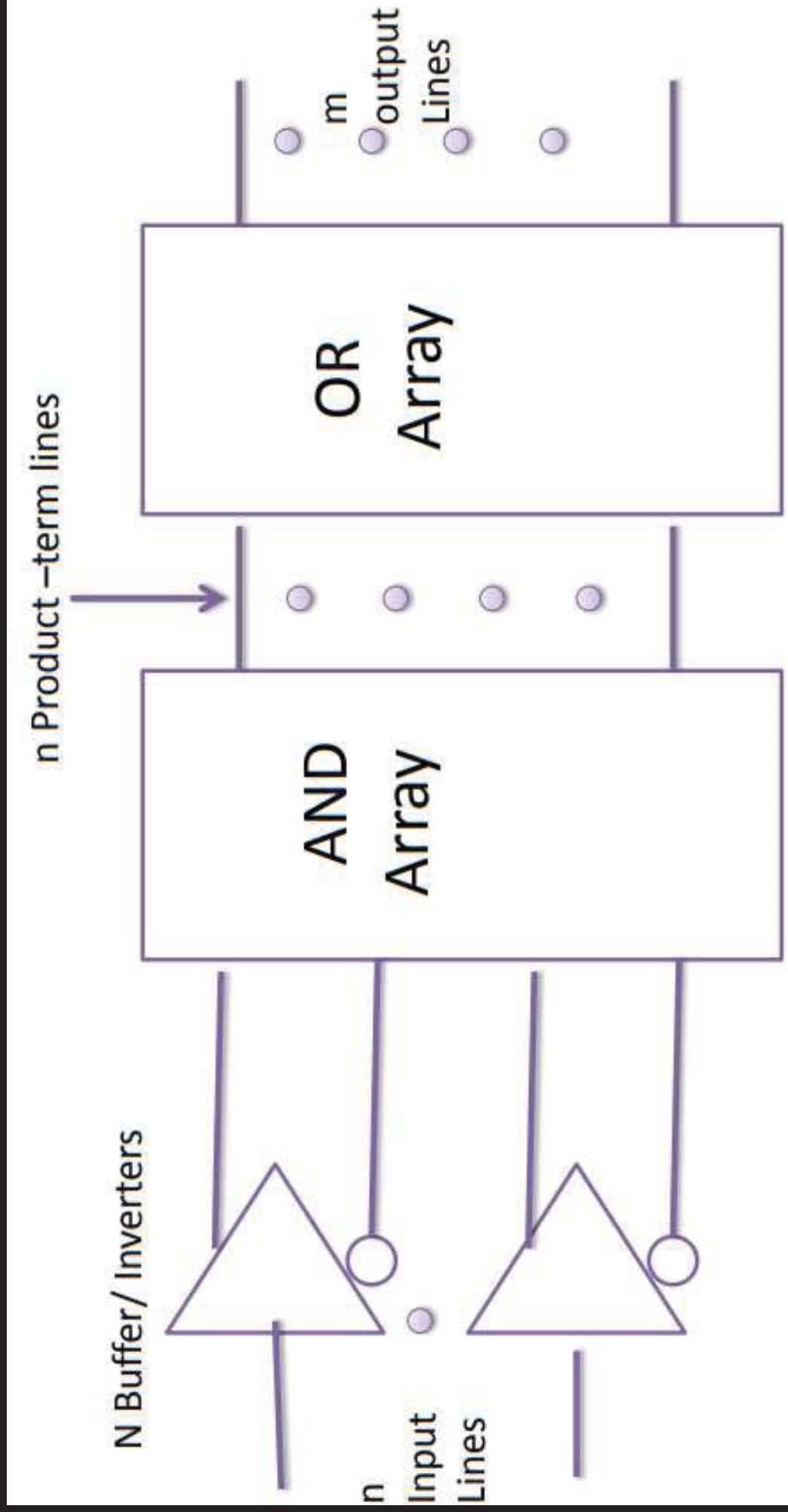

About PLDs

- Large circuit is designed on a single chip
- Can be programmed by the users as per their requirement
- Possible to implement a combinational or sequential circuit using the PLD
- Consist of array of AND, OR, NOT gates
- Any Boolean function can be represented by sum of the product (SOP) form.

Digital Design

Lecture 17: Programmable Logic Devices



Birla Institute of Technology & Science, Pilani
Hyderabad Campus

9/26/2021



Thank you

| A | Q | Q₋₁ | M = 0111 |
|-------------|-------------|-----------------------|-----------------|
| 0000 | 1101 | 0 | initial |
| 1001 | 1101 | 0 | A ← A-M |
| 1100 | 1110 | 1 | shift |
| 0011 | 1110 | 1 | A ← A+M |
| 0001 | 1111 | 0 | shift |
| 1010 | 1111 | 0 | A ← A-M |
| 1101 | 0111 | 1 | shift |
| 1110 | 1011 | 1 | shift |

Verify the operation of

$(+7) \times (-3)$

Multiplicand M = 0111

Multiplier Q = 1101

| A | Q | Q ₋₁ | M | Initial Values | |
|------|------|-----------------|------|----------------------|--------------|
| 0000 | 0011 | 0 | 0111 | | |
| 1001 | 0011 | 0 | 0111 | $A \leftarrow A - M$ | First Cycle |
| 1100 | 1001 | 1 | 0111 | Shift | |
| 1110 | 0100 | 1 | 0111 | Shift | Second Cycle |
| 0101 | 0100 | 1 | 0111 | $A \leftarrow A + M$ | |
| 0010 | 1010 | 0 | 0111 | Shift | Third Cycle |
| 0001 | 0101 | 0 | 0111 | Shift | |
| | | | | | Fourth Cycle |

| A | Q | Q ₋₁ | M | Initial Values | |
|------|------|-----------------|------|----------------------|-----------------|
| 0000 | 0011 | 0 | 0111 | | |
| 1001 | 0011 | 0 | 0111 | $A \leftarrow A - M$ | First Cycle |
| 1100 | 1001 | 1 | 0111 | Shift | |
| 1110 | 0100 | 1 | 0111 | Shift | Second Cycle |
| 0101 | 0100 | 1 | 0111 | $A \leftarrow A + M$ | |
| 0010 | 1010 | 0 | 0111 | Shift | Third Cycle |

| A | Q | Q ₋₁ | M | Initial Values | |
|------|------|-----------------|------|----------------------|-----------------|
| 0000 | 0011 | 0 | 0111 | | |
| 1001 | 0011 | 0 | 0111 | $A \leftarrow A - M$ | First Cycle |
| 1100 | 1001 | 1 | 0111 | Shift | |
| 1110 | 0100 | 1 | 0111 | Shift | Second Cycle |
| 0101 | 0100 | 1 | 0111 | $A \leftarrow A + M$ | |

| A | Q | Q ₋₁ | M | Initial Values | |
|------|------|-----------------|------|----------------------|--------------|
| 0000 | 0011 | 0 | 0111 | | |
| 1001 | 0011 | 0 | 0111 | $A \leftarrow A - M$ | First Cycle |
| 1100 | 1001 | 1 | 0111 | Shift | |
| 1110 | 0100 | 1 | 0111 | Shift | Second Cycle |


| A | Q | Q ₋₁ | M | Initial Values |
|------|------|-----------------|------|------------------------------------------------------------------------------------------------------|
| 0000 | 0011 | 0 | 0111 | |
| 1001 | 0011 | 0 | 0111 | $\left. \begin{array}{l} A \leftarrow A - M \\ \text{Shift} \end{array} \right\} \text{First Cycle}$ |
| 1100 | 1001 | 1 | 0111 | |

| A | Q | Q ₋₁ | M | Initial Values |
|------|------|-----------------|------|----------------------|
| 0000 | 0011 | 0 | 0111 | |
| 1001 | 0011 | 0 | 0111 | $A \leftarrow A - M$ |

| A | Q | Q ₋₁ | M | Initial Values |
|------|------|-----------------|------|----------------|
| 0000 | 0011 | 0 | 0111 | |

Booth's Algorithm

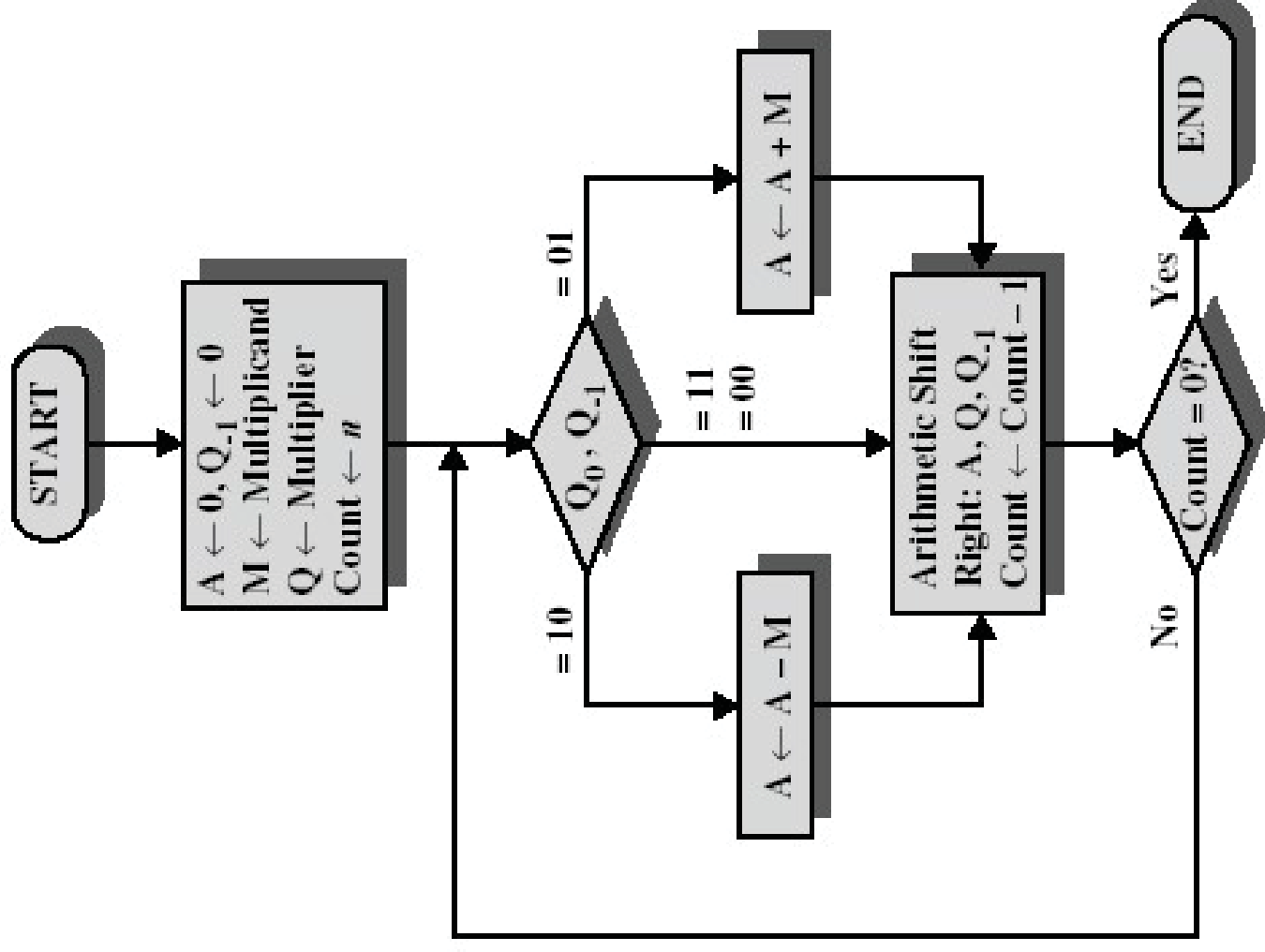1. Multiplier and multiplicand are placed in Q and M registers.
2. A 1-bit register is placed to the right of the least significant bit (Q_0) and designated Q_{-1} .
3. Control logic scans the bits of the multiplier one at a time; but a bit and its bit to the right are examined. If the bits are the same (1-1 or 0-0) then all bits of the A, Q, and Q_{-1} registers are shifted to the right 1 bit. If the two bits differ, then the multiplicand is added/subtracted depending on whether the bits are 0-1 or 1-0. Addition is followed by a **right arithmetic shift**.



- Booth re-coding Procedure working from LSB to MSB retain each 0 until a 1 is reached
- When a 1 is encountered insert $\overline{1}$ at that position and complement all the succeeding 1's until a 0 is encountered
- Replace that 0 with 1 and continue same
- while multiplying with $\overline{1}$; 2's complement addition is used

- Booth's algorithm called skipping over one's
- String of 1's replaced by 0's
- **For example: 30 = 0011110**
- **= 32 – 2 = 0100000 – 0000010**
- **In the coded form = 01000[–]10**

Multiplicand ‘M’ unchanged

The multiplier ‘Q’ to a re-coded value R

Each digit can assume a negative as well as positive and zero values

Signed Digit (SD) encoding

**This Approach will not work if numbers
are signed**

ALTERNATIVE


BOOTH'S MULTIPLIER

| C | A | Q | M | Initial Values |
|---|------|------|------|----------------|
| 0 | 0000 | 1101 | 1011 | |
| 0 | 1011 | 1101 | 1011 | } First Cycle |
| 0 | 0101 | 1110 | 1011 | |
| 0 | 0010 | 1111 | 1011 | } Second Cycle |
| 0 | 1101 | 1111 | 1011 | |
| 0 | 0110 | 1111 | 1011 | } Third Cycle |
| 1 | 0001 | 1111 | 1011 | |
| 0 | 1000 | 1111 | 1011 | } Fourth Cycle |
| | | | | |

| C | A | Q | M | Initial Values |
|---|------|------|------|----------------------------------------------------------|
| 0 | 0000 | 1101 | 1011 | |
| 0 | 1011 | 1101 | 1011 | <div> <div>Add</div> <div>Shift</div> </div> First Cycle |
| 0 | 0101 | 1110 | 1011 | |
| 0 | 0010 | 1111 | 1011 | <div>Shift</div> |
| | | | | |

| C | A | Q | M | |
|---|------|------|------|----------------|
| 0 | 0000 | 1101 | 1011 | Initial Values |
| 0 | 1011 | 1101 | 1011 | } First Cycle |
| 0 | 0101 | 1110 | 1011 | |


| C | A | Q | M | |
|---|------|------|------|----------------|
| 0 | 0000 | 1101 | 1011 | Initial Values |

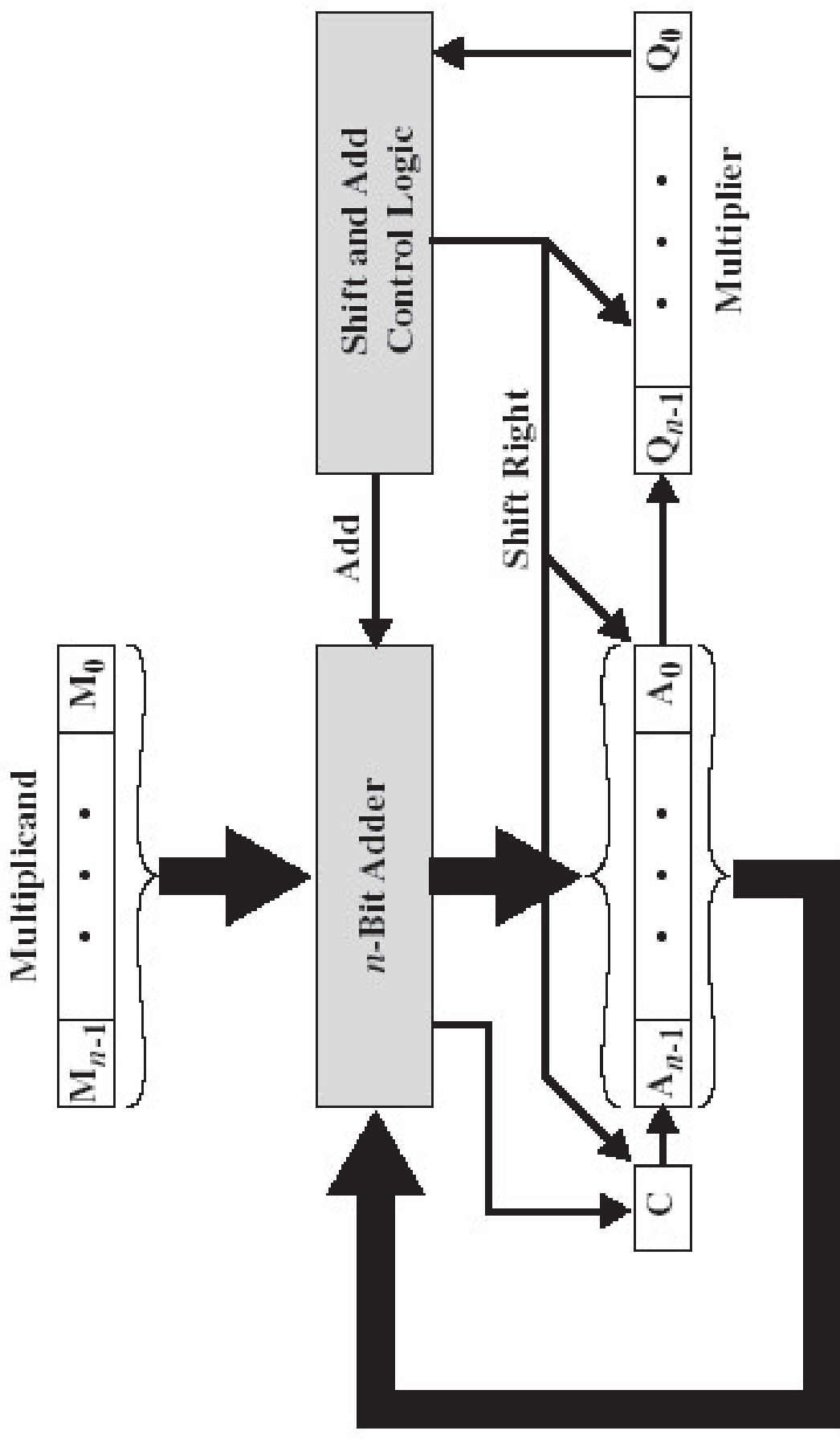

1. Multiplier and multiplicand are loaded into registers Q and M.
2. A third register (A) is initially set to zero.
3. A one-bit C register (initialised to zero) holds carry bits.

Multiplication

 1. The Digital system can keep a running product rather than summing at the end.
2. For each '1' in the multiplier we can apply an 'add' and a 'shift'.
3. For each '0' only a shift is needed.



Multiplication

Some general observations

- Multiplication involves the generation of partial products – one for each digit in the multiplier.
- Partial products are summed to produce the final product.
- Partial products are simple to define for binary multiplication. If the digit in multiplier is ‘one’ the partial product is the multiplicand, otherwise the partial product is zero.
- The total product is the sum of the partial products. Each successive partial product is shifted one position to the left.
- The multiplication of two n-bit binary numbers results in a product of up to 2n bits in length.

$$\begin{array}{r} 1011 \\ 1101 \\ \hline 1011 \\ 0000 \\ 1011 \\ 1011 \\ \hline 10001111 \end{array}$$

Digital Design

Lecture No. 16


MULTIPLICATION ALGORITHMS




Thank You

74HCT125 Quad Tri-State Buffer


LOGIC SYMBOL

 


Tri-state Buffer

 

Mux

 


Decoder

 

Encoder

Multiplexers: Realization using Op-Amp

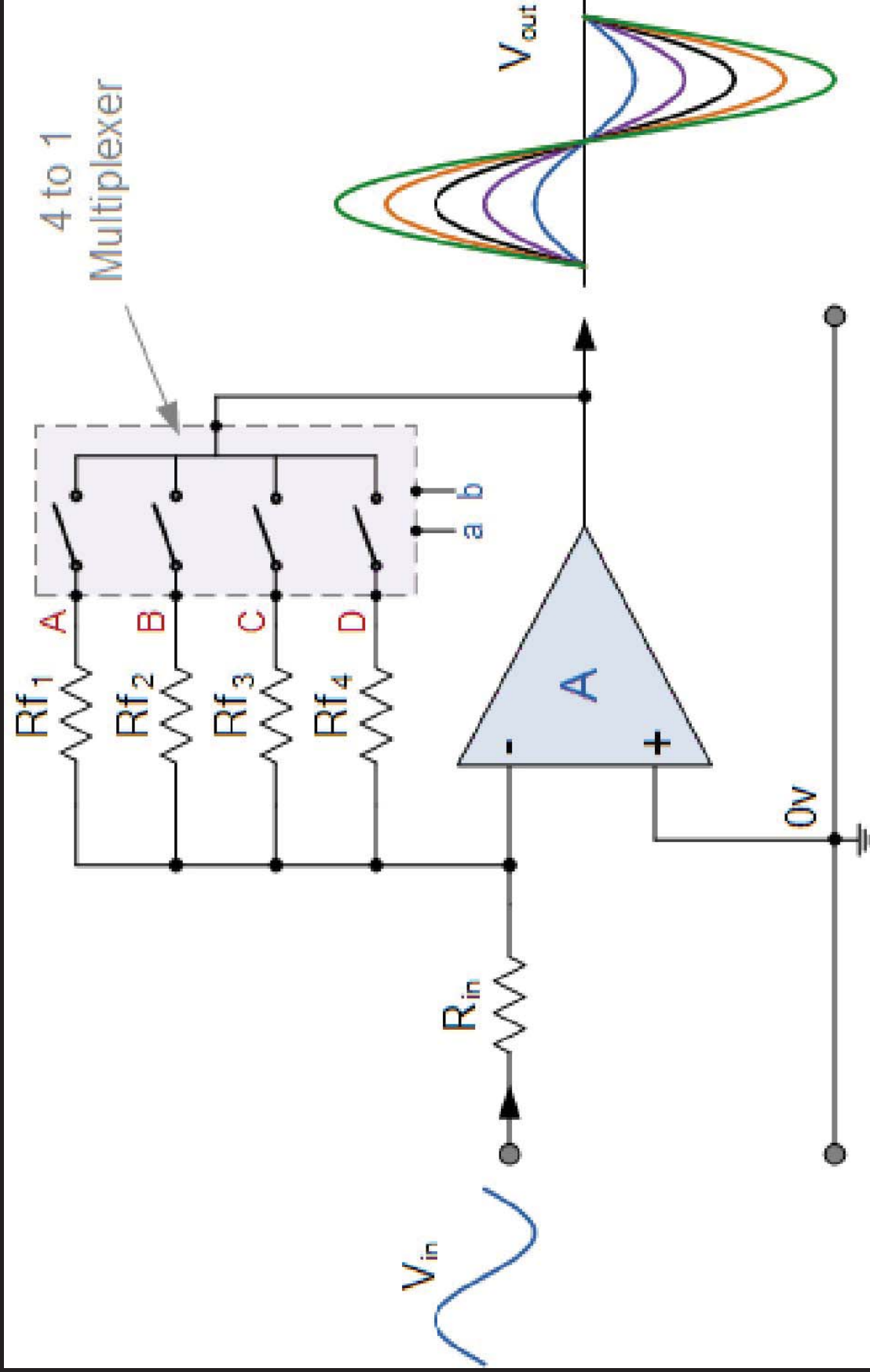


Multiplexers

Boolean Function implementation

1. $F(X,Y,Z) = \sum(1, 3, 5, 6, 7)$ using 4:1 MUX and 2:1 MUX

2. $F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$ Using 8:1 MUX and 4:1 MUX

 3. The logic function implemented by the circuit below is (Ground implies logic '0')




Efficient implementation: Even-parity function

Original truth table

| A | B | C | F_1 |
|---|---|---|-------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

New truth table

| A | B | F_1 |
|---|---|----------------|
| 0 | 0 | C |
| 0 | 1 | \overline{C} |
| 1 | 0 | \overline{C} |
| 1 | 1 | C |

 



Multiplexers

Boolean Function implementation


$$F(X,Y,Z) = \sum (1, 2, 6, 7)$$

2:1
Multiplexer

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

$F = Y \oplus Z$

$F = Y$

 



Multiplexers

Boolean Function implementation

$$F(X,Y,Z) = \sum (1, 2, 6, 7)$$

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |


$$F = Z$$

$$F = Z'$$

$$F = 0$$

$$F = 1$$

4:1
Multiplexer

 


Multiplexers

Boolean Function implementation using MUX,

$$F(X,Y,Z) = \sum (1, 2, 6, 7)$$

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

 

Digital Design

Lecture 15: Multiplexer and Demultiplexer


Contd....



Birla Institute of Technology & Science, Pilani

Hyderabad Campus

9/23/2023

 





Thank You

74HCT125 Quad Tri-State Buffer


LOGIC SYMBOL

 


Tri-state Buffer

 

Mux

 


Decoder

 

Encoder

Multiplexers: Realization using Op-Amp

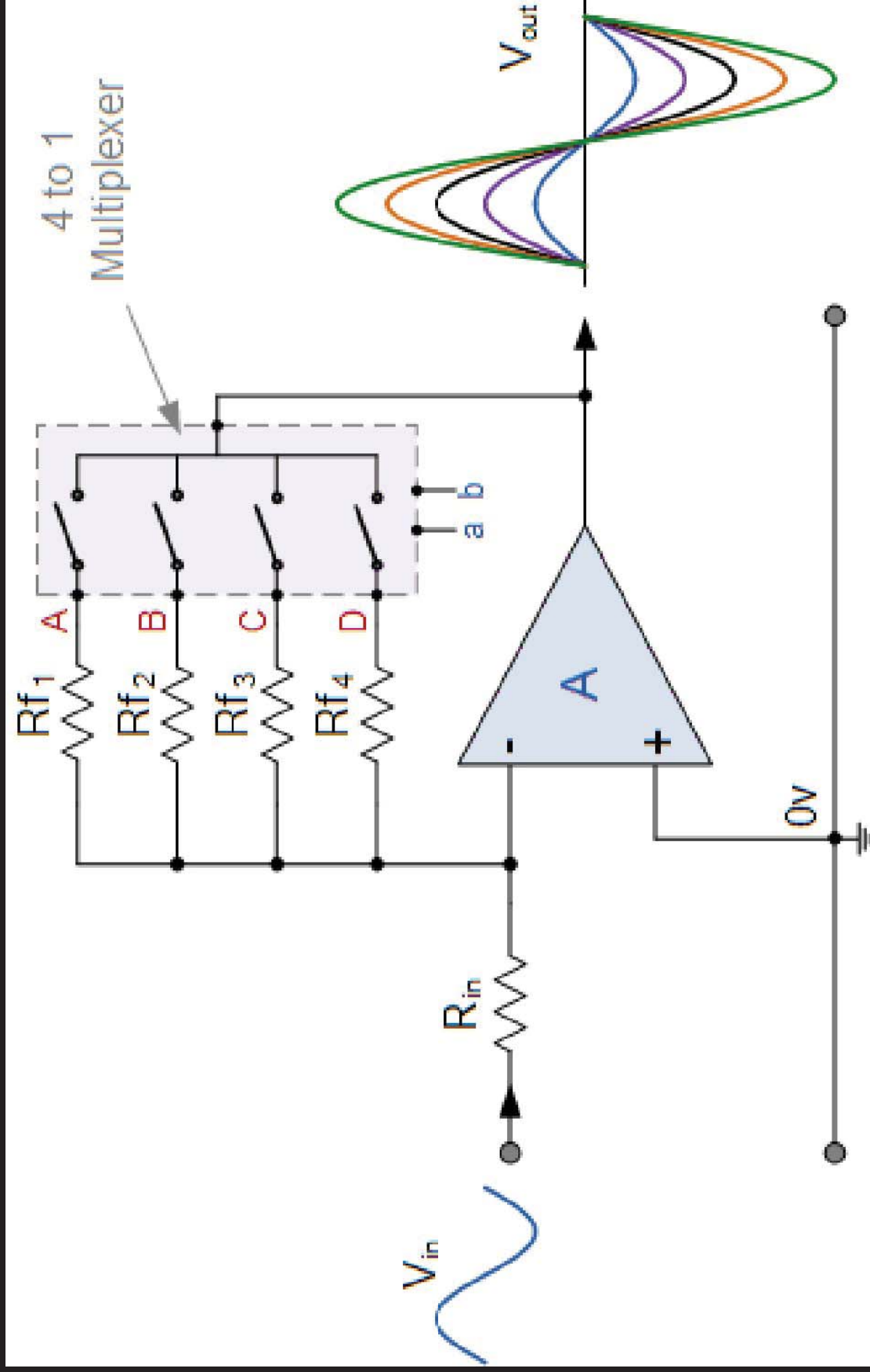


Multiplexers

Boolean Function implementation

1. $F(X,Y,Z) = \sum (1, 3, 5, 6, 7)$ using 4:1 MUX and 2:1 MUX

2. $F(A, B, C, D) = \sum (1, 3, 4, 11, 12, 13, 14, 15)$ Using 8:1 MUX and 4:1 MUX

 3. The logic function implemented by the circuit below is (Ground implies logic '0')





Multiplexers

Boolean Function implementation


$$F(X,Y,Z) = \sum (1, 2, 6, 7)$$

2:1
Multiplexer

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

$F = Y \oplus Z$

$F = Y$

 



Multiplexers

Boolean Function implementation

$$F(X,Y,Z) = \sum (1, 2, 6, 7)$$

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |


$$F = Z$$

$$F = Z'$$

$$F = 0$$

$$F = 1$$


4:1
Multiplexer

 



Boolean Function implementation

$$F(X,Y,Z) = \sum (1, 2, 6, 7)$$

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

 

 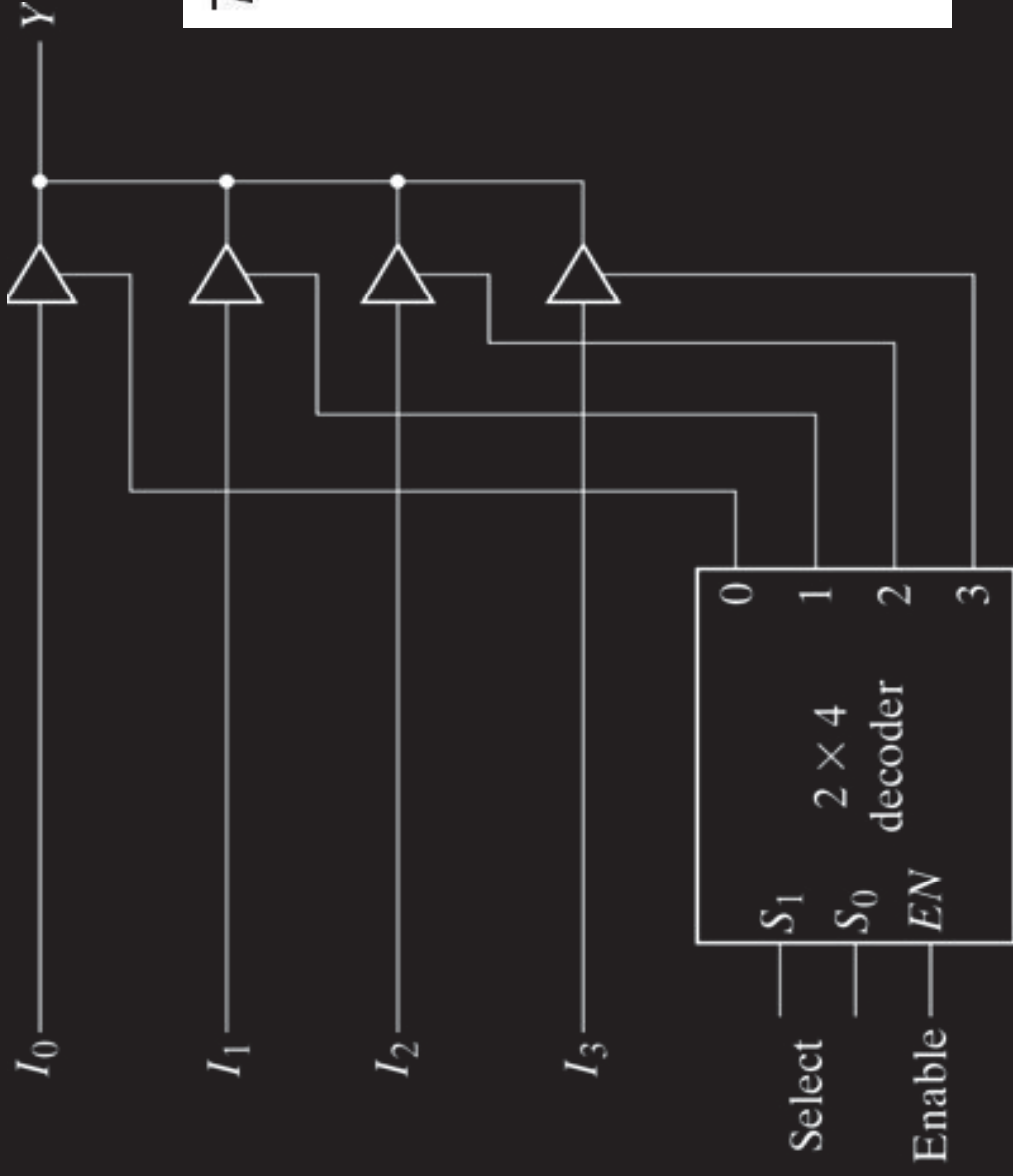4:1 MUX using Tri-state buffers and 2 to 4 Decoder





Multiplexers

Multiplexers can be constructed using 3-state gates


Tri-State Buffer



2:1 MUX using Tri-state buffer

  

Multiplexers

 


Multiple Bit Selection Logic

| E | S | Output Y |
|---|---|----------|
| 1 | 0 | |
| 1 | 1 | |
| 0 | 0 | |
| 0 | 1 | |

Analyze and Complete the table

4:1 Multiplexer – 4:1 MUX Using 2:1 MUX

| S_1 | S_0 | O/P |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |

 




Multiplexers


4:1 Multiplexer – 4:1 MUX Using 2:1 MUX

| S_1 | S_0 | O/P |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |

 


4:1 Multiplexer – 4:1 MUX Using 2:1 MUX

| S_1 | S_0 | O/P |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |

 

4:1 Multiplexer – 4:1 MUX Using 2:1 MUX


| S_1 | S_0 | O/P |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |

 

Multiplexers

4:1 Multiplexer – 4:1 MUX

| S_1 | S_0 | O/P |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |

 

$$O/P = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$

Implement the operation using suitable logic circuit



Multiplexers

2:1 Multiplexer – 2:1 MUX

I_0 and I_1 are input lines and 'S' is select line

If $s=0$ then $o/p = I_0$
 If $s=1$ then $o/p = I_1$

$$o/p = I_0 \cdot S' + I_1 \cdot S$$

  




Multiplexers


Multiplexer - combinational circuit that selects binary information from one of many input lines and directs it to single output line

The selection is controlled by Select lines

 In general, 2^n input lines, 'n' selection lines and 1 output



(a)

 


(b)

BCD-7segment display using decoders

Most digital equipment has some means for displaying information in a form that can be understood by the user.

 One of the simplest and most popular methods for displaying numerical digits uses a 7-segment configuration to form digital characters 0 to 9 and some times the hex characters A to F



Digital Design

Lecture 14: Multiplexer



Birla Institute of Technology & Science, Pilani


Hyderabad Campus

9/23/2023




Thank You


Decoder Applications

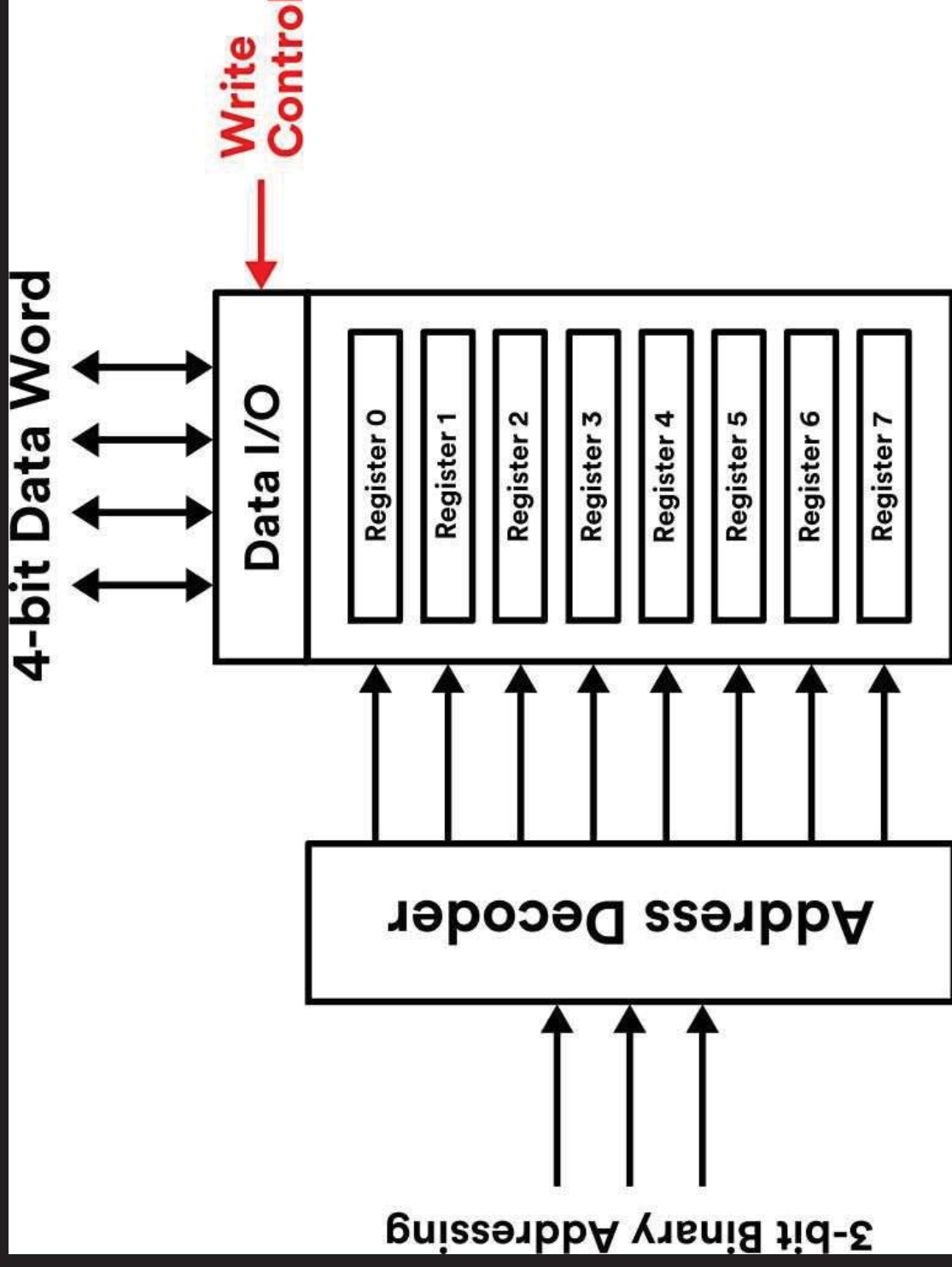


Encoder Applications

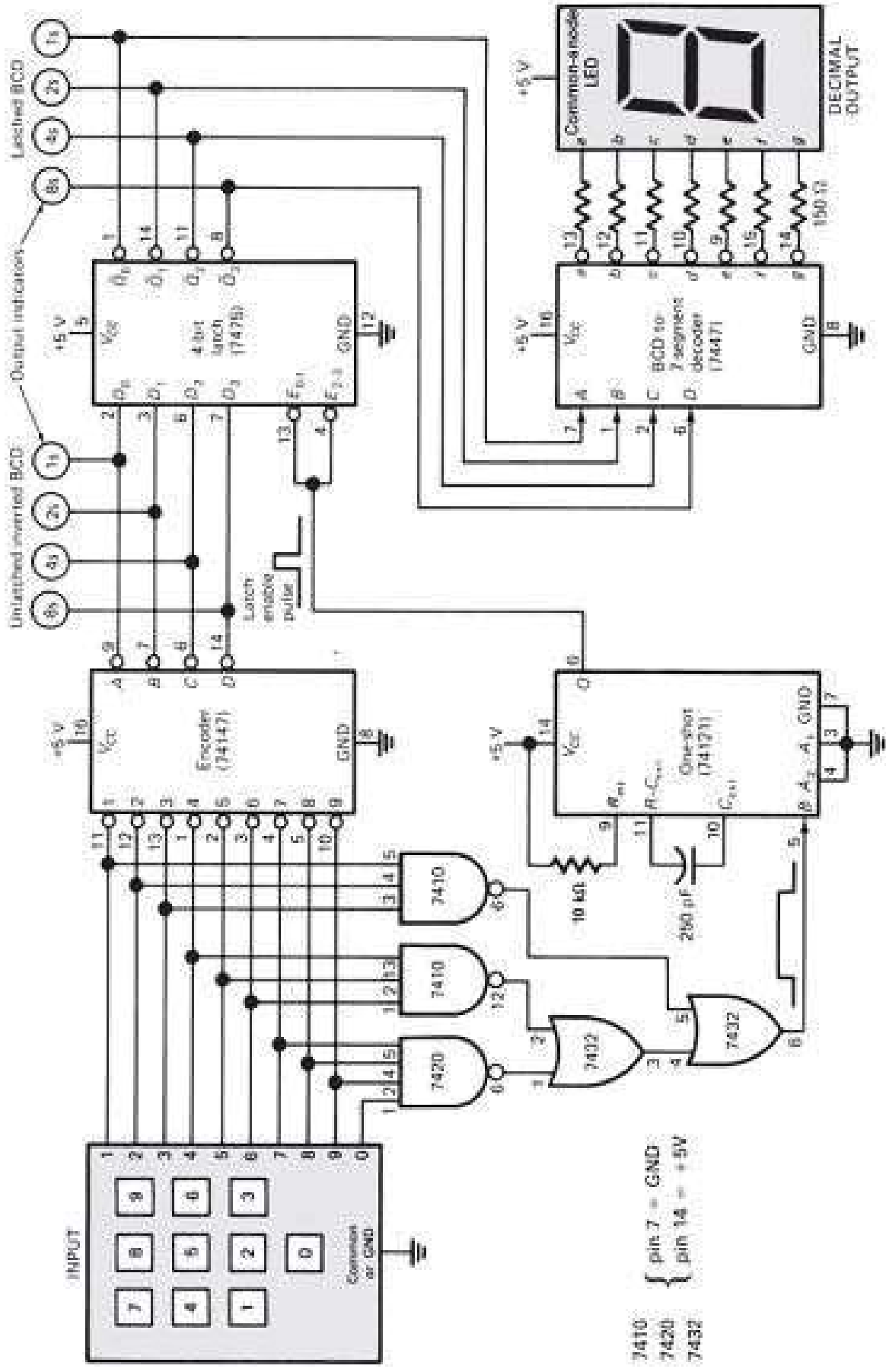

 
Encoder Applications : Optical Encoder for motor position control



Encoder Applications

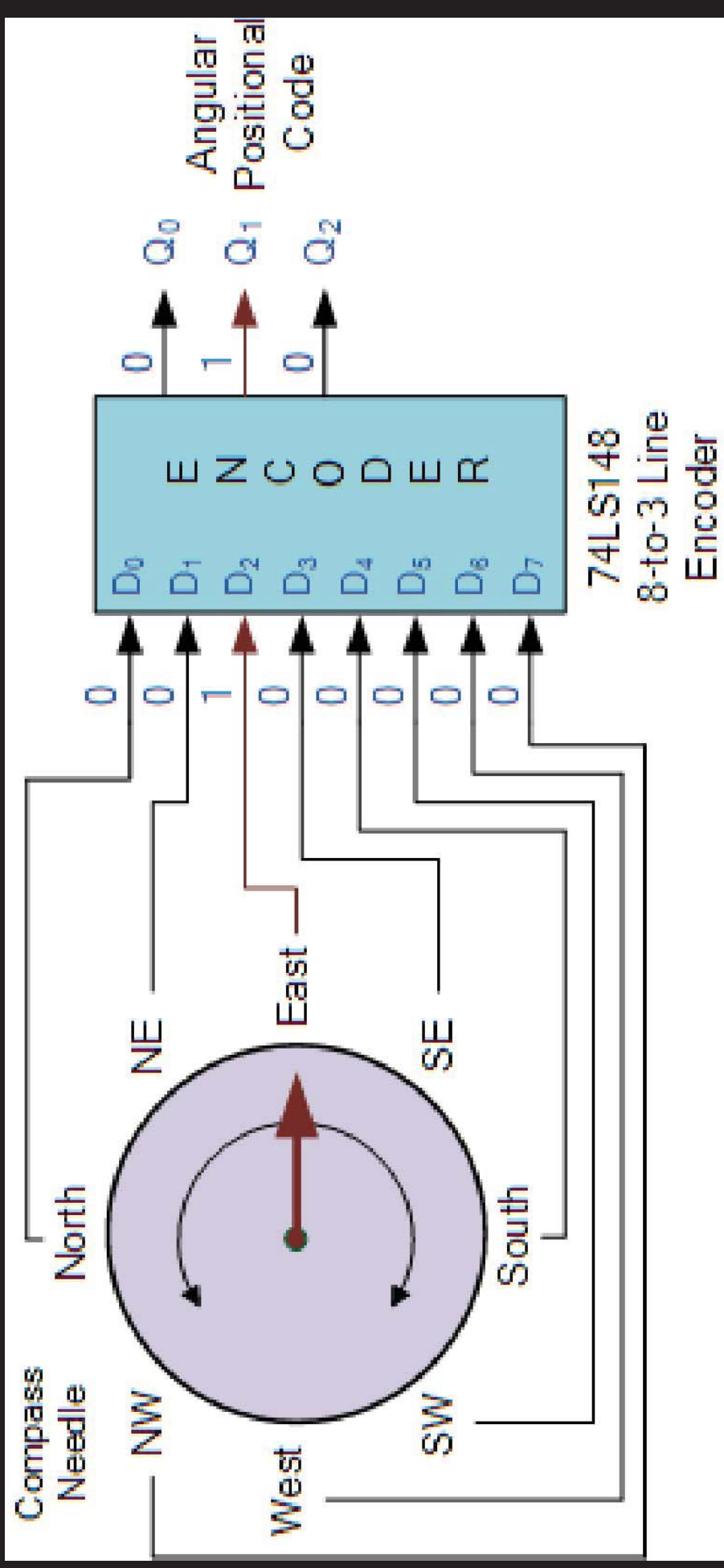

Binary to Gray Using Encoder-Decoder

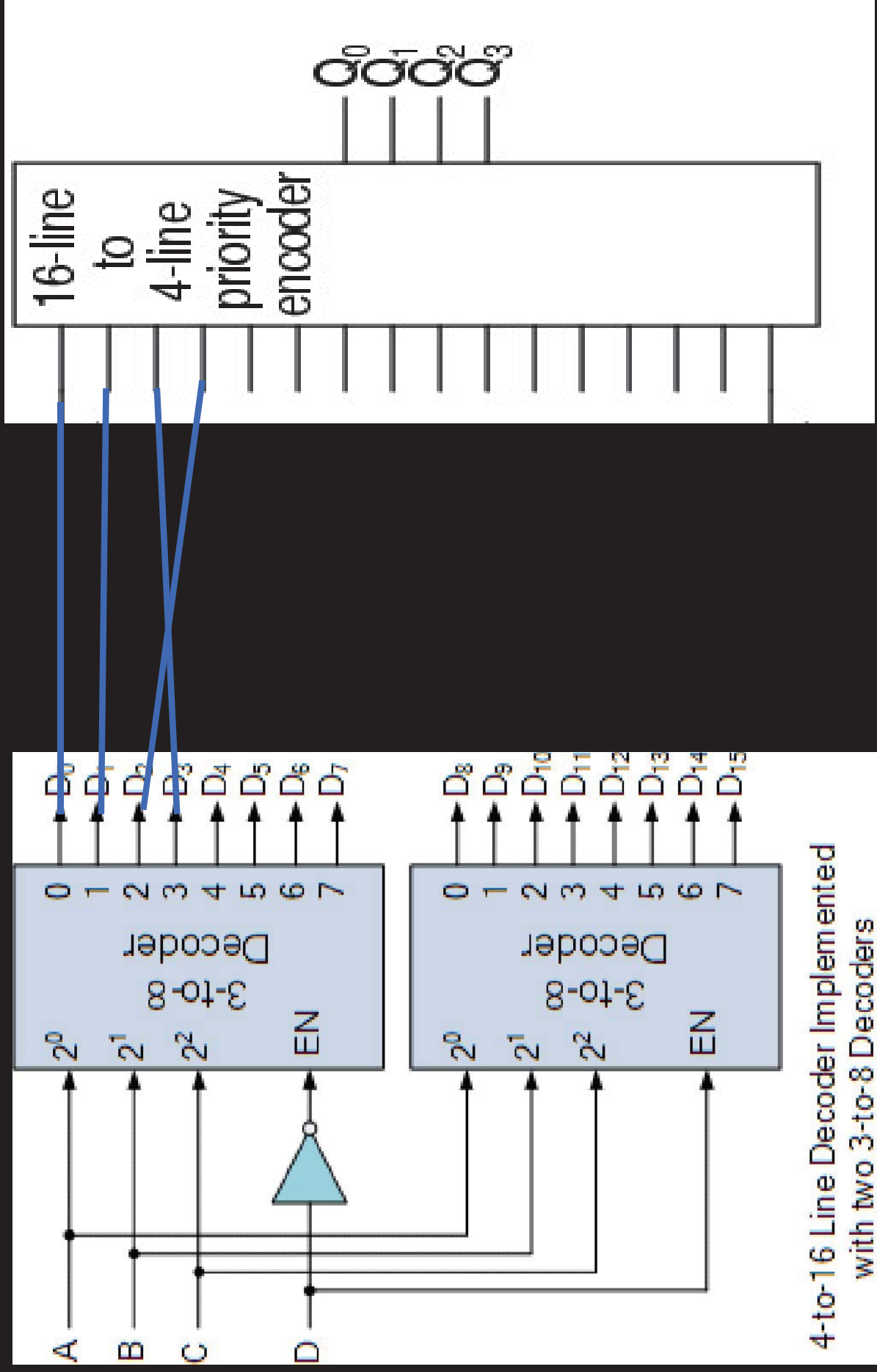


Priority Encoder

Priority Encoder

$$X = D_2 + D_3$$

$$Y = D_1 D_2' + D_3$$

$$V = D_0 + D_1 + D_2 + D_3$$

 

Priority Encoder

| D_0 | D_1 | D_2 | D_3 |
|-------|-------|-------|-------|
| 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 |

| X | Y |
|---|---|
| 0 | 0 |
| 0 | 1 |
| 1 | 0 |
| 1 | 1 |

Encoder

$$X = D_2 + D_3$$

$$Y = D_1 + D_3$$

| D_0 | D_1 | D_2 | D_3 |
|-------|-------|-------|-------|
| 1 | 0 | 0 | 0 |
| X | 1 | 0 | 0 |
| X | X | 1 | 0 |
| X | X | X | 1 |
| 0 | 0 | 0 | 0 |

| X | Y | V |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |
| X | X | 0 |

Priority Encoder

$$X = D_2 + D_3$$

$$Y = D_1 D_2' + D_3$$

$$V = D_0 + D_1 + D_2 + D_3$$



Priority Encoder

If all the inputs are zeros then output is 00 – which indicates that D_0 is 1

This ambiguity can be resolved by **providing one more output.**

Extra Output indicates whether at least one input is equal to 1



Priority Encoder

If two ones appear i.e. if D_1 and D_2 are '1' then both X and Y will be '1' resulting in output 11

Encoder circuits must establish **input priority**

E.g. If high priority is given to inputs with higher subscripts
If both D_1 and D_2 are '1' then resulting o/p should be 10



Encoder

$$X = D_2 + D_3$$

$$Y = D_1 + D_3$$

| D_0 | D_1 | D_2 | D_3 | X | Y |
|-------|-------|-------|-------|---|---|
| 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 1 | 1 |

Limitations:

If two ones appear i.e. if D_1 and D_2 are '1' then both X and Y will be '1' resulting in output 11

If all the inputs are zeros then output is 00 – which indicates that D_0 is 1



Encoder

Encoder - combinational circuit that performs inverse operation of decoder

Has 2^n or fewer input lines and n output lines

An Example:

$$X = D_2 + D_3$$


$$Y = D_1 + D_3$$

| D_0 | D_1 | D_2 | D_3 | X | Y |
|-------|-------|-------|-------|---|---|
| 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 1 | 1 |


Decoder

Implementing function using Decoders
 
$$F = \sum (1, 2, 4, 7) = X'Y'Z + X'YZ' + XY'Z' + XYZ$$



 3 to 8 Decoder using 2nos of 2 to 4 Decoder






Decoder

Can implement a 3 to 8 decoder using two 2 to 4 decoders with enable pin

| X | Y | Z |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |
| 1 | 1 | 1 |

| D ₀ | D ₁ | D ₂ | D ₃ | D ₄ | D ₅ | D ₆ | D ₇ |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |

 




Decoder

Can you implement a 3 to 8 decoder using two 2 to 4 decoders with enable pin

| X | Y | Z |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |
| 1 | 1 | 1 |

| D ₀ | D ₁ | D ₂ | D ₃ | D ₄ | D ₅ | D ₆ | D ₇ |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |

 



Decoder


An Example: 3 to 8 Line Decoder

| X | Y | Z | D ₀ | D ₁ | D ₂ | D ₃ | D ₄ | D ₅ | D ₆ | D ₇ |
|---|---|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |

Direct Implementation – Home Assignment

Decoder

 An Example: 2 to 4 Line Decoder with Enable





Decoder

An Example: 2 to 4 Line Decoder with Enable


| E | X | Y | D ₀ | D ₁ | D ₂ | D ₃ |
|---|---|---|----------------|----------------|----------------|----------------|
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |
| 0 | X | X | 0 | 0 | 0 | 0 |

Decoder with enable pin is also called as **Demultiplexer**

X and Y – Select Lines E- Input line

Decoder

An Example: 2 to 4 Line Decoder

 

Minterms
(0, 1, 2, 3)

Minterm Generating circuit



Decoder

An Example: 2 to 4 Line Decoder

| X | Y |
|---|---|
| 0 | 0 |
| 0 | 1 |
| 1 | 0 |
| 1 | 1 |

| D_0 | D_1 | D_2 | D_3 |
|-------|-------|-------|-------|
| 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 |



Decoder

A Decoder is a combinational circuit that converts binary information from 'n' input lines to 2^n output lines

n to m decoders where $m \leq 2^n$

The name decoder is also used in conjunction with other code converters (e.g. BCD to seven segment decoder)

Digital Design

Lecture 13: Decoders and Encoders



Birla Institute of Technology & Science, Pilani
Hyderabad Campus

2019/2020





Thank You



Next Module

Decoders

Encoders

Multiplexers

Magnitude Comparator


4-Bit Comparator

$$G = G_3 + E_3 \cdot G_2 + E_3 \cdot E_2 \cdot G_1 + E_3 \cdot E_2 \cdot E_1 \cdot G_0$$

$$L = L_3 + E_3 \cdot L_2 + E_3 \cdot E_2 \cdot L_1 + E_3 \cdot E_2 \cdot E_1 \cdot L_0$$

$$E = E_2 \cdot E_1 \cdot E_0$$

Can you draw the circuit ??

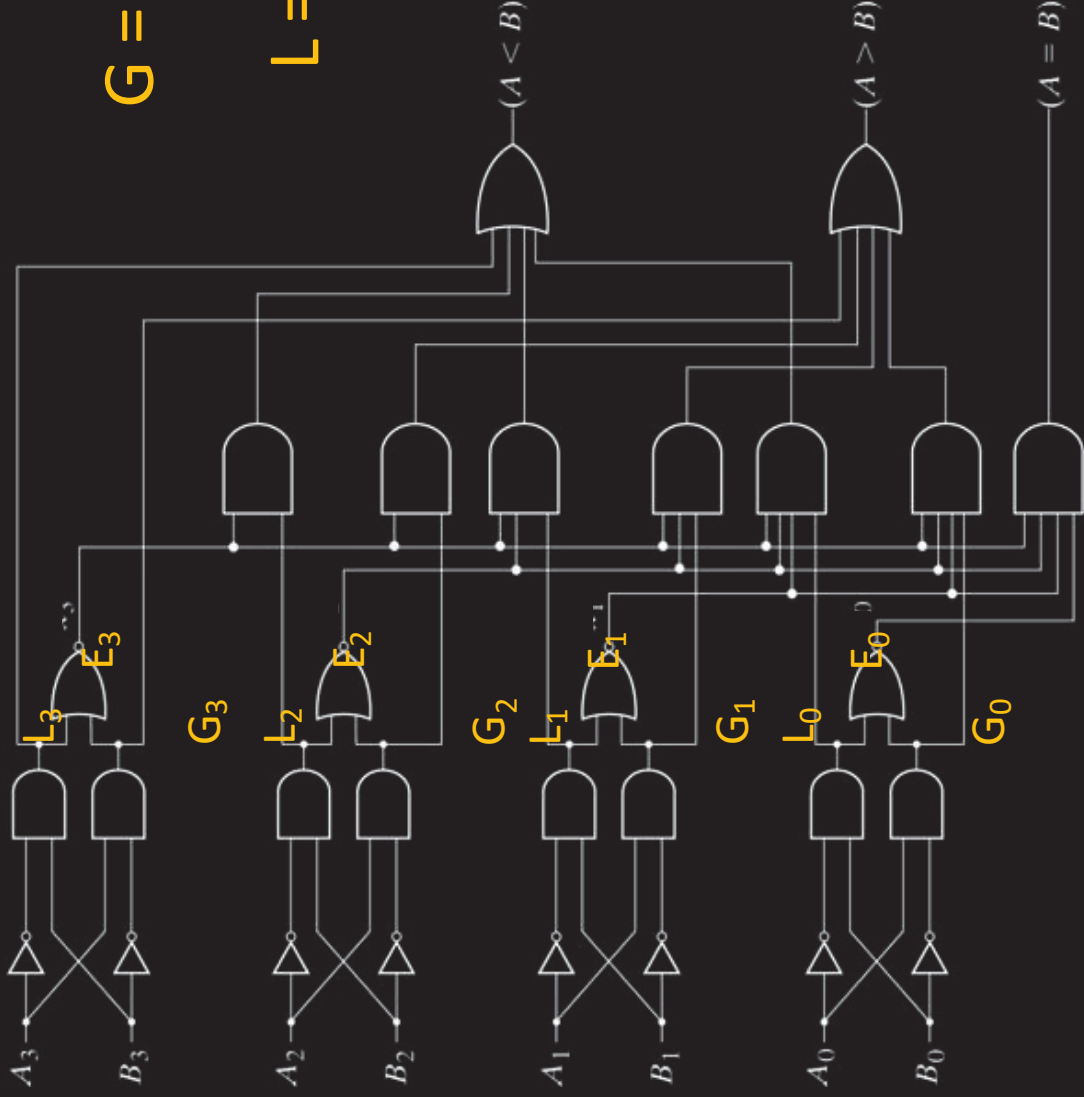



Magnitude Comparator

1 Bit Comparator

$$G = G_0 \quad L = L_0 \quad E = E_0$$

2 Bit Comparator

$$G = G_1 + E_1 \cdot G_0 \quad L = L_1 + E_1 \cdot L_0 \quad E = E_1 \cdot E_0$$

3 Bit Comparator

$$G = G_2 + E_2 \cdot G_1 + E_2 \cdot E_1 \cdot G_0$$

$$L = L_2 + E_2 \cdot L_1 + E_2 \cdot E_1 \cdot L_0$$

$$E = E_2 \cdot E_1 \cdot E_0$$




Magnitude Comparator

2-Bit Comparator


A $A_1 A_0$

B $B_1 B_0$

 

$A < B$ When $A_1 < B_1$ OR
When $A_1 = B_1$ and $A_0 < B_0$

$$L = L_1 + E_1 \cdot L_0$$

 




Magnitude Comparator

2-Bit Comparator


A $A_1 A_0$

B $B_1 B_0$

 

$A > B$ When $A_1 > B_1$ OR
When $A_1 = B_1$ and $A_0 > B_0$

$$G = G_1 + E_1 \cdot G_0$$

 



Magnitude Comparator

2-Bit Comparator

| | |
|---|-----------|
| A | $A_1 A_0$ |
| B | $B_1 B_0$ |



Magnitude Comparator


2-Bit Comparator

A $A_1 A_0$

B $B_1 B_0$

$A = B$ When $A_0 = B_0$ and $A_1 = B_1$

$$E = E_0 \cdot E_1$$

 

Magnitude Comparator

1-Bit Comparator



A_0

B_0

$$G_0 = A_0 B_0'$$

$$L_0 = A_0' B_0$$
  
$$E_0 = (G_0 + L_0)' = (A_0 \oplus B_0)'$$





Magnitude Comparator

1-Bit Comparator

A_0

B_0

Let G_0 indicate greater, L_0 indicate Lesser and E_0 indicate equal

| A_0 | B_0 | G_0 | L_0 | E_0 |
|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 |

$$G_0 = A_0 B_0'$$

$$L_0 = A_0' B_0$$

$$E_0 = (A_0 \oplus B_0)' = (A_0 \odot B_0) = (G_0 + L_0)'$$



Magnitude Comparator

| | | |
|---|---|---|
| 1 | 0 | 1 |
| 1 | 1 | 0 |



Magnitude Comparator

| | | |
|---|---|---|
| 1 | 0 | 1 |
| 1 | 1 | 0 |



Magnitude Comparator

If most significant digits are equal ??

| | | |
|---|---|---|
| 2 | 3 | 4 |
| 2 | 6 | 4 |

Compare the next significant digit

If next significant digit of first number is greater than the next significant digit of second number then

First Number > Second number



Magnitude Comparator

How do you compare two numbers?

| | | |
|---|---|---|
| 2 | 3 | 4 |
| 5 | 6 | 4 |

Compare most significant digit

If most significant digit of first number is greater than the most significant digit of second number then

First Number > Second number




Magnitude Comparator

A Magnitude comparator is a combinational circuit that compares two numbers A and B .

The output of the magnitude comparator are three signals that indicate if $(A > B)$, $(A < B)$, $(A = B)$

Even a 3-bit comparator results in 6 inputs – Too complex to solve using K-maps

A 4x4 binary multiplier

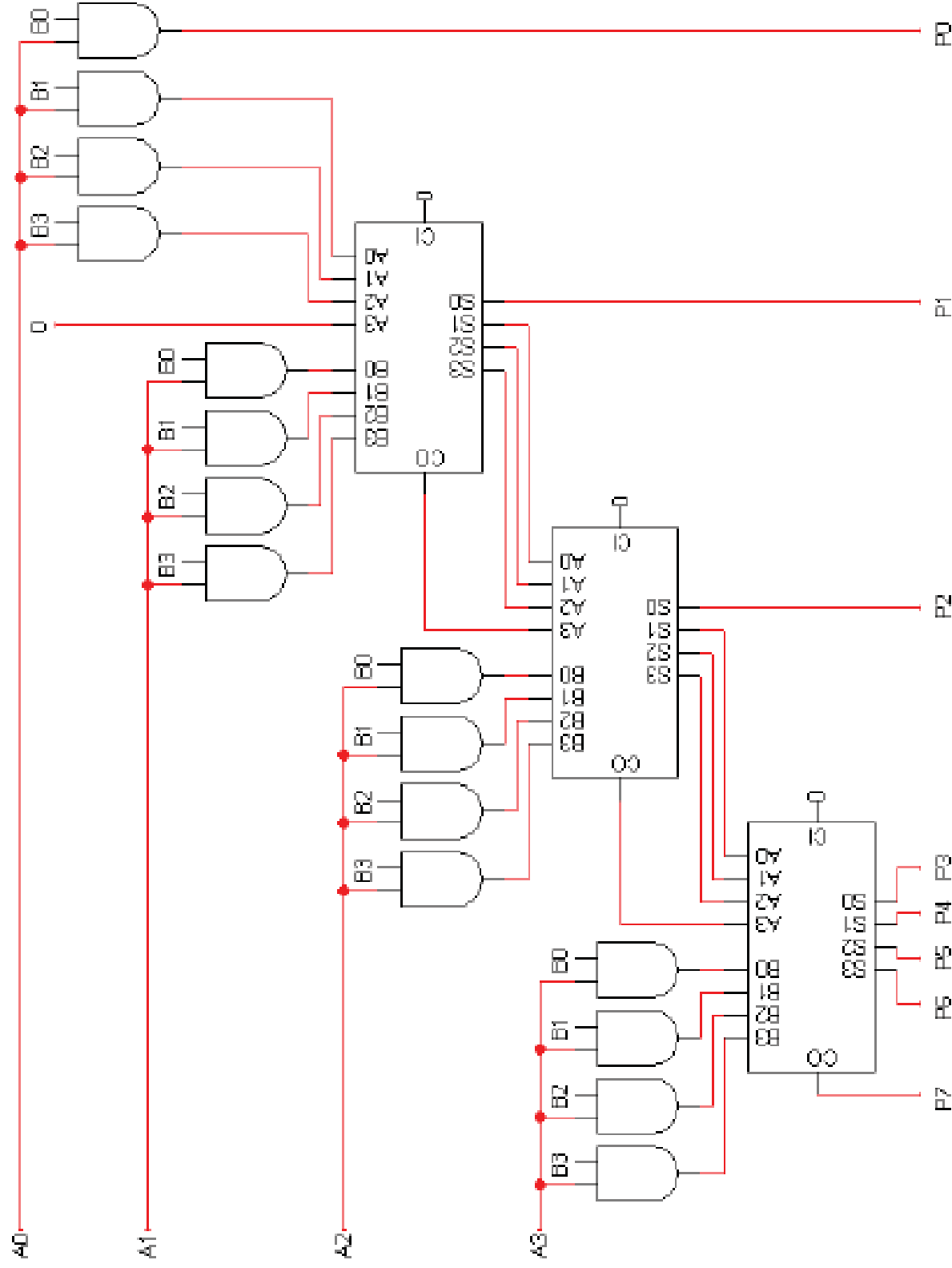



4 x 4 bit Binary Multiplier


Circuit

A_0B_3 A_0B_2 A_0B_1 A_0B_0

A_1B_3 A_1B_2 A_1B_1 A_1B_0

A_2B_3 A_2B_2 A_2B_1 A_2B_0

A_3B_3 A_3B_2 A_3B_1 A_3B_0

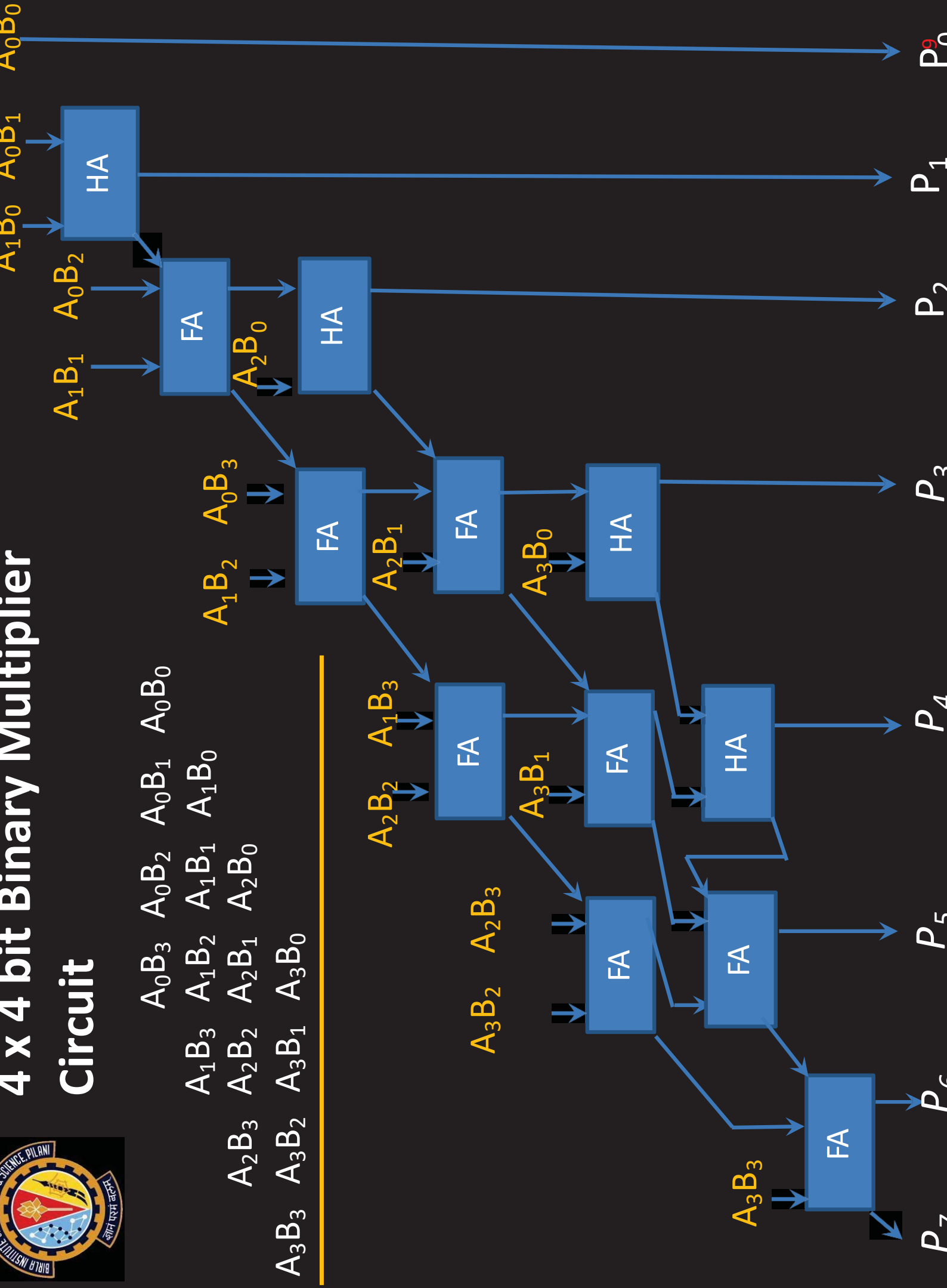




Binary Multiplier (4-bit x 4-bit)

(Multiplicand) $B_3 B_2 B_1 B_0$
(Multiplier) $A_3 A_2 A_1 A_0$

 $A_0 B_3 \quad A_0 B_2 \quad A_0 B_1 \quad A_0 B_0$ $A_1 B_3 \quad A_1 B_2 \quad A_1 B_1 \quad A_1 B_0$ $A_2 B_3 \quad A_2 B_2 \quad A_2 B_1 \quad A_2 B_0$ $A_3 B_3 \quad A_3 B_2 \quad A_3 B_1 \quad A_3 B_0$



 Binary Multiplier Circuit (2-bit x 2-bit)



B₁ B₀

A₁ A₀

x

B₁A₀ B₀A₀

B₁A₁ B₀A₁

P₃ P₂ P₁ P₀



Binary Multiplier (2-bit x 2-bit)

$$\begin{array}{r}
 \begin{array}{r}
 \text{B}_1 \quad \text{B}_0 \\
 \times \quad \begin{array}{r} \text{A}_1 \quad \text{A}_0 \end{array} \\
 \hline
 \begin{array}{r}
 \text{B}_1\text{A}_0 \quad \boxed{\text{B}_0\text{A}_0} \\
 \text{B}_1\text{A}_1 \quad \text{B}_0\text{A}_1 \\
 \hline
 \text{P}_3 \quad \text{P}_2 \quad \text{P}_1 \quad \text{P}_0
 \end{array}
 \end{array}$$

Gate for 1-bit Multiplication (B_0A_0) ?

| A_0 | B_0 | F |
|--------------|--------------|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |





Binary Multiplier

$$\begin{array}{r} 2 \quad 3 \\ \times 5 \quad 2 \\ \hline 4 \quad 6 \\ 1 \quad 1 \quad 5 \\ \hline 1 \quad 1 \quad 9 \quad 6 \end{array}$$

$$\begin{array}{r} 1 \quad 0 \\ \times 1 \quad 1 \\ \hline 1 \quad 0 \\ 1 \quad 1 \quad 0 \\ \hline 1 \quad 1 \quad 1 \quad 0 \end{array}$$

$$2 \times 3 = 6$$



Binary Multiplier

2 3

x 5 2

4 6

1 1 5

1 1 9 6

1 0

x 1 1




Multiplier

2 3

x 5 2

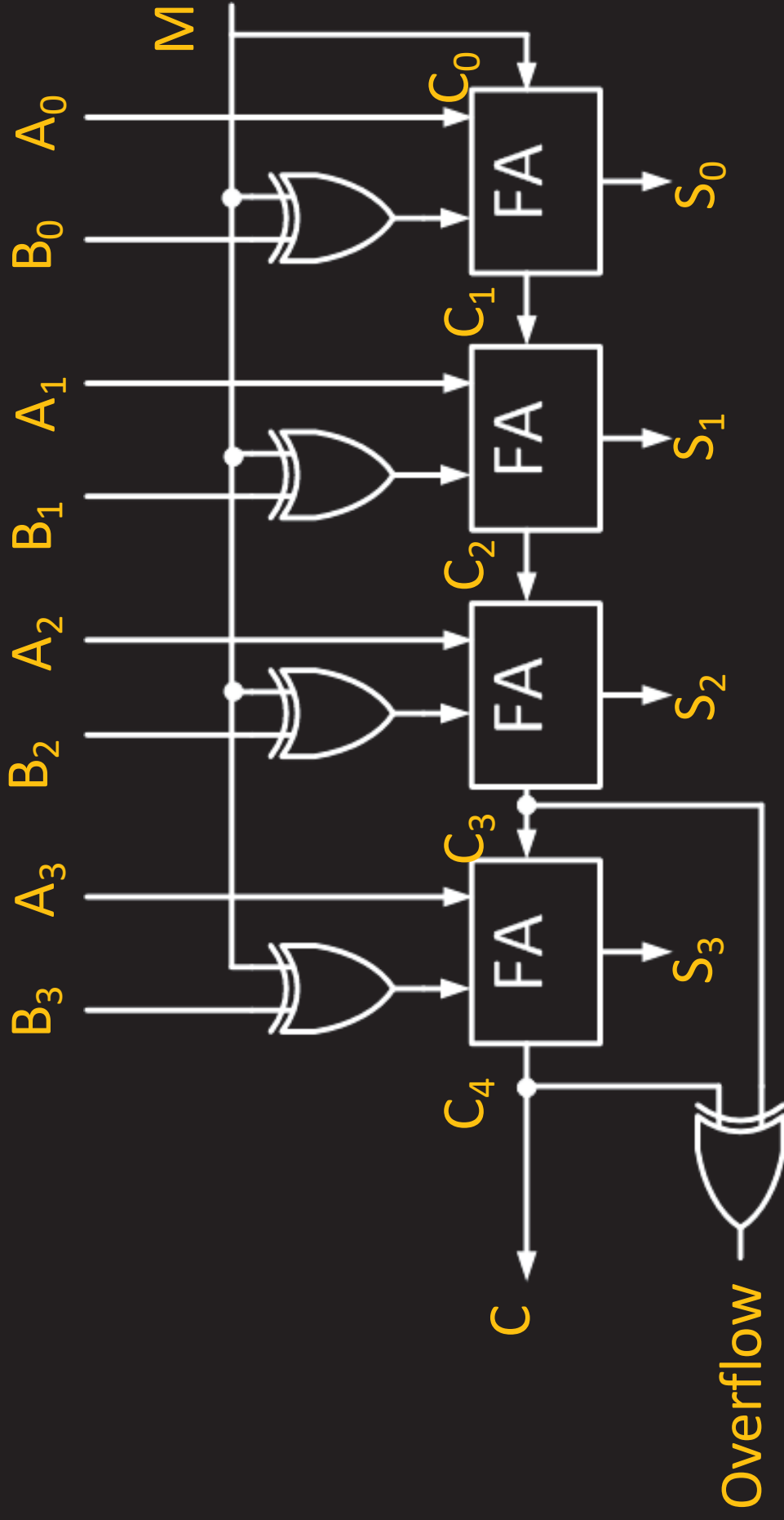4-bit Adder subtractor with overflow detection



Digital Design

Lecture 12:

Binary Multipliers and Magnitude Comparators




Birla Institute of Technology & Science, Pilani
Hyderabad Campus

9/18/2021



Thank you


 


4-Bit Adder with Carry Lookahead

- Let's look at the carry out equations for specific bits, using the general equation from the previous page $C_{i+1} = G_i + P_i C_i$.

$$C_1 = G_0 + P_0 C_0$$
  
$$\begin{aligned} C_2 &= G_1 + P_1 C_1 \\ &= G_1 + P_1 (G_0 + P_0 C_0) \\ &= G_1 + P_1 G_0 + P_1 P_0 C_0 \end{aligned}$$



A faster way to compute carry outs

- Instead of waiting for the carry out from each previous stage, we can minimize the delay by computing it directly with a two-level circuit.
- First we'll define two functions.
 - The “generate” function G_i produces 1 when there *must* be a carry out from position i (i.e., when A_i and B_i are both 1).


$$G_i = A_i B_i$$

- The “propagate” function P_i is true when an incoming carry is propagated (i.e, when $A_i=1$ or $B_i=1$, but not both).

$$P_i = A_i \oplus B_i$$

- Then we can rewrite the carry out function.


$$C_{i+1} = G_i + P_i C_i$$

 

| A_i | B_i | C_i | C_{i+1} |
|-------|-------|-------|-----------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |


Ripple carry delays

 - This is called a **ripple carry adder**, because the inputs A0, B0 and C1 “ripple” leftwards until C0 and S3 are produced.
- Ripple carry adders are slow!
 - There is a very long path from A0, B0 and C1 to C0 and S3.
 - For an n -bit ripple carry adder, the longest path has $2n+1$ gates.
 - The longest path in a 64-bit adder would include 129 gates!





Design of a Carry Look Ahead adder

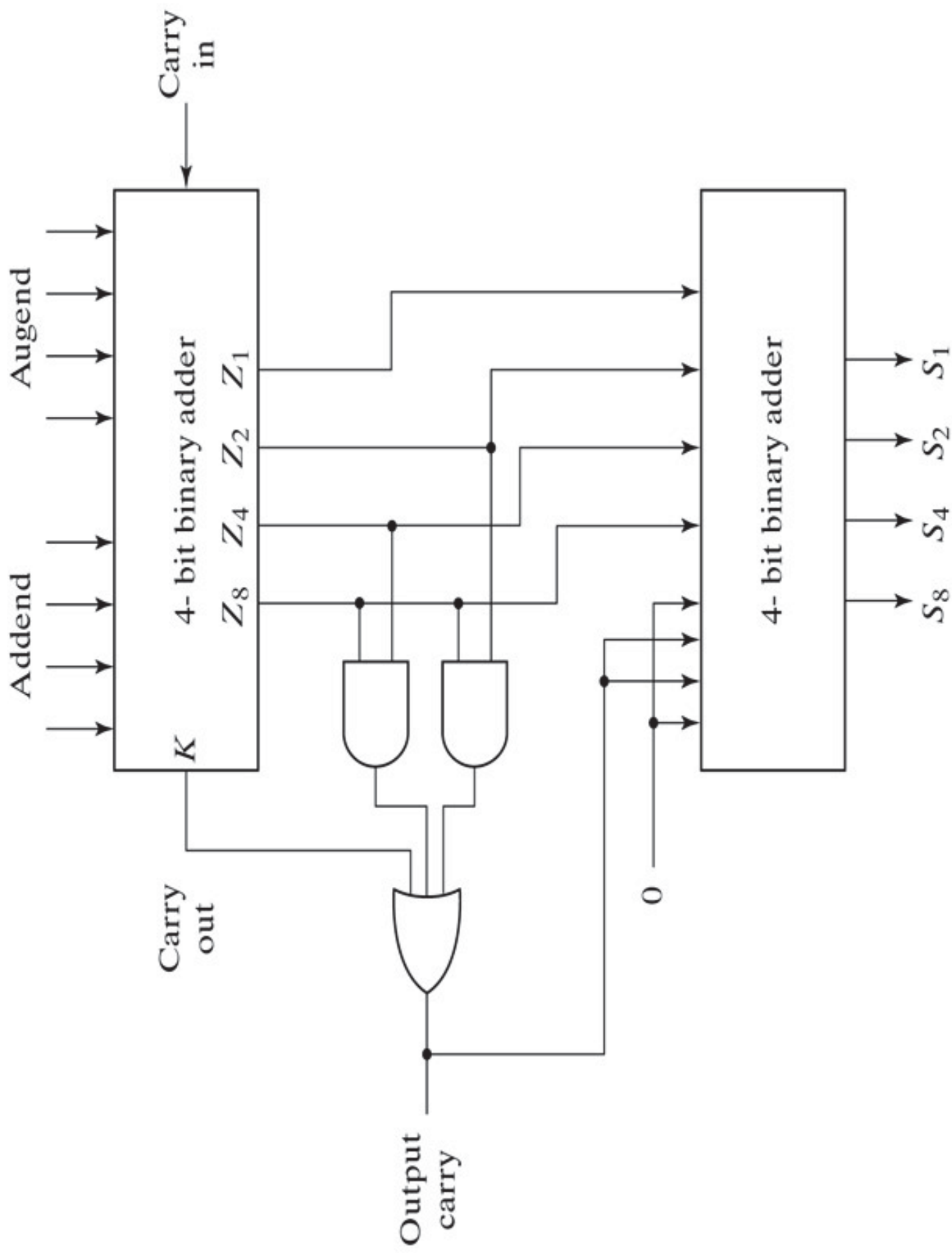

Block Diagram of a BCD Adder



BCD Adder

Principle:


- Is Binary sum less than or equal to 1001 (9 in decimal)?
- For Binary sum more than 1001, add 0110 (6 in decimal) as **correction factor**
- Circuit needs modification accordingly

Larger Adder

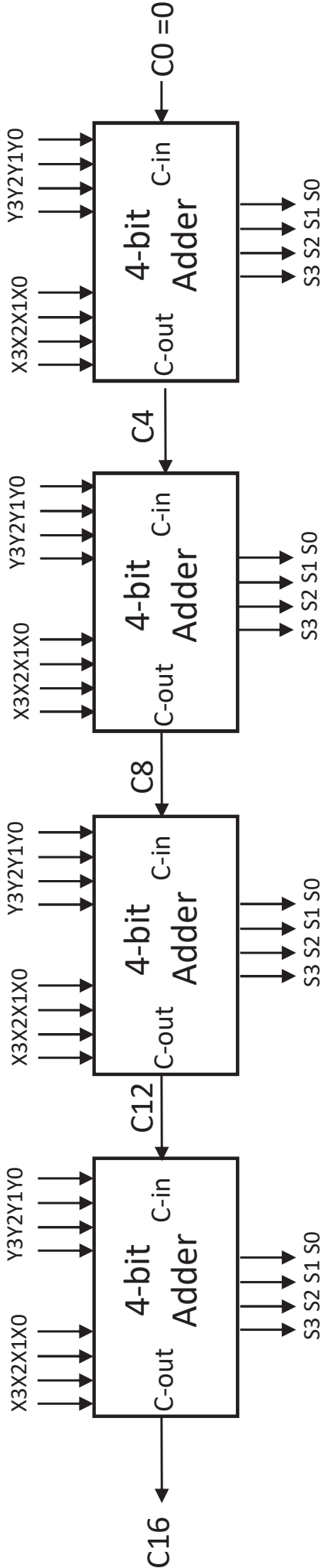Example: 16-bit adder using 4, 4-bit adders

Adds two 16-bit inputs X (bits X0 to X15), Y (bits Y0 to Y15) producing a 16-bit Sum S (bits S0 to S15) and a carry out C1 from most significant position.

Data inputs to be added X (X0 to X15) , Y (Y0-Y15)



Sum output S (S0 to S15)


Implementation of a Subtractor using Adder




The subtraction $X-Y$ can be performed by taking the 2's complement of Y and adding to X .

$$\begin{aligned} X-Y &= X + 2C(Y) \\ &= X + 1C(Y) + 1 \\ &= X + Y' + 1 \end{aligned}$$

Inputs to be subtracted

 

4 bit Binary Adder

 


*Each full adder represents a bit position 'j' (from 0 to n-1).

*Each carry out (C_out) from a full adder at position j is connected to the carry in C-in of the full adder at the higher position j+1.

4 bit Binary Adder

Inputs to be added

 

Sum Output


A 4-bit Adder is used to add two 4-bit binary numbers can be built by connecting in series/cascaded 4 full adders.

FULL ADDER

Adding two single-bit binary values, X, Y and a carry input bit C_in, produces a sum bit S and a carry out C_out bit.

(X + Y + C_in)

| X | Y | C-in | S | C-out |
|---|---|------|---|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

 


Building blocks - contd

Subtracting a single-bit binary value Y from another X (i.e. $X - Y$) and producing a difference bit D and a borrow out bit B_out. This operation is called half addition – **Half Subtractor**

Half Subtractor Truth Table

| Inputs | | Outputs | |
|--------|---|---------|-------|
| X | Y | D | B_out |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

 


$$D(X,Y) = \Sigma (1,2)$$

$$D = X'Y + XY'$$

$$D = X \oplus Y$$

$$B_out(x, y)$$

$$B_out = X'Y$$

 

Adders : Building blocks

Adding two single-bit binary values, X, Y and produces a sum S and a carry out C_out

This operation is called half addition – **Half Adder**

Half Adder Truth Table

| Inputs | | Outputs | |
|--------|---|---------|------|
| X | Y | S | Cout |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |


$$S(X,Y) = \Sigma (1,2)$$

$$S = X'Y + XY'$$


$$S = X \oplus Y$$

$$C\text{-out}(x, y)$$

$$C\text{-out} = XY$$

 

Blocks of a Digital Processor

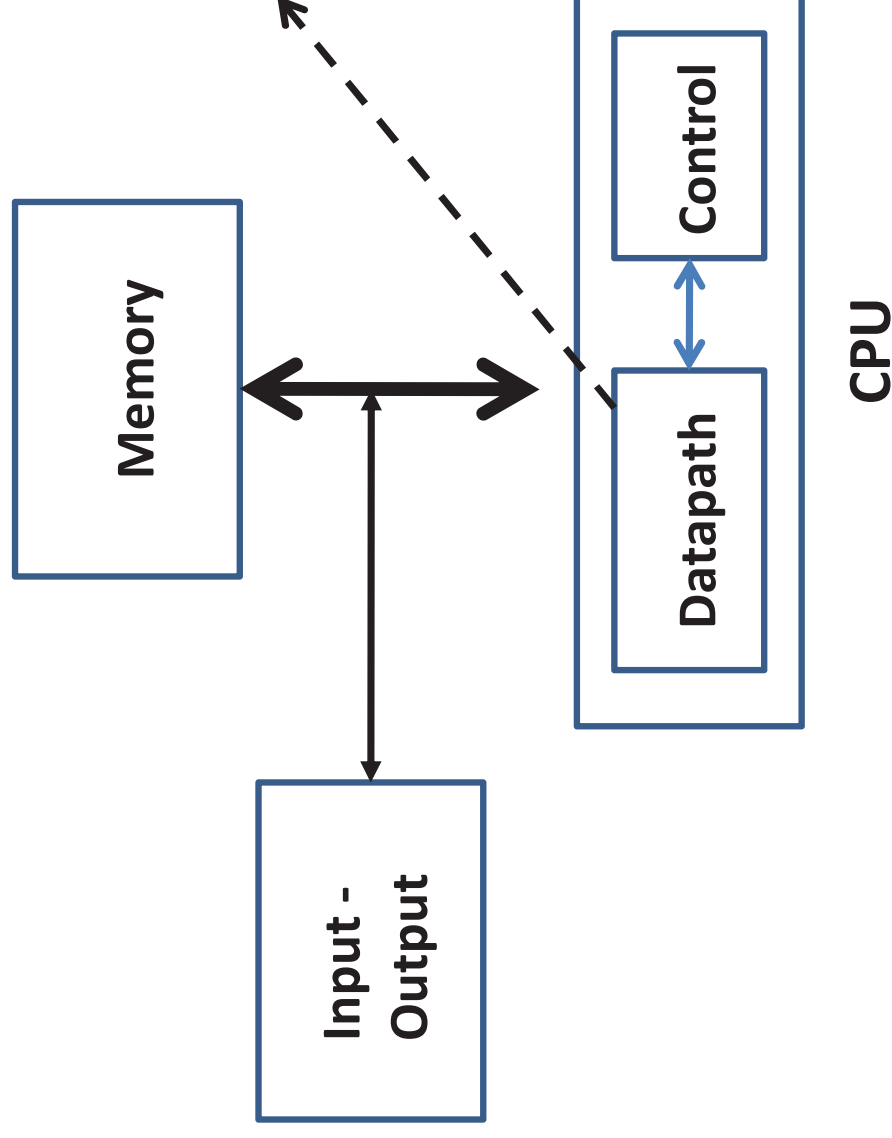

Digital Design


Lecture 11: Combinational Logic and Arithmetic Circuits




Thank you

Parity Generator/Checker using IC's

 The IC 74180 does the function of parity generation as well as checking. The 9 bit (8 data bits, 1 parity bit) Parity Generator/Checker is shown in the below figure.



 Parity checker Logic Circuit for 5-bit received message



An additional 4th EX-OR Gate is introduced

K-Map For Even Parity Checker

| CD \ AB | | | | |
|---------|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | 0 | 1 | 0 | 1 |
| 01 | 1 | 0 | 1 | 0 |
| 11 | 0 | 1 | 0 | 1 |
| 10 | 1 | 0 | 1 | 0 |

$$= (A \oplus B \oplus C \oplus D)$$



Example: A 4 bit Even Parity Checker Truth Table

| 4-bit received message | | | | Parity error check P |
|------------------------|---|---|---|----------------------|
| A | B | C | D | |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 |



Even Parity Checker

In even parity checker if the error bit (E) is equal to '1', then we have an error. If error bit $E=0$ then indicates there is no error.

Error Bit (E) =1, error occurs

Error Bit (E) =0, no error

Odd Parity Checker


In odd parity checker if an error bit (E) is equal to '1', then it indicates there is no error. If an error bit $E=0$ then indicates there is an error.

Error Bit (E) =1, no error

Error Bit (E) =0, error occurs

K-map for Odd Parity generator and its reduced expression for logic circuit design

| | | BC | | | |
|---|---|--------|--------|--------|--------|
| | | 00 | 01 | 11 | 10 |
| A | 0 | 0 1 | 1 1 | 3 1 | 2 |
| | 1 | 4 1 | 5 1 | 7 | 6 1 |

 

$$\begin{aligned}
 P_{od} &= (\bar{A} \bar{B} \bar{C} + A \bar{B} C) + (\bar{A} B C + A B \bar{C}) \\
 &= \bar{C} (A B + \bar{A} \bar{B}) + B (A \bar{B} + \bar{A} B) \\
 &= \bar{C} (A \oplus B) + C (A \oplus B) \\
 &= \bar{C} \bar{X} + C X = C \odot X = C \odot A \oplus B
 \end{aligned}$$




Odd Parity Generator

Odd Parity Generator Truth Table

| ABC | Odd Parity |
|-------|------------|
| 0 0 0 | 1 |
| 0 0 1 | 0 |
| 0 1 0 | 0 |
| 0 1 1 | 1 |
| 1 0 0 | 0 |
| 1 0 1 | 1 |
| 1 1 0 | 1 |
| 1 1 1 | 0 |

K-map for Even Parity generator and its reduced expression for logic circuit design

| | | BC | | | |
|---|---|--------|--------|--------|--------|
| | | 00 | 01 | 11 | 10 |
| A | 0 | 0 1 | 1 1 | 3 | 2 1 |
| | 1 | 4 1 | 5 | 7 1 | 6 |

 

$$\begin{aligned}
 P_{ev} &= (A \bar{B} \bar{C} + \bar{A} \bar{B} C) + (A B C + \bar{A} B \bar{C}) \\
 &= \bar{B} (A \bar{C} + \bar{A} C) + B (A C + \bar{A} \bar{C}) \\
 &= \bar{B} (A \oplus C) + B (\overline{A \oplus C}) = \bar{B}x + B\bar{x} = B \oplus x = B \oplus A \oplus C
 \end{aligned}$$

Even Parity Generator

Even Parity Generator Truth Table

| A B C | Even Parity |
|-------|-------------|
| 0 0 0 | 0 |
| 0 0 1 | 1 |
| 0 1 0 | 1 |
| 0 1 1 | 0 |
| 1 0 0 | 1 |
| 1 0 1 | 0 |
| 1 1 0 | 0 |
| 1 1 1 | 1 |



Parity Generation and Checking:

- Parity is used to detect errors in transmitted data caused by noise or other disturbances.
- A parity bit is an extra bit that is added to a data word and can be either odd or even parity.
- In an even parity system, the sum of all the bits (including the parity bit) is an even number
- In an odd parity system the sum of all the bits must be an odd number.
- The circuit that creates the parity bit at the transmitter is called the parity generator.
- The circuit that determines if the received data is correct is the parity checker.
- Parity is good for detecting a single bit error only.
- The parity generator and the parity checker can both be built using Exclusive-OR gates.



- A combinational circuit consists of logic gates whose outputs at any time are determined by combining the values of the inputs.
- For n input variables, there are 2^n possible binary input combinations.
- For each binary combination of the input variables, there is one possible output.

Digital Design

CS / EEE / ECE/ INSTR F215

Lecture 10: Combinational Circuits



Birla Institute of Technology & Science, Pilani
Hyderabad Campus

9/15/2021

