


# Digital Logic Families

# Digital Logic Families

- ICs are also classified based on their specific circuit technology, known as *digital logic family*.
- Each family has its own basic electronic components (NAND, NOR, and NOT gates), used to build complex digital circuits.
- Various digital logic families have been introduced and used over the years.


# Digital Logic Families

## (in chronological order)

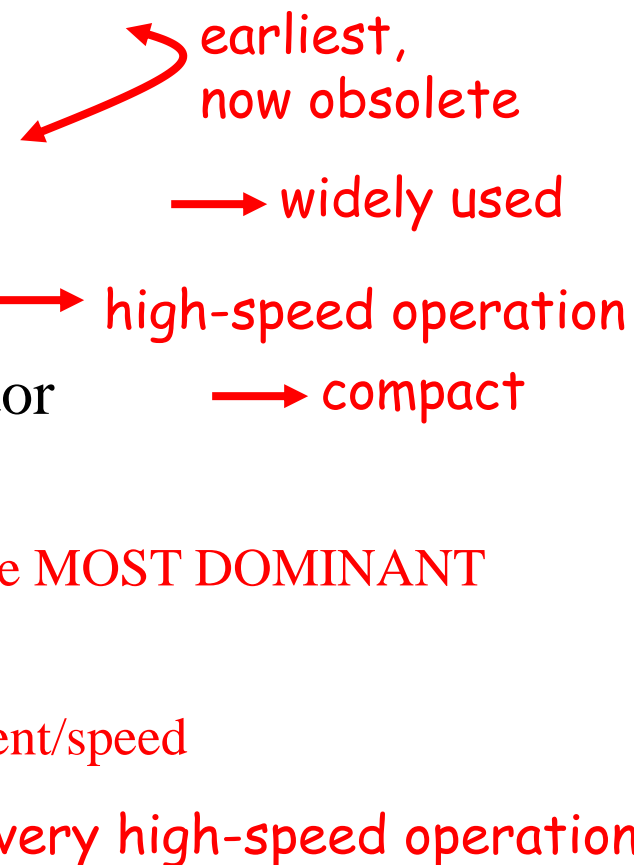
- RTL: Resistor-Transistor Logic
  - DTL: Diode-Transistor Logic
  - TTL: Transistor-Transistor Logic
  - ECL: Emitter-coupled Logic
  - MOS: Metal-Oxide Semiconductor
  - CMOS: Complementary MOS
    - Low power dissipation, currently the MOST DOMINANT
  - BiCMOS: Bipolar CMOS
    - CMOS and TTL for additional current/speed
  - GaAs: Gallium-Arsenide
- 
- earliest,  
now obsolete
- widely used
- high-speed operation
- compact
- very high-speed operation
 
# Defining Characteristics of Digital Logic Families

- ***Fan-in***: # of gate inputs.
- ***Fan-out***: # of standard loads a gate's output can drive.
- ***Noise margin***: max external noise tolerated.
- ***Power dissipation***: power consumed by the gate (dissipated as heat).
- ***Propagation delay***: time required for an input signal change to be observed at an output line.




(a) High-level output

 


(b) Low-level output

Fan-Out Computation

 

Measurement of Propagation Delay

 


Signals for Evaluating Noise Margin

# Power Dissipation ( $P_D$ )


- **Expressed in Milliwatts**
- **$PD = V_{CC} * I_{CC}$**
- **$I_{CC(avg)} = (I_{CCH} + I_{CCL}) / 2$**




# **TTL LOGIC FAMILY**

 


(a) Inverter circuit

 

(a) Inverter circuit

 


(b) Transistor-base characteristic

 

(c) Transistor-collector characteristic

Silicon *npn* Transistor Characteristics

 

(a) Inverter circuit

$$R_C = 1\text{k}\Omega, R_B = 22\text{k}\Omega, \beta = 50$$

$V_{CC} = 5\text{V}$ , find  $V_o$  for

$V_i = 0.2\text{V}$  and  $V_i = 5\text{V}$

# BJT Characteristics

- Base-Emitter voltage less than 0.6V ;  $I_B = 0$   
: **Cut-Off region**
- Base-Emitter voltage more than 0.6V,  
transistor starts conducting - **active region**  
 $I_C = \beta I_B$
- Maximum collector current  $I_C = V_{CC}/R_C$


- **In the cut-off region  $V_{BE} < 0.6V$ ,  
 $V_{CE}$  – open circuit,  $I_C$ ,  $I_B$  negligible**
- **In the active region  $V_{BE}$  about 0.7  
 $V_{CE}$  wide range and  $I_C = \beta I_B$**
- **In the saturation region  $V_{BE}$  hardly  
changes,  $V_{CE} = 0.2V$**

<b>TTL Series name</b>	<b>Prefix</b>
<b>Standard</b>	<b>74</b>
<b>Low-power</b>	<b>74L</b>
<b>High-speed</b>	<b>74H</b>
<b>Schottky</b>	<b>74S</b>
<b>Low-power Schottky</b>	<b>74LS</b>
<b>Advanced Schottky</b>	<b>74AS</b>
<b>Advanced Low power- Schottky</b>	<b>74ALS</b>
<b>Fast</b>	<b>74F</b>

 
## **Three Types of TTL gates**

- Open - collector output**
- Totem- pole output**
- Three- state output**






Open-Collector TTL Gate

 


Open-Collector TTL Gate

 - **Output impedance of a gate is resistive plus Capacitive load**
- **For output low to high transition C charges exponentially through RC**
- **R is  $R_L$  ( external) in open collector**
- **With active pull-up delay can be reduced**




TTL Gate with Totem-Pole Output

# MOS Transistor

 


(a) p-channel


 


(b) n-channel


Basic Structure of MOS Transistor

 


(a) p-channel

  

(b) n-channel

 


Symbols for MOS Transistors

 


(a) Inverter


$n$ -channel MOS Logic Circuits

 


(b) NAND gate

 


(a) Inverter

 

(b) NAND gate

 

(a) Inverter

 


(c) NOR gate


*n*-channel MOS Logic Circuits




# Design the logic Using NMOS

$$Z = (A(D+E) + BC)'$$

 


 

(a) Inverter

 


(a) Switch model

 


(b) Logical model


*CMOS* inverter

 

(a) Inverter

 

(b) NAND gate

 

(c) NOR gate

# Design the logic Using CMOS

$$Z = (A(D+E) + BC)'$$

